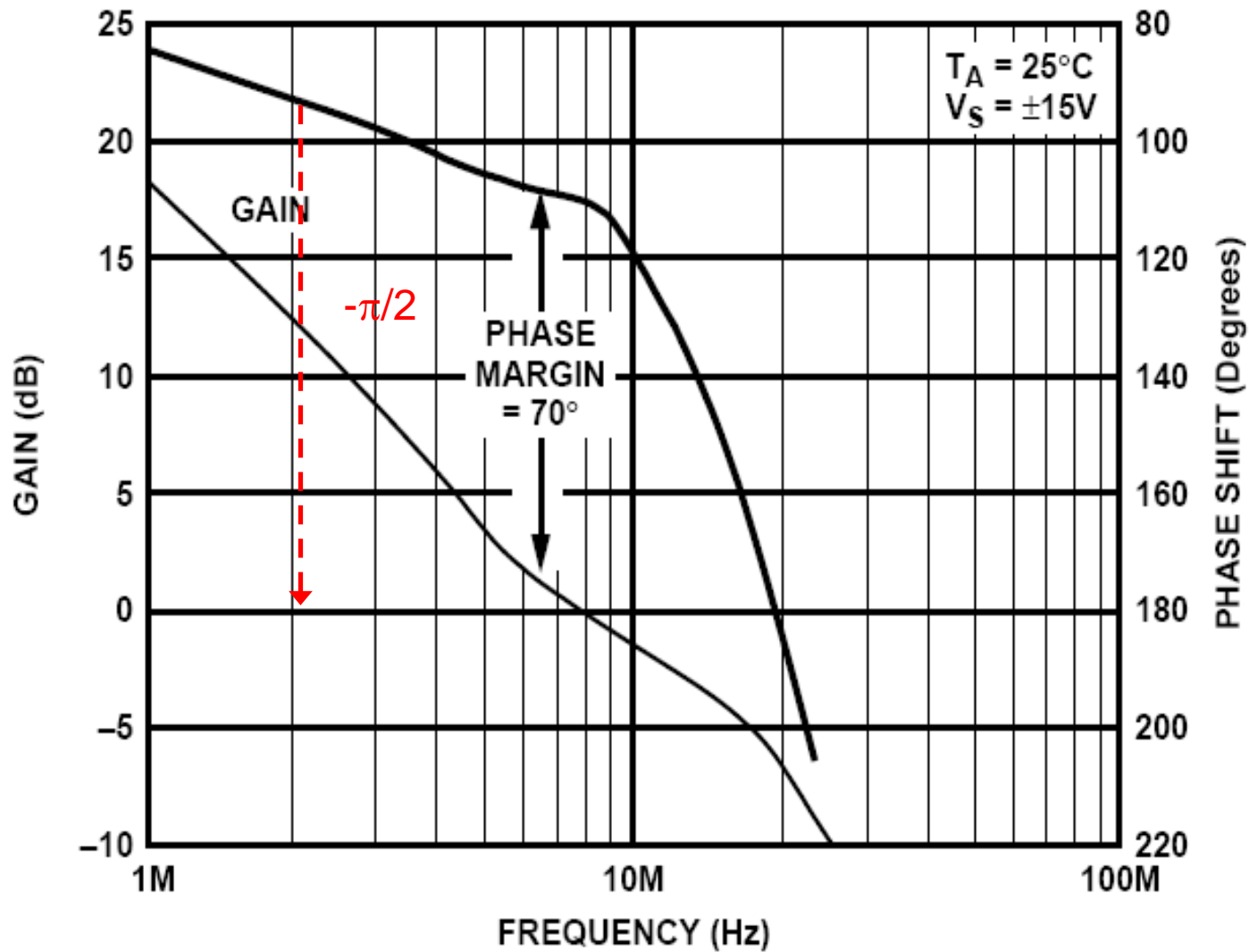


Op-amp Buffet

MENU:

- Op-amps and complex impedances.
 - **Integrators** and active low-pass filters.
 - **Differentiators** and active high-pass filters.
- Op-amps and **power amplifiers**.
 - Op-amps with transistor outputs.
- Op-amp **constant current sources**.
- Op-amps and **photodiodes**.


Watch out for positive feedback !!!



When would you use an op-amp integrator or differentiator?

- **Do not use an op-amp for a high-pass or low-pass filter.**
 - R and C components work up to very high frequencies, but op-amps have limited bandwidth.
 - **exception:** RC op-amp circuits can imitate the impedance of a perfect inductor → make ideal “RLC” circuits.
- RC op-amp circuits are good if you need a true differentiator or integrator, or very high fidelity performance.
 - more on this next week.
 - A true integrator can measure charge (particle physics).
- Integrators and differentiators were the basis of analog computers (outdated).


Op-amps for power amplifiers

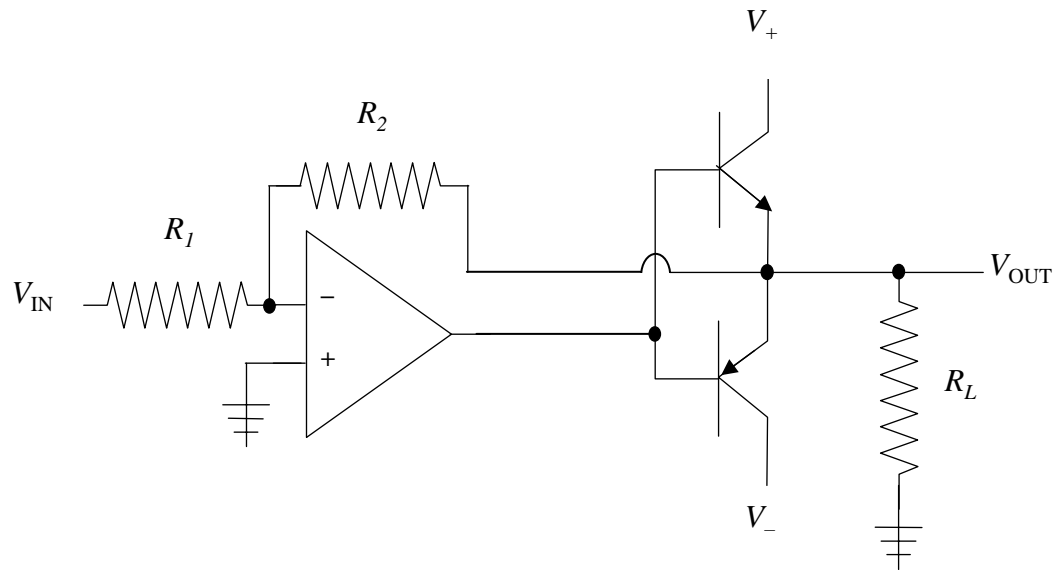

Inverting amplifier with a push-pull buffer
inside the feedback loop.


If the signal is not too fast (i.e. slower than the slew rate $\sim 1 \text{ V}/\mu\text{s}$), then the feedback of the op-amp will significantly suppress cross-over distortion (which is due to the 0.6 V diode drop of the base-emitter path).

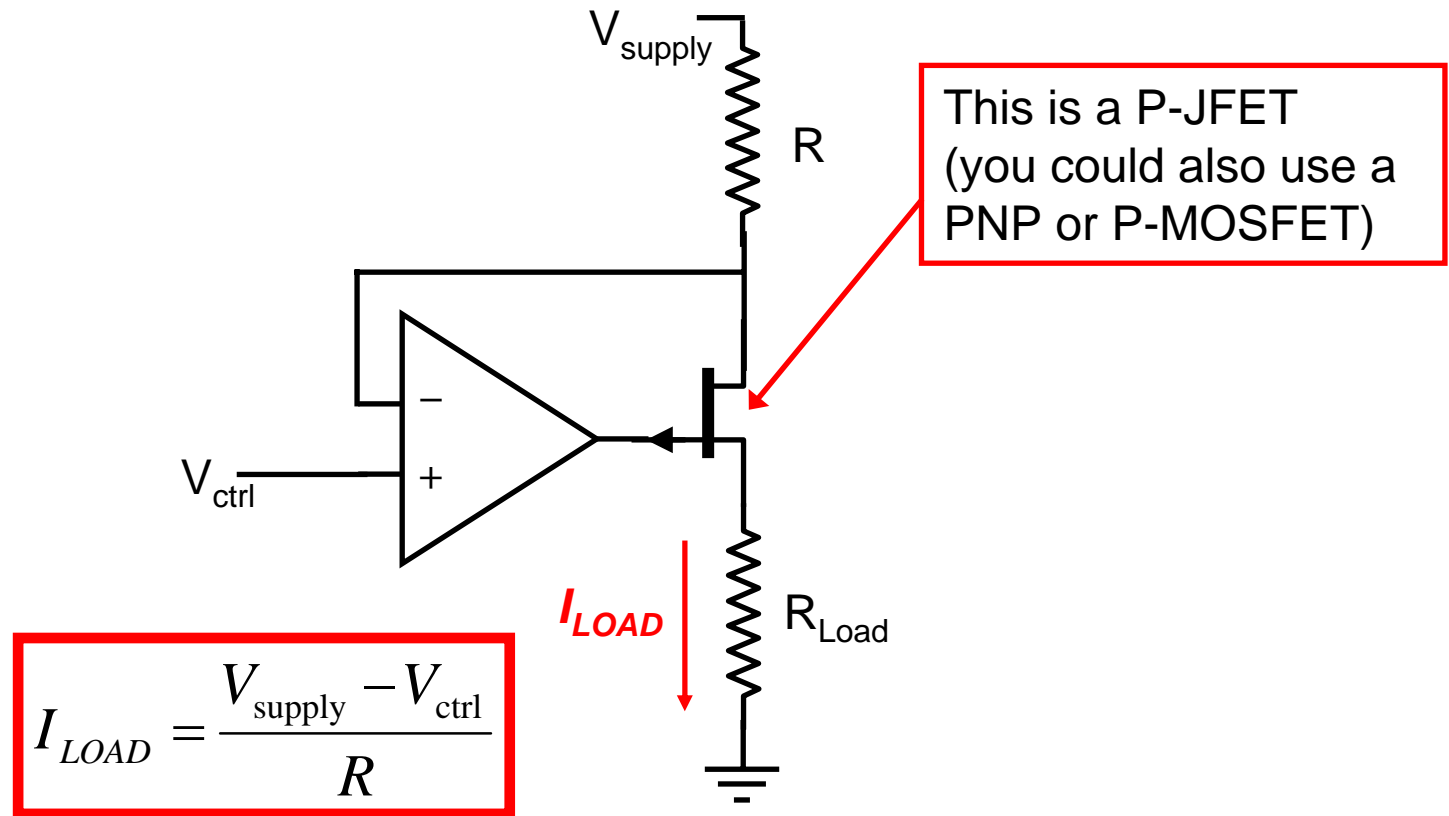Constant Current Source with Grounded Load




Bonus Question:

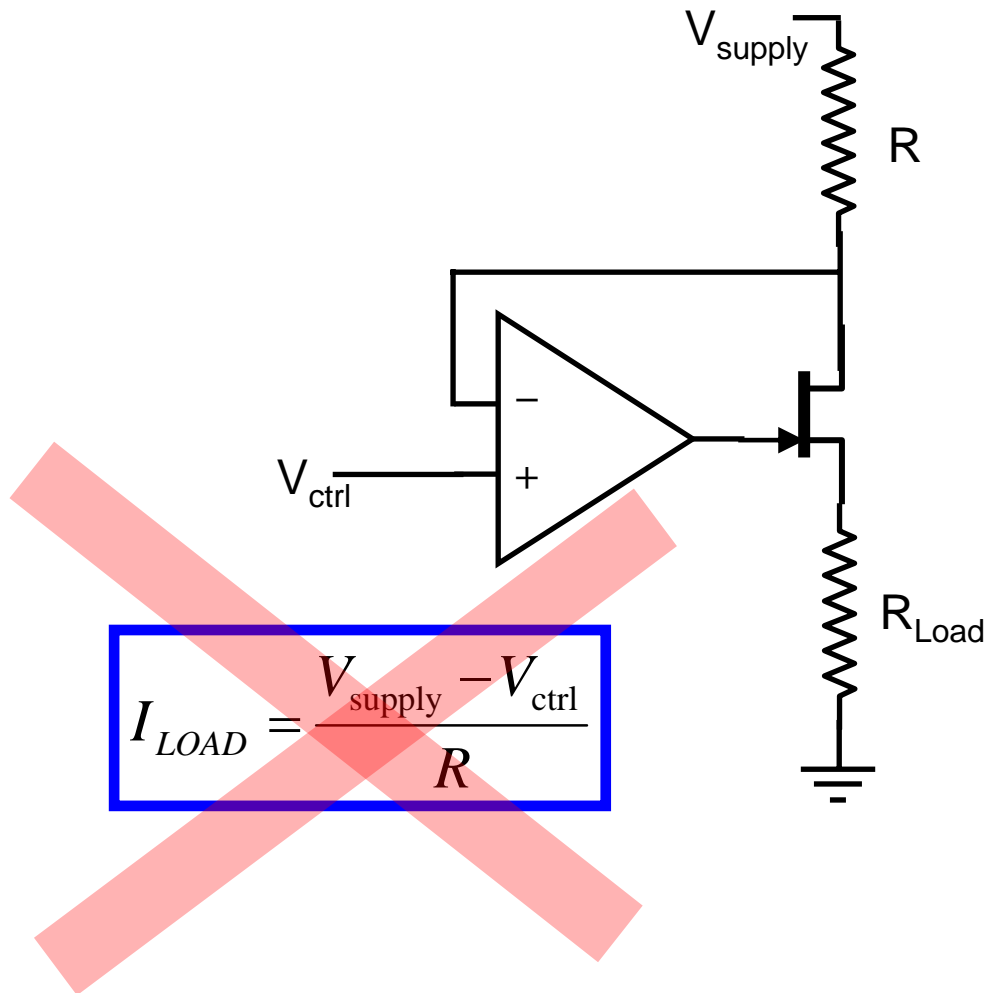Why doesn't this circuit work? (as a constant current source)



Photodiodes and Op-amps


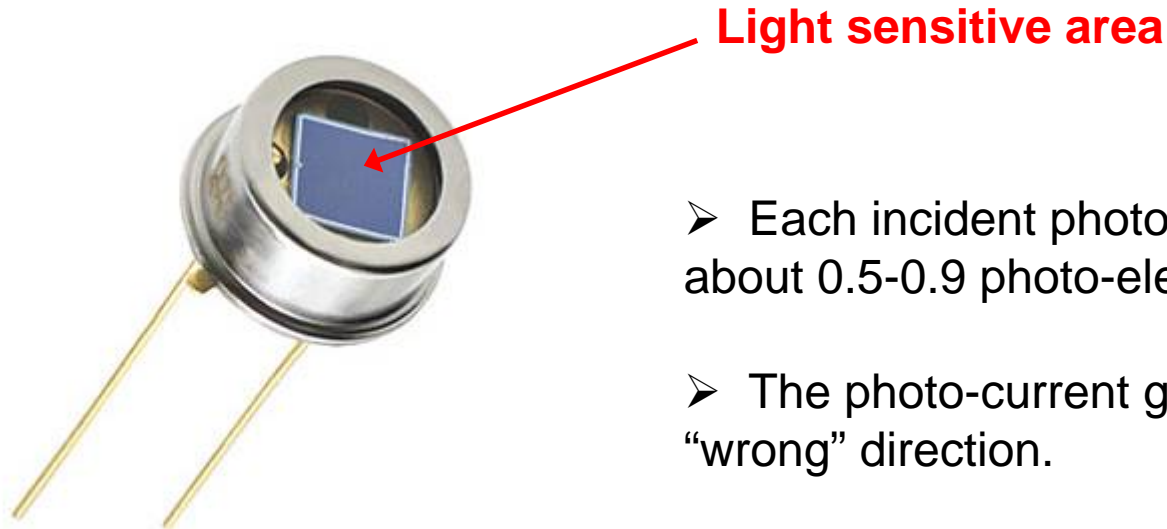


FDS100 photodiode

[Image from www.thorlabs.com]

➤ Each incident photon will produce about 0.5-0.9 photo-electrons.

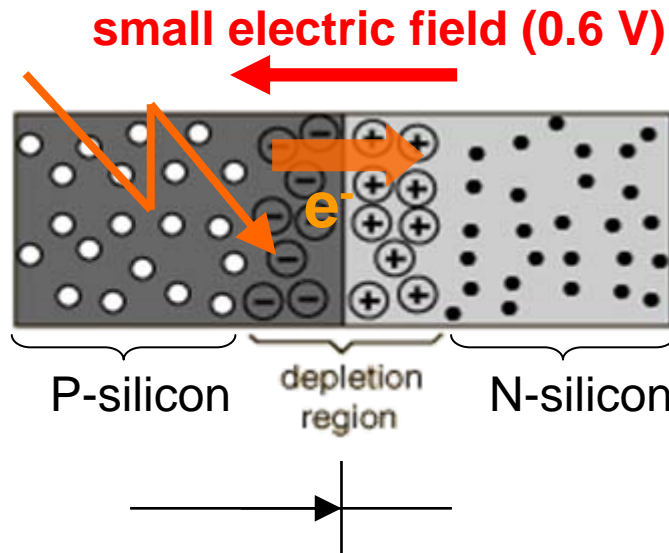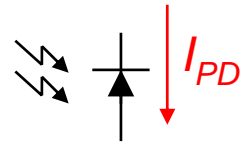➤ The photo-current goes in the "wrong" direction.





- electron
- hole
- ⊖ negative ion from filled hole
- ⊕ positive ion from removed electron

Reverse-biasing Photodiodes

Why use reverse-biasing?

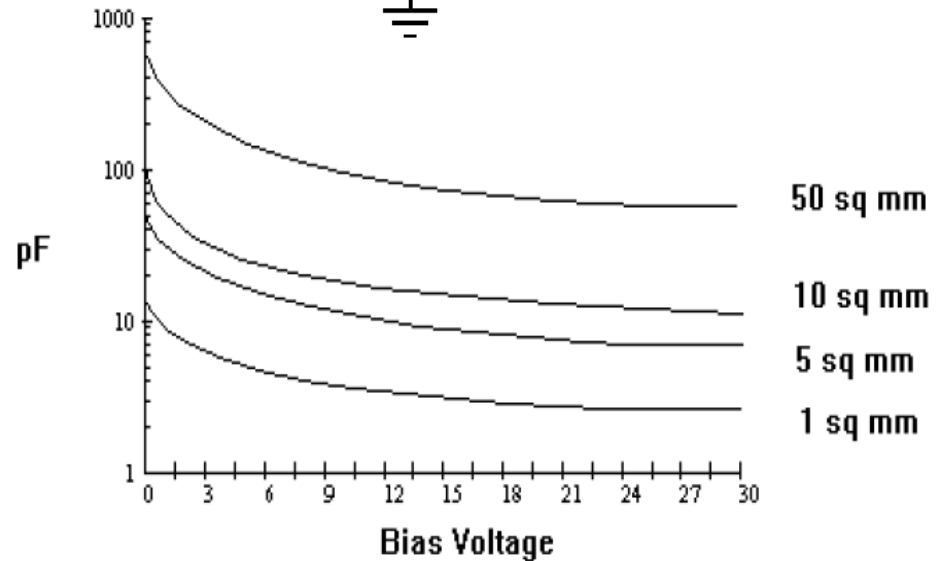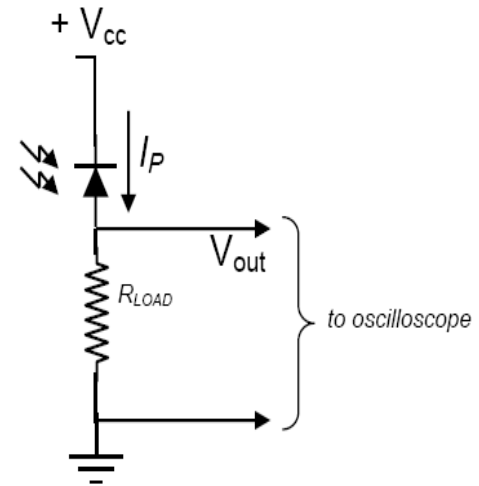- It reduces the PN junction **capacitance**.
- ➔ **Faster time response.**
- It improves the **linearity** of the photo-current (i.e. photo-electrons per photon) at higher illumination.



[figure from www.centrovision.com]

Drawback: *increased noise at ultra-low intensities.*