Midterm this Week

- ➢ Midterm in lab.
- ➤ Duration: 1 hour (2-3pm).
- Material on midterm: Everything from first 4 weeks of class.
 - Thévenin's Theorem & Source Impedance.
 - Impedance of resistors, capacitors, and inductors.
 - Filters (RC,RL,RLC,low-pass,high-pass, bandpass, notch, Chebyshev, Butterworth, etc ...).
 - Basic oscilloscope use, resistor code, etc...
- Midterm will cover design exercises and lab exercises.

> The purpose of the midterm is to consolidate passive analog linear circuitry before we move onto non-linear devices.



a non-linear circuit element

> 2-terminal quantum device



- > A diode only conducts in one direction !!!
- ➢ Non-linear → Ohm's Law doesn't apply !
 - \rightarrow There is no simple Z_{diode} formula !
 - → Thevenin's theorem doesn't apply !

> **Calculus:** you can linearize a function/system in the vicinity of some V_0 or I_0 .

→ Ohm's law, Z_{diode} , and Thevenin's theorem can only be used locally around some value of V₀ and I₀.

 \rightarrow i.e. you can still write down a differential equation for your circuit (i.e. Kirchhoff's loop and junction laws are still valid).

Intro to Semiconductors


- Semiconductors have a modest resistivity:
- Normally we think of electrons moving in a circuit
- In a semiconductor things are a little different
 - \rightarrow We think of either holes or electrons.
 - Holes (+ charge)
 - Electrons (- charge)

| Material | Resistivity |
|----------|-----------------------|
| Copper | 1.70x10-8 Ω.m |
| Silicon | 6400 Ω.m |
| Rubber | ~10 ¹³ Ω.m |




The PN junction

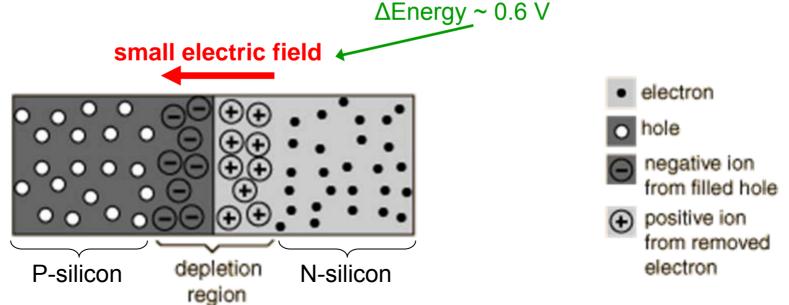
- Made from differently doped silicon
 - \rightarrow N region has more electrons
 - \rightarrow P region had more holes
- At the PN junction the holes & electrons recombine to form a small insulating depletion region.




How a diode works

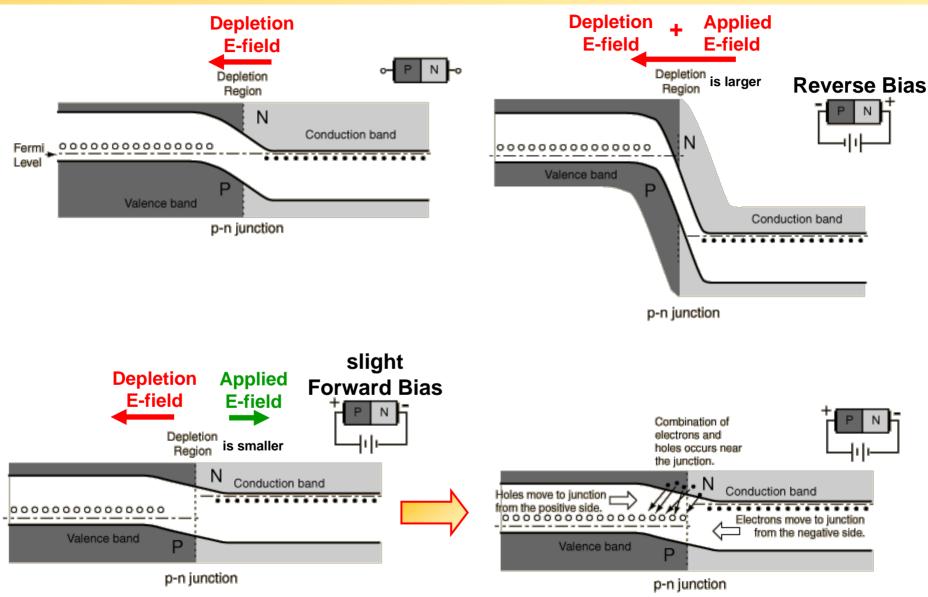

How a diode works

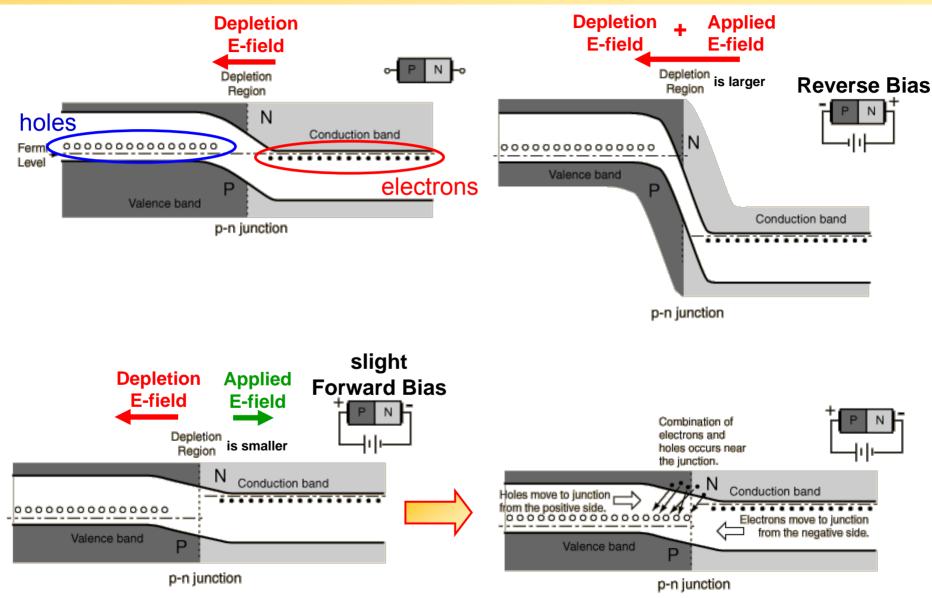

Diode: I-V characteristic curve I

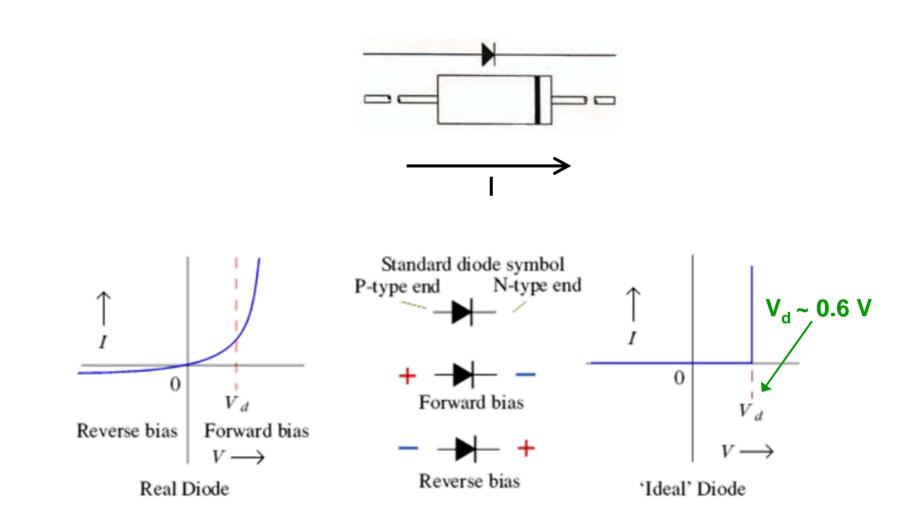


[image from www.mtmi.vu.lt]

Diode: I-V characteristic curve II


Simple model

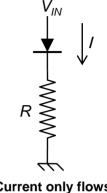- \rightarrow Current can only flow in one direction.
- \rightarrow A 0.6V "diode drop" when conducting.
- \rightarrow IR=V_{IN} 0.6 V
- \rightarrow Useful for designing circuits.



Current only flows in the direction of the arrow.

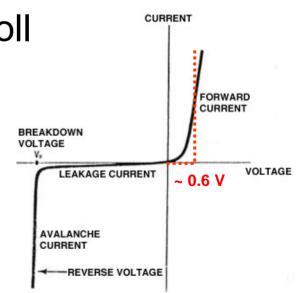- More complete model: Ebers-Moll equation.
 - \rightarrow Not so useful for designing circuits.
- A little negative is OK
 A lot is "bad" → smoke!!!!





Thermal Characteristics

| Symbol Parameter | | Max. | Units |
|------------------|-----------------------------------------|-------------------------------|-------|
| Symbol Parameter | Farameter | 1N/FDLL 914/A/B / 4148 / 4448 | Units |
| PD | Power Dissipation | 500 | mW |
| R _{SJA} | Thermal Resistance, Junction to Ambient | 300 | *C/W |


1

@2007 Fairchild Semiconductor Corporation 1N/FDLL 914/A/B / 916/A/B / 4148 / 4448 Rev. B2

| Symbol | Parameter | Test Conditions | Min. | Max. | Units |
|---------------------------|----------------------------------------------------------------------------------------------------|-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|----------------------------|----------------------------------------|-------------------------|
| / _R | Breakdown Voltage | I _R = 100μA I _R = 5.0μA | 100 75 | | v v |
| VF | Forward Voltage 1N9145/4448 1N9165 1N914916/64148 1N914916A 1N9148/4448 1N9148/4448 | $l_F = 5.0mA$ $l_F = 5.0mA$ $l_F = 10mA$ $l_F = 20mA$ $l_F = 20mA$ | 620 630 | 720 730 1.0 1.0 1.0 1.0 | mV mV V V V |
| R | Reverse Leakage | V _R = 20V V _R = 20V, T _A = 150°C V _R = 75V | | 25 50 5.0 | nA μA μA |
| ۲ | Total Capacitance 1N916A/B/4448 1N914A/B/4148 | V _R = 0, f = 1.0MHz V _R = 0, f = 1.0MHz | | 2.0 4.0 | pF pF |
| t _{er} | Reverse Recovery Time | I _F = 10mA, V _R = 6.0V (600mA) I _m = 1.0mA, R _L = 100Ω | | 4.0 | ns |
| Severse Voltage | 2 3 6 10 20 33 50 100 Reverse Current, L. [UA] | | 20 Tee Voltage, V, | | |
| Figu | re 1. Reverse Voltage vs Reverse Current BV - 1.0 to 100µA | entetbal, Ruit: The file could for which the Figure 2. Reverse (IR - | Current vs R 10 to 100V | h Terpentare everse Volt | ° age |
| Forward Voltage, V , [mV] | | 750 Transition of the second s | | | |
| | Forward Current, I, [uA] | FORM | rd Current, I, () | maj | |

2

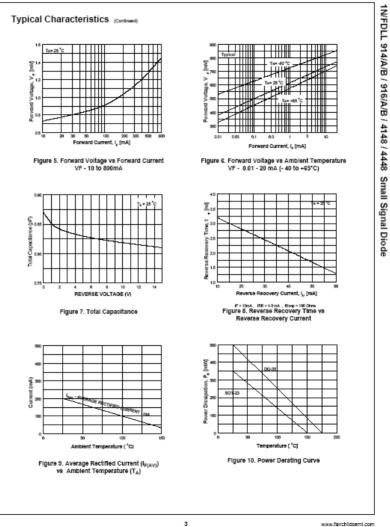1N/FDLL 914/A/B / 916/A/B / 4148 / 4448 Rev. B2



1N/FDLL 914/A/B / 916/A/B / 4148 / 4448 Rev. B2

www.fairchildsemi.com

FAIRCHILD MOONDLOTO

FAIRCHILD SEMICONDUCTOR TRADEMARKS

| ActiveArray™ Bottomiess™ | | | SILENT SWITCHER® | UnIFET™ |
|-----------------------------|--------------------------------|--------------------------|-----------------------|------------------|
| Bottomiess™ | GlobalOptolsolator™ | OCXPro™ | SMART START™ | VCX [™] |
| | GTO™ . | OPTOLOGIC [®] | SPM™ | Wire ** |
| Bulld It Now™ | HISeC** | OPTOPLANAR [™] | Stealth ** | |
| CoolFET [™] | I ² C™ | PACMAN [™] | SuperFET** | |
| CROSSVOLT [™] | I-Lo** | POP ** | SuperSOT™-3 | |
| DOME ** | ImpliedDisconnect [™] | Power247 ** | SuperSOT™-6 | |
| EcoSPARK [™] | IntellIMAX [™] | PowerEdge** | SuperSOT™-8 | |
| E ² CMOS™ | ISOPLANAR [™] | PowerSaver [®] | SyncFET [™] | |
| EnSigna™ | LittleFET [™] | PowerTrench [®] | TCM [™] | |
| FACT® | MICROCOUPLER [™] | QFET [®] | TinyBoost** | |
| FAST® | MICROFET ** | QS™ | TinyBuck™ | |
| FASTr™ | MicroPak [™] | QT Optoelectronics™ | TinyPWM ^{**} | |
| FPS™ | MICROWIRE [™] | Quiet Series™ | TinyPower** | |
| FRFET" | MSX™ | RapidConfigure** | TinyLogic® | |
| | MSXPro** | RapidConnect™ | TINYOPTO** | |
| Across the board. Aro | und the world.** | µSerDes™ | TruTranslation** | |

DISCLAIMER

FAIRCHILD SEMICONDUCTOR RESERVES THE RIGHT TO MAKE CHANGES WITHOUT FURTHER NOTICE TO ANY PRODUCTS HEREIN TO INFROME RELIVELITY, FUNCTION CROBENTES INFERIORIL DIARDE DUCT ASSUME ANY LIABILITY ANSING OUT OF THE APPLICATION OR USE OF ANY PRODUCT OR CIRCUIT DESCRIBED HEREINNETHER DOES IT CONVEY ANY LICENSE UNDER THE APPLICATION OR USE RIGHTS OF OTHERS. THESE SECONDENDE DO TOT EXAMOL THE TERMS OF PARCHLD'S WORLDWIDE TERMS AND CONDITIONS, SPE-CIFICALLY THE WARRANTY THEREIN, WHICH COVERS THESE PRODUCTS.

LIFE SUPPORT POLICY

FAIRCHILD'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF FAIRCHILD SEMICONDUCTOR CORPORATION.

whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

As used herein:

1. Life support devices or systems are devices or systems which, (a) are 2. Acritical component is any component of a life support device or system Intended for surgical implant into the body, or (b) support or sustain life, or (c) whose failure to perform when property used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in significant injury to the user.

PRODUCT STATUS DEFINITIONS

Definition of Terms

| Product Status | Definition |
|------------------------|----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| Formative or in Design | This datasheet contains the design specifications for product development. Specifications may change in any manner without notice. |
| First Production | This datasheet contains preliminary data, and supprementary data will be published at a later date. Farchild Semiconductor reserves the right to make changes at any time without notice in order to improve design. |
| Full Production | This datasheet contains final specifications. Fairchlid Semiconductor reserves the right to make changes at any time without notice in order to improve design. |
| Not in Production | This datasheet contains specifications on a product that has been discontinued by Fairchild semiconductor. The datasheet is printed for reference information only. |
| | Formative or in Design First Production Full Production |

4

1N/FDLL 914/A/B / 916/A/B / 4148 / 4448

Small

l Signal

Diode

Applications

- Circuit Protection
- Rectification
 - → half wave rectifier
 - \rightarrow full wave rectifier
 - \rightarrow Power Supplies
- ➢ Frequency manipulation
 → Frequency multiplier
 → Mixers

Fourier Transform (FFT) of Full Wave Rectifier

Fourier space representation of rectified output

