

# MidTerm Results and Overall Performance

## Midterm:

Average: 69%.

High Score: 94%.

**Lab Books:** The lab books have been improving ... mostly (write down as much as you can).

→ You should expect to do more analysis at home after the lab.

**Lab Report:** Quality has been decreasing ... mostly. You need to invest more care and effort into your lab reports.

# Transistors II: AC transistor Amplifiers

## Emitter-Follower Amplifier Summary

### Pros:

- Power/Current Gain.  
→ Speaker got louder.
- Simple.
- Moderate input impedance.
- Does not depend on  $\beta$ .

### Cons:



- Requires a DC bias.  
→ Signal cannot be negative !  
→ Signal must be larger than 0.6 V.
- Cannot provide **Voltage Gain**.
- Significant power consumption.

# The DC bias problem


There are 2 simple solution to the DC bias problem:

- ***Push-Pull*** amplifier.
- **AC-coupled biased-amplifier**



# Push-Pull BJT Amplifier (I)

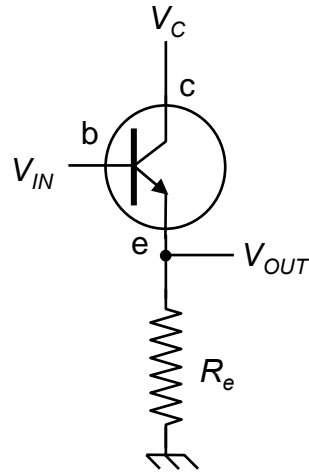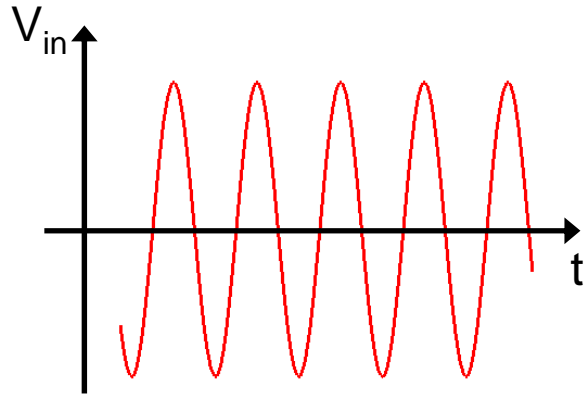




NPN Emitter Follower

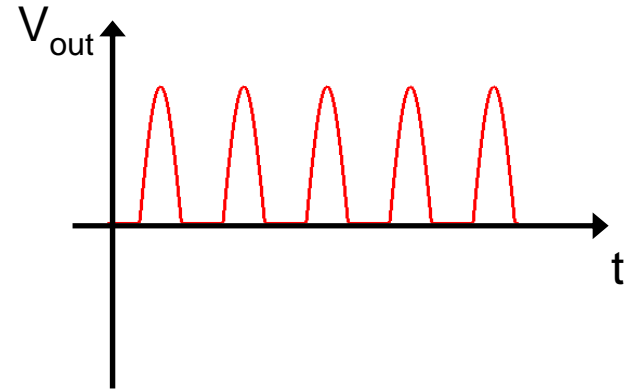


# Push-Pull BJT Amplifier (I)

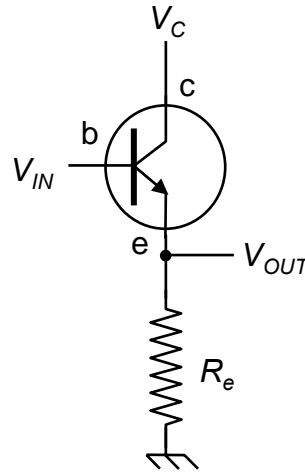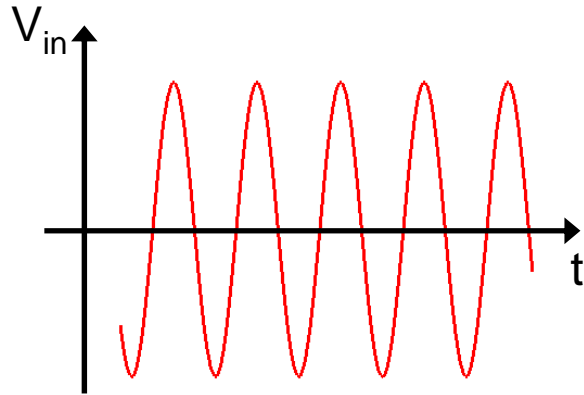

NPN Emitter Follower

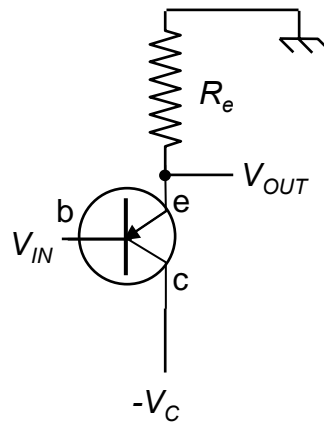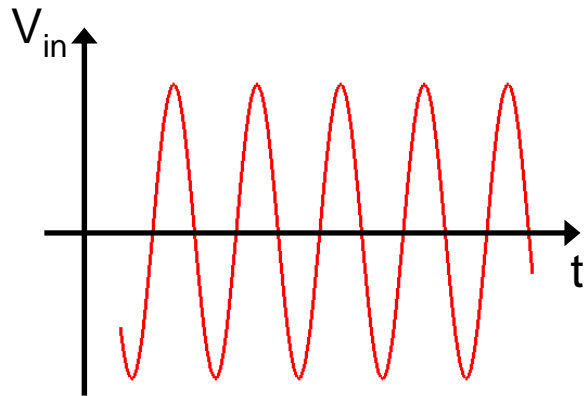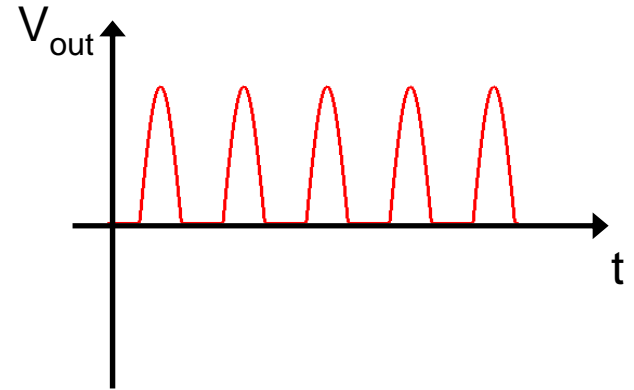


PNP Emitter Follower

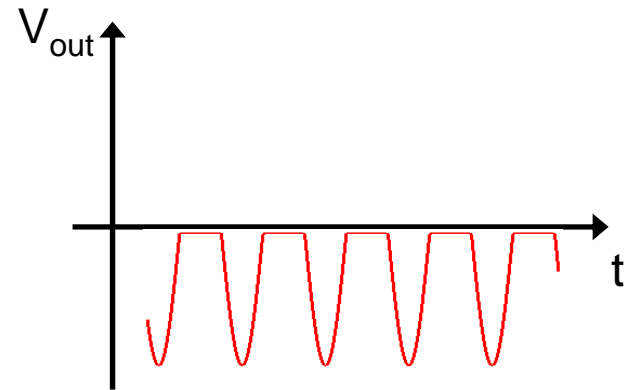

# Push-Pull BJT Amplifier (II)


Combine both circuits:

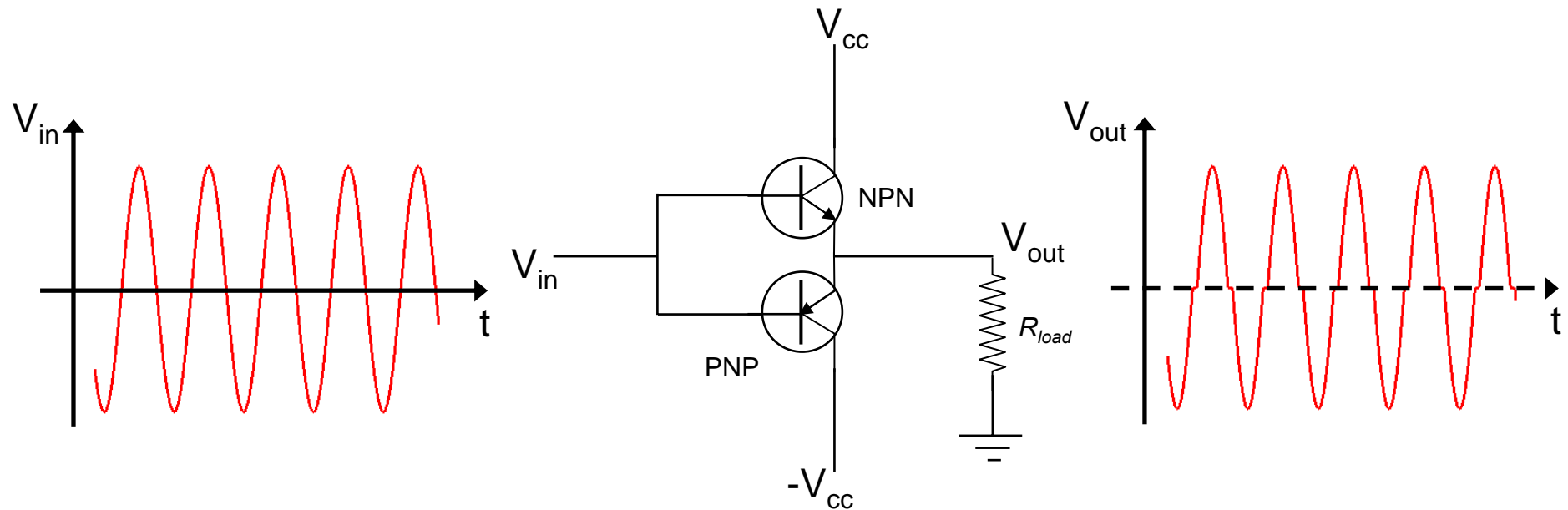

Push-Pull BJT Amplifier  
No DC bias required

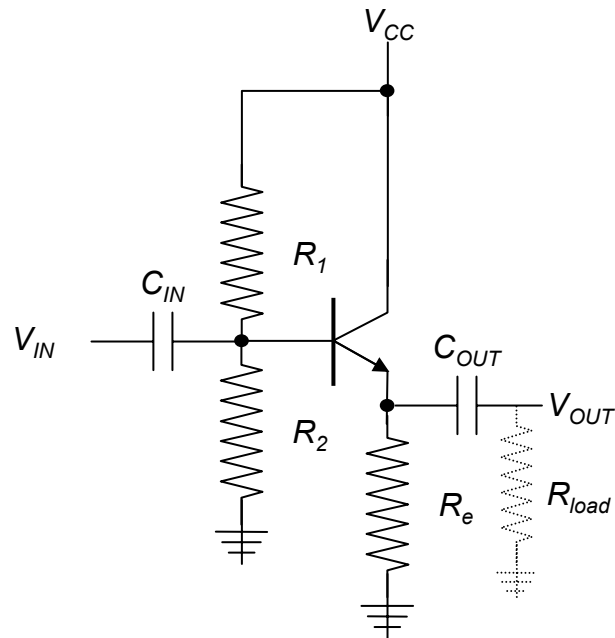
# AC-coupled Biased-Amplifier

- AC-couple the input and output signals with capacitors (i.e. high-pass RC filters)
- DC-bias the input with a voltage divider.


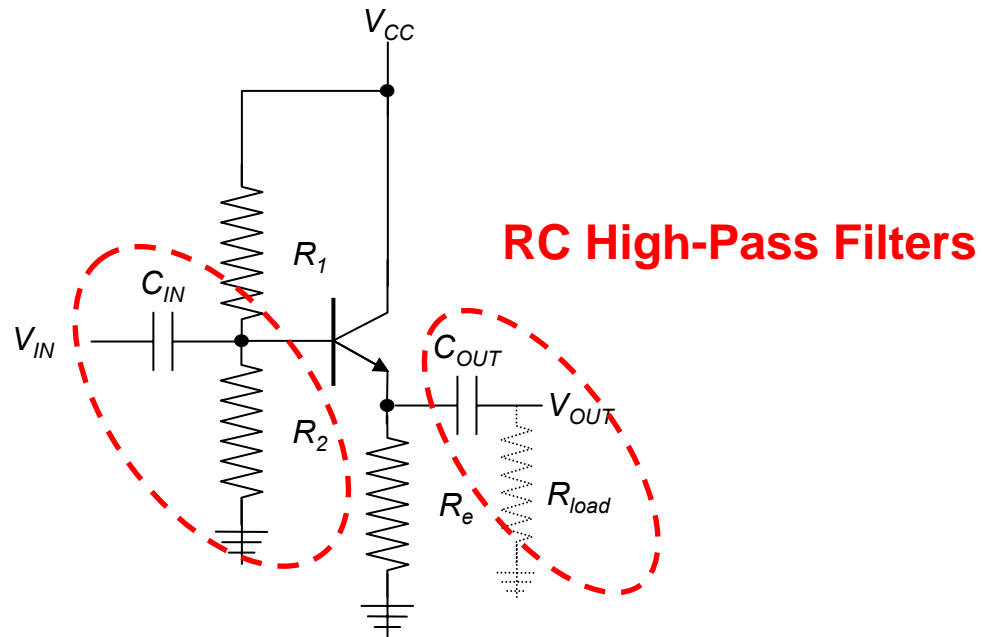
# AC-coupled Biased-Amplifier


- AC-couple the input and output signals with capacitors (i.e. high-pass RC filters)
- DC-bias the input with a voltage divider.




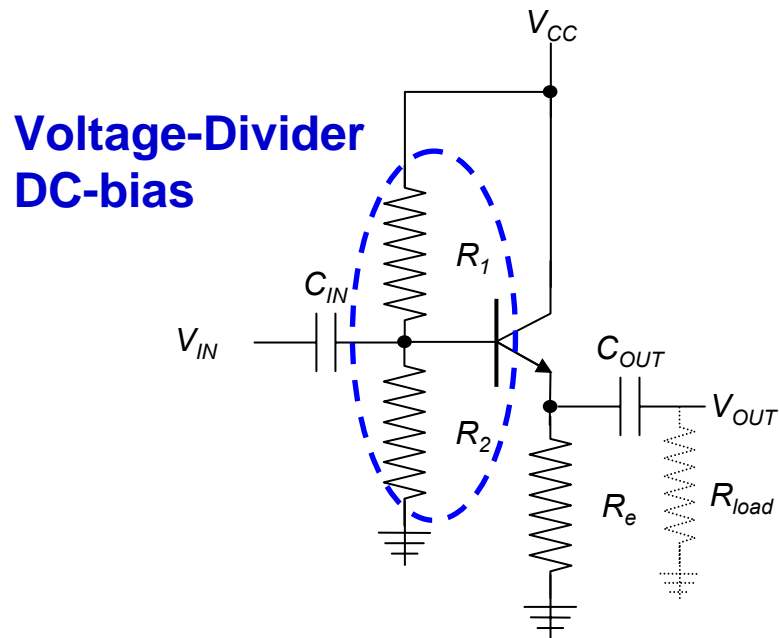
# AC-coupled Biased-Amplifier

- AC-couple the input and output signals with capacitors (i.e. high-pass RC filters)
- DC-bias the input with a voltage divider.



# AC Transistor Amplifier Design

## 4 rules:

- Choose a **quiescent collector current** (no load current) which is at least 10x larger than load current.
- Choose  $V_{out, DC}$  in the middle of the supply voltage range for maximum signal voltage amplitude.
- Choose the DC-bias such that  $V_{collector} > V_{base}$  (NPN) to avoid saturation, and  $V_{base} \sim V_{emitter} + 0.6$ .
- Make sure that the voltage divider DC-bias and the transistor don't load each other (i.e.  $I_{base}$  10x smaller than  $I_{voltage-divider}$ ).