
 


 
# Transistors III: FETs

- 3-terminal device like a BJT
- New names for the connections
  - **Drain** (input) ... sort of like collector
  - **Source** (output) ... sort of like emitter
  - **Gate** (controls flow) ... sort of like base
- 2 broad types
  - Junction FETs (JFETs)
  - Metal-oxide-semiconductor (MOSFETs)


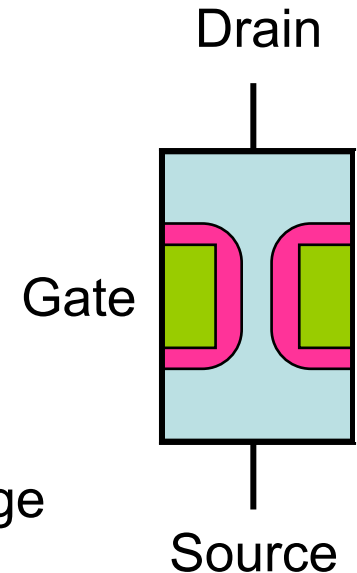
# Principle of Operation

- Made from a conducting piece of silicon
  - This is called the **channel**
  - **Drain** on one end
  - **Source** on the other
  - In the middle a **gate** is embedded
- Current regulation
  - If the gate is at a negative voltage there is a charge **depletion zone** around the gate
    - Current cannot flow in this zone
    - Expands as the gate becomes more negative
  - Controls the conductivity of the channel
- At a **pinch off voltage** the current stops ( $V_p$ )
  - Think of pinching a hose to cut off the flow of water



# JFETs vs. MOSFETs

- JFET gate forms a diode junction with the channel. Input impedance  $\sim 10^{12} \Omega$ .
- MOSFET has a insulating layer for better input impedance (up to  $10^{14}\Omega$ ).
- MOSFETs have an extra terminal called the **body**.
  - Usually just connected to the source to remove charge.
- MOSFETs are generally used for power circuits and digital circuits.
- Many other types now available.

# FETs vs. BJTs

## FET Pros


- The gate of a FET draws almost no current (i.e. pA range).
- FETs have almost infinite input impedance.
- Can frequently make a better amplifier circuit with a FET.
- Can operate bi-directionally sometimes.

## FET cons

- FETs are more complicated than BJTs
  - complicated operational model.
- FET have even larger parameter spreads than BJTs.
 
# FET properties

- Can be a n-channel or a p-channel
  - **N-channel** like *npn*
  - **P-channel** like *pnp*
- Gate may be centered on some diagrams
  - Have to figure out it which is which from “context”
  - Source & Drain are nearly identical
  - Can be used backwards with almost same performance
- **N-channel usually faster** than **P-channel** due to higher mobility of electrons vs holes moving in the channel.



n-channel JFET (left)  
p-channel JFET (right)

# Gate Voltage Rules

$V_p$  = pinch-off voltage: this is an intrinsic parameter of the JFET.

➤  $V_{GS} < V_p$   
→  $I_D = 0$


➤ For  $V_{GS} > 0.6$  V  
→ **Device Fails!!!**

→ Try to keep  $V_{GS} < 0$

➤  **$V_p < V_{GS} < 0.6$  V**

→  $I_D$  depends on both  $V_{GS}$  &  $V_{DS}$

 → A complete description would require a  
2D function:  $I_D(V_{GS}, V_{DS})$



# Linear and Saturation Regions


Linear Region :  $V_{DS} < V_{GS} - V_P$

$$\rightarrow I_D = k [ 2(V_{GS} - V_P)V_{DS} - V_{DS}^2 ]$$



Saturation Region :  $V_{DS} > V_{GS} - V_P$

$$\rightarrow I_D = k (V_{GS} - V_P)^2$$

 - $V_p$  is the **pinch-off** voltage
  - It's negative for n-channel.
  - Voltage where conductance stops
  - **Huge** manufacturing spread
- $k$  is a constant
  - Depends on the physical size of the channel (length/width)
  - Depends on the manufacturing details



# Ideal Performance vs. Reality

 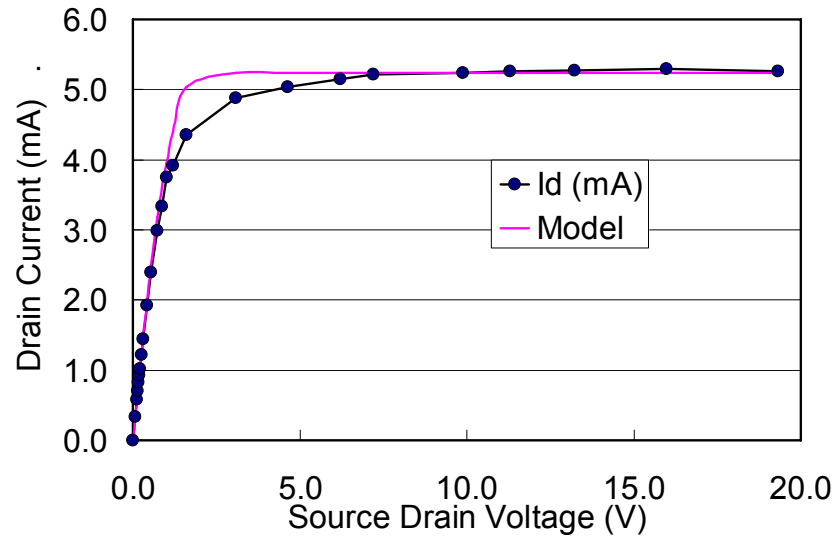



# 2N3958

## Vishay Siliconix




### SPECIFICATIONS ( $T_A = 25^\circ\text{C}$ UNLESS OTHERWISE NOTED)

Parameter	Symbol	Test Conditions	Limits			Unit
			Min	Typ <sup>a</sup>	Max	
<b>Static</b>						
Gate-Source Breakdown Voltage	$V_{(BR)GSS}$	$I_G = -1\ \mu\text{A}, V_{DS} = 0\ \text{V}$	-50	-57		V
Gate-Source Cutoff Voltage	$V_{GS(off)}$	$V_{DS} = 20\ \text{V}, I_D = 1\ \text{nA}$	-1.0	-2	-4.5	
Saturation Drain Current <sup>b</sup>	$I_{DSS}$	$V_{DS} = 20\ \text{V}, V_{GS} = 0\ \text{V}$	0.5	3	5	mA
Gate Reverse Current	$I_{GSS}$	$V_{GS} = -30\ \text{V}, V_{DS} = 0\ \text{V}$ $T_A = 150^\circ\text{C}$		-10	-100	pA
				-20	-500	nA
Gate Operating Current	$I_G$	$V_{DG} = 20\ \text{V}, I_D = 200\ \mu\text{A}$ $T_A = 125^\circ\text{C}$		-5	-50	pA
				-0.8	-250	nA
Gate-Source Voltage	$V_{GS}$	$V_{DG} = 20\ \text{V}, I_D = 200\ \mu\text{A}$ $I_D = 50\ \mu\text{A}$	-0.5	-1.5	-4	V
					-4.2	
Gate-Source Forward Voltage	$V_{GS(F)}$	$I_G = 1\ \text{mA}, V_{DS} = 0\ \text{V}$			2	
<b>Dynamic</b>						
Common-Source Forward Transconductance	$g_{fs}$	$V_{DS} = 20\ \text{V}, V_{GS} = 0\ \text{V}$ $f = 1\ \text{kHz}$	1	2.5	3	mS
Common-Source Output Conductance	$g_{os}$				2	35

$V_P$



# Solving for the current graphically

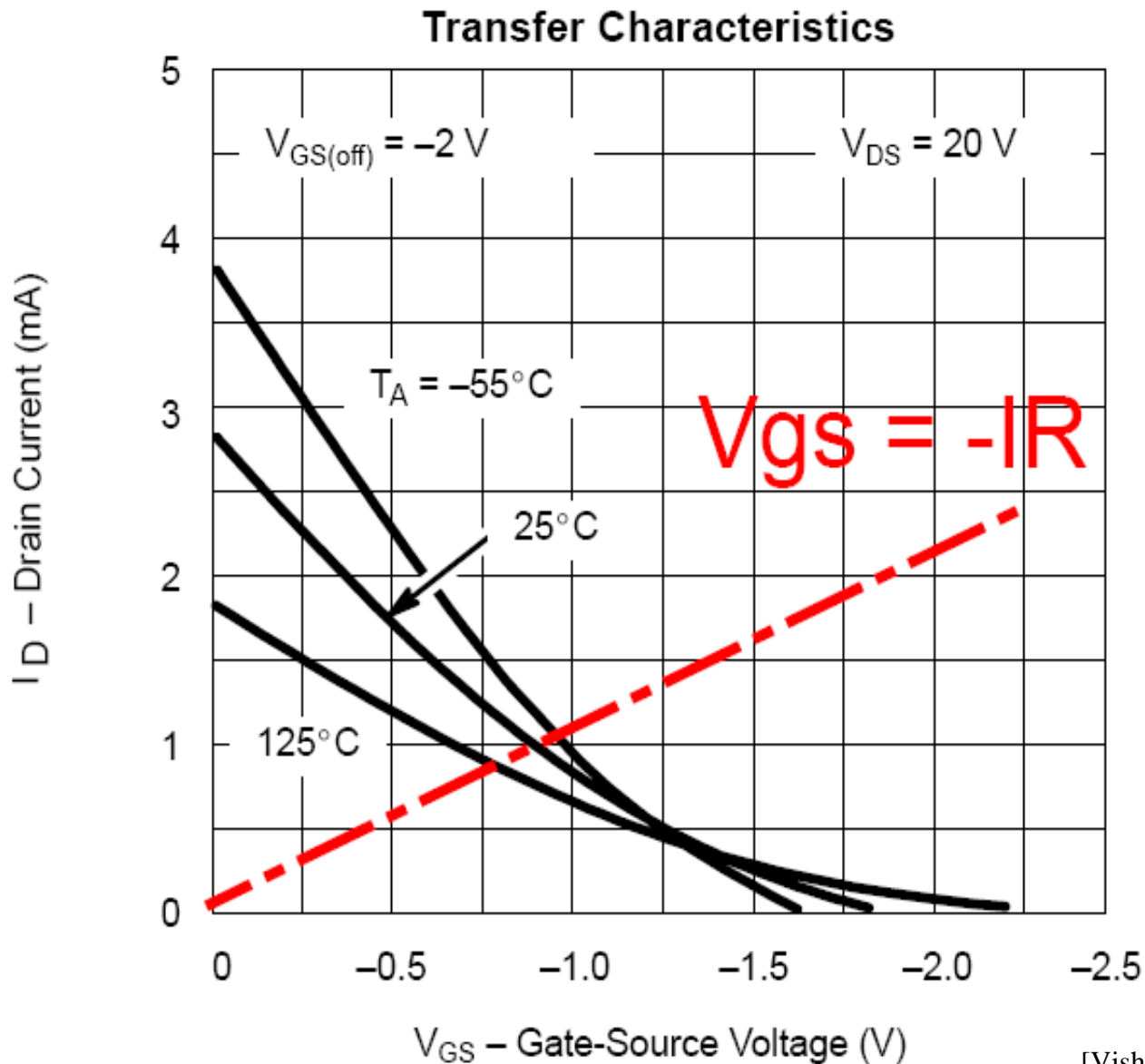

# Transconductance in the Saturation Region

- There is a quiescent current given by  $I_D$ .
- Use lower case symbols to represent small changes around the quiescent values
- **Transconductance:**  $g_m = i_d/v_{gs}$ 
  - Just the slope of  $I_D$  vs  $V_{GS}$  in the saturated region.
  - Depends on  $I_D$ .
- Smaller variation for  $V_{GS} < 0$  V.
- Units:  $\Omega^{-1}$ =mho (pronounced “Moe”)
  - $\mu$ mho or umho for  $10^{-6}$  mho.
  - mmho for  $10^{-3}$  mho.
  - Sometimes see  $\bar{U}$

