

Flip-Flops

Outline:

1. *Timing noise*
 - Signal races, glitches
 - FPGA example (“assign” → bad)
2. *Synchronous circuits and memory*
 - Logic gate example
3. *Flip-Flop memory*
 - RS-latch example
4. *D and JK flip-flops*
 - Flip-flops in FPGAs
5. *Synchronous circuit design with FPGAs*
 - FPGA example (“always” → good).
 - Parallel circuit design with FPGAs.

Timing noise

Amplitude Noise

A digital circuit is very immune to amplitude noise, since it can only have two values (Low or High, True or False, 0 or 1). Digital electronics circuits typically have error rates smaller than 1 part in 10^9 .

Timing Noise



Just like an analog circuit, a digital circuit can experience timing noise. Fortunately, good clocks are cheap and easily available, and a good design will eliminate the effects of timing noise.

If attention is not paid to timing issues can easily produce amplitude noise (bit errors).

Signal Race

The timing delays produced by wires and logic gates can produce unwanted (illogical) outputs.



Example: 3-input NAND gate

  

Signal Race

The timing delays produced by wires and logic gates can produce unwanted (illogical) outputs.



Example: 3-input NAND gate

  


Signal Race

The timing delays produced by wires and logic gates can produce unwanted (illogical) outputs.

Example: 3-input NAND gate

  


Signal Race with Glitch

 

[diagram courtesy of Altera Inc.]

XOR


A	B	Y
L	L	L
L	H	H
H	L	H
H	H	L

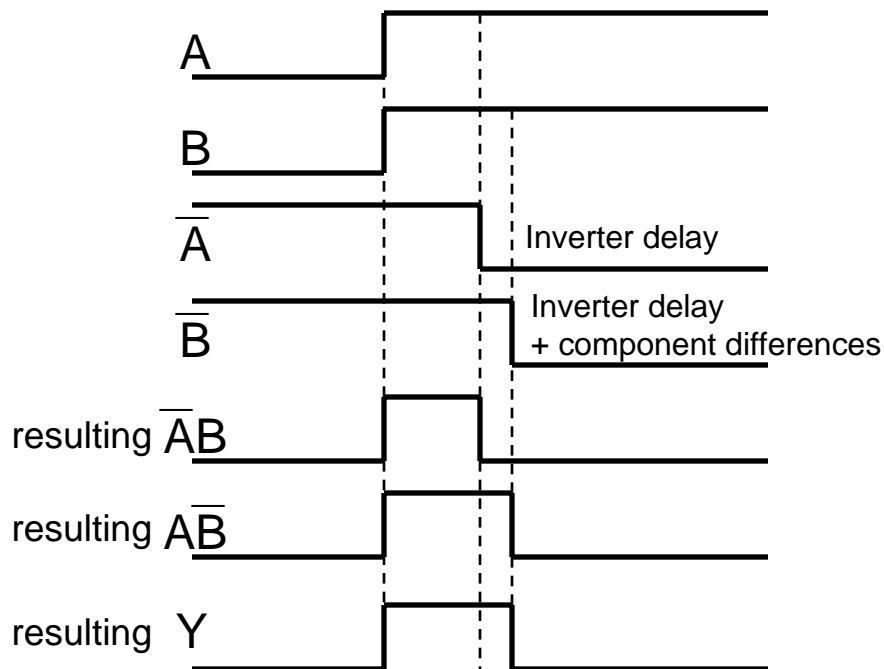

Time →

[Figure adapted from *Principles of Electronics: Analog & Digital* by L. R. Fortney]


Signal Race with Glitch

 

[diagram courtesy of Altera Inc.]

XOR

A	B	Y
L	L	L
L	H	H
H	L	H
H	H	L

 


Time →

[Figure adapted from *Principles of Electronics: Analog & Digital* by L. R. Fortney]

Glitches with FPGAs

Quartus II will simulate glitches
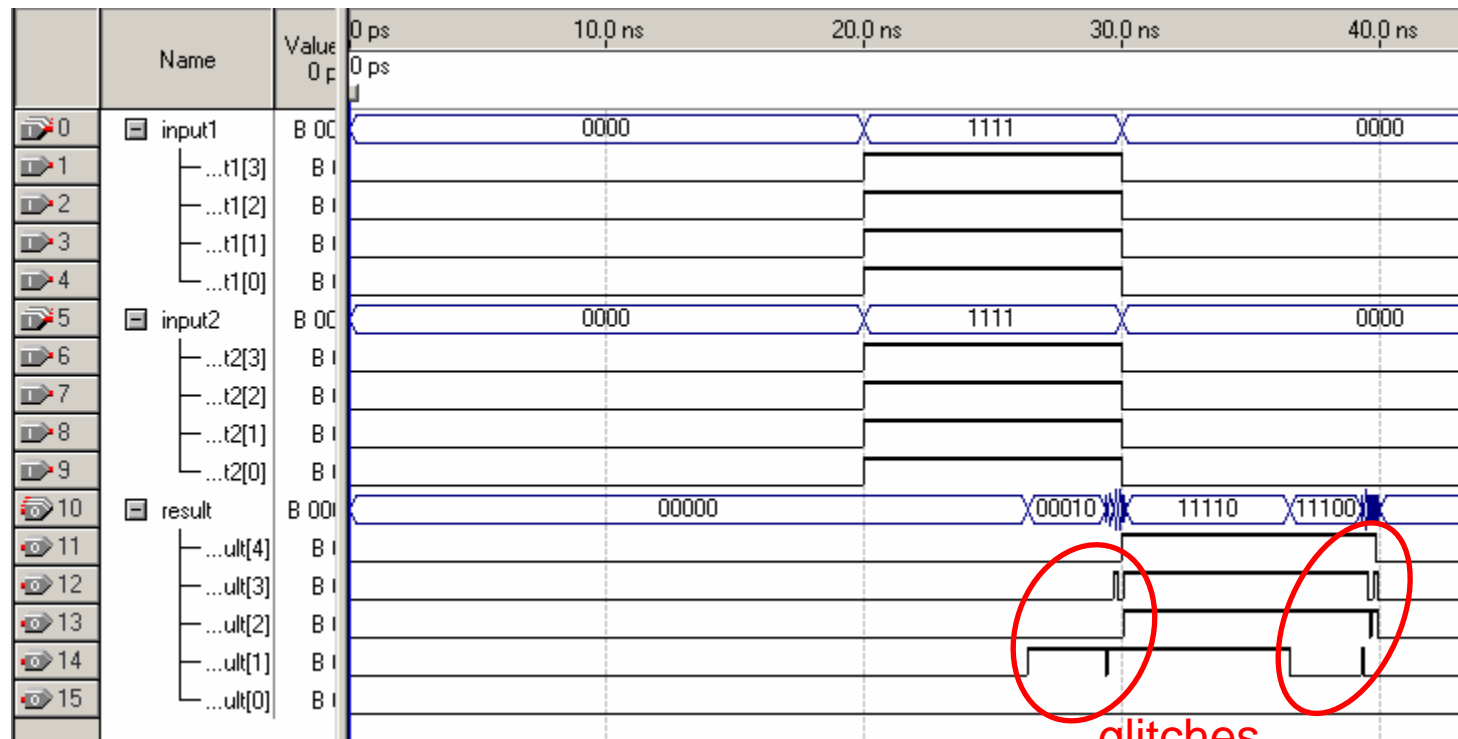
```
1 module adder_assign(input1, input2, result);
2     input [3:0] input1;
3     input [3:0] input2;
4     output [4:0] result;
5
6     assign result = input1 + input2;
7
8 endmodule
9
```



glitches

Asynchronous Design


Asynchronous design requires very careful attention to signal delays to avoid producing glitches and other spurious signals.

Glitches will produce false data and can produce very wrong results
e.g. a glitch on the most-significant-bit will produce a factor of 2 error.

Asynchronous design can produce very fast digital circuits, but is generally avoided due to more difficult design.

Synchronous Design

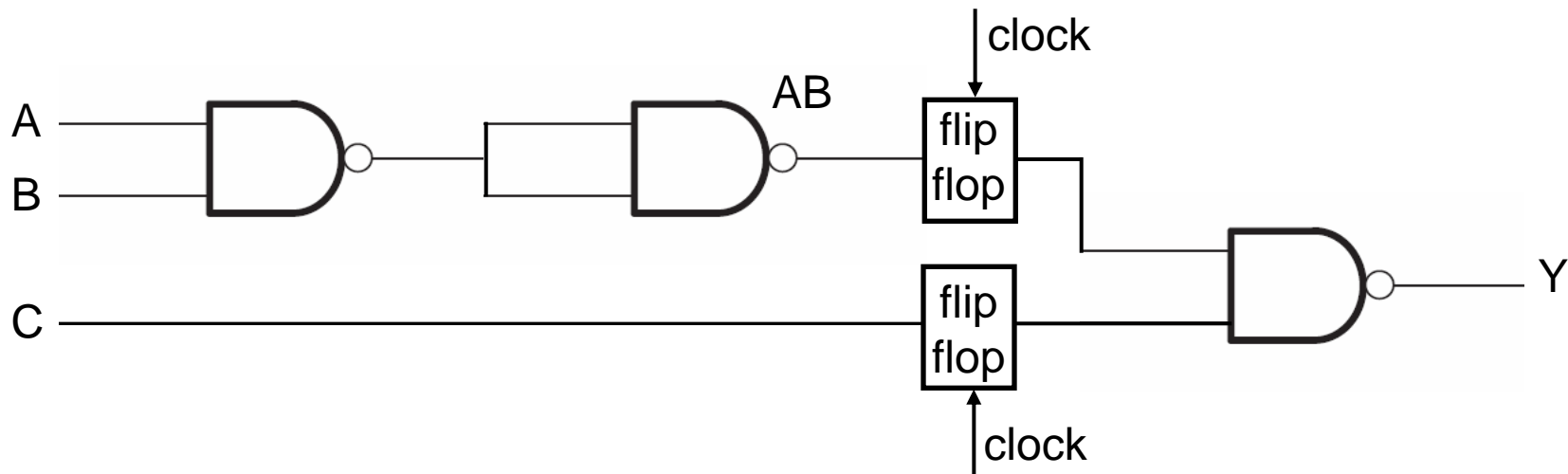The use of **memory** and a **clock** can eliminate signal races and glitches.




Basic flip-flop operation

The flip-flop will record and output the value at the input if the **clock** is HIGH. If the **clock** goes LOW, then the flip-flop does not change its value or output.



- Glitches are eliminated if
1. The clock HIGH and LOW times are longer than any gate delays.
 2. The inputs are synchronized to the clock.

Synchronous Timing

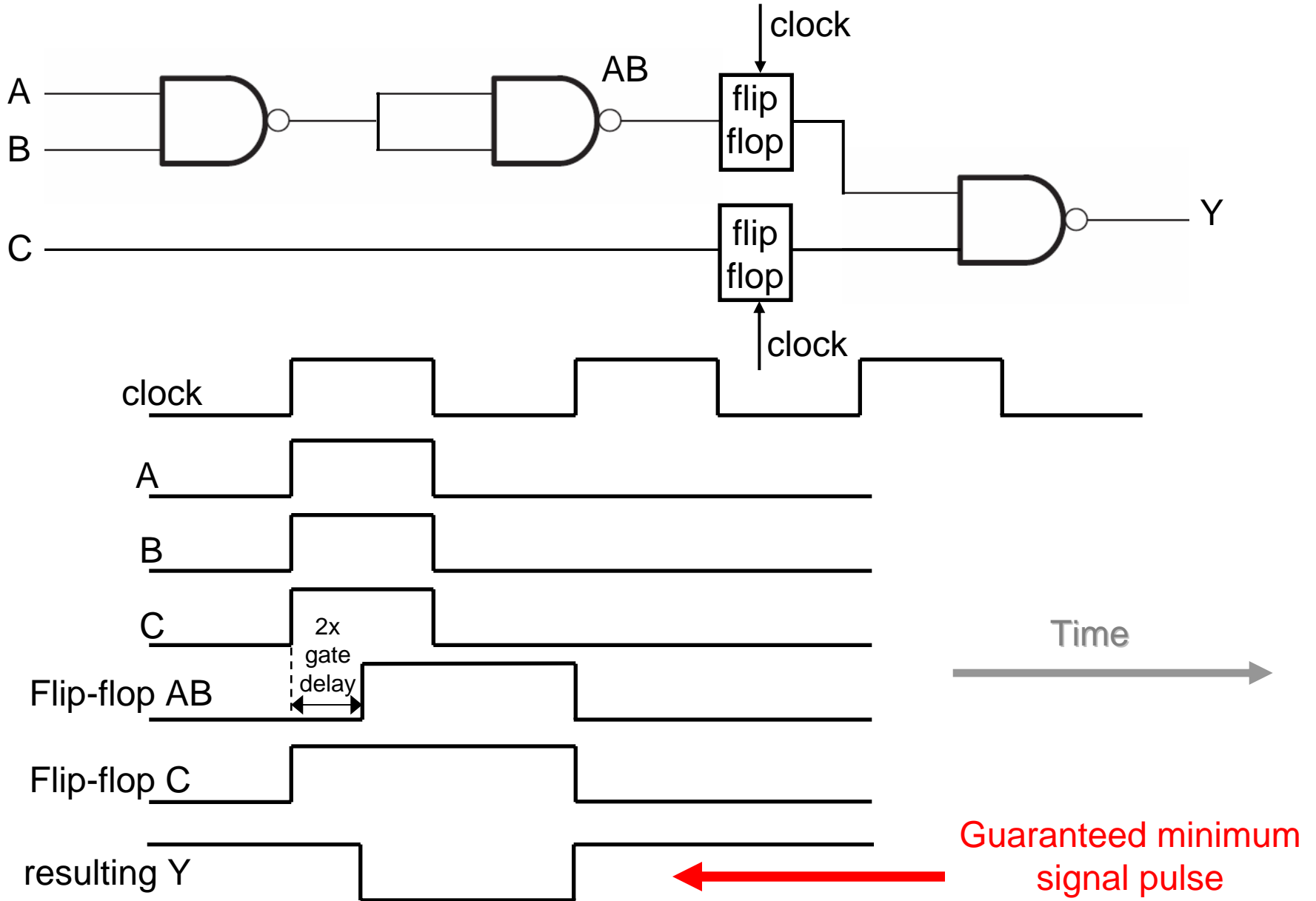

D-type Edge-Triggered Flip-Flop

  Generally, the flip-flop changes state on a clock signal “edge”, not the level. The flip-flop takes the value *just before* the clock “edge”.



For 74LS74: minimum $t_s = 20 \text{ ns}$
 minimum $t_h = 5 \text{ ns}$

FUNCTION TABLE



INPUTS				OUTPUTS	
$\overline{\text{PRE}}$	$\overline{\text{CLR}}$	CLK	D	Q	$\overline{\text{Q}}$
L	H	X	X	H	L
H	L	X	X	L	H
L	L	X	X	H [†]	H [†]
H	H	↑	H	H	L
H	H	↑	L	L	H
H	H	L	X	Q ₀	$\overline{\text{Q}}_0$

[Texas Instruments 74LS74 flip-flop datasheet]

Note: A flip-flop saves information (i.e. 1 bit); it does not modify it.

D-type Edge-Triggered Flip-Flop

  Generally, the flip-flop changes state on a clock signal “edge”, not the level. The flip-flop takes the value *just before* the clock “edge”.



For 74LS74: minimum $t_s = 20 \text{ ns}$
 minimum $t_h = 5 \text{ ns}$


FUNCTION TABLE

INPUTS				OUTPUTS	
$\overline{\text{PRE}}$	$\overline{\text{CLR}}$	CLK	D	Q	$\overline{\text{Q}}$
L	H	X	X	H	L
H	L	X	X	L	H
L	L	X	X	H [†]	H [†]
H	H	↑	H	H	L
H	H	↑	L	L	H
H	H	L	X	Q ₀	$\overline{\text{Q}}_0$

[Texas Instruments 74LS74 flip-flop datasheet]


Note: A flip-flop saves information (i.e. 1 bit); it does not modify it.

Synchronous Timing (revisited)

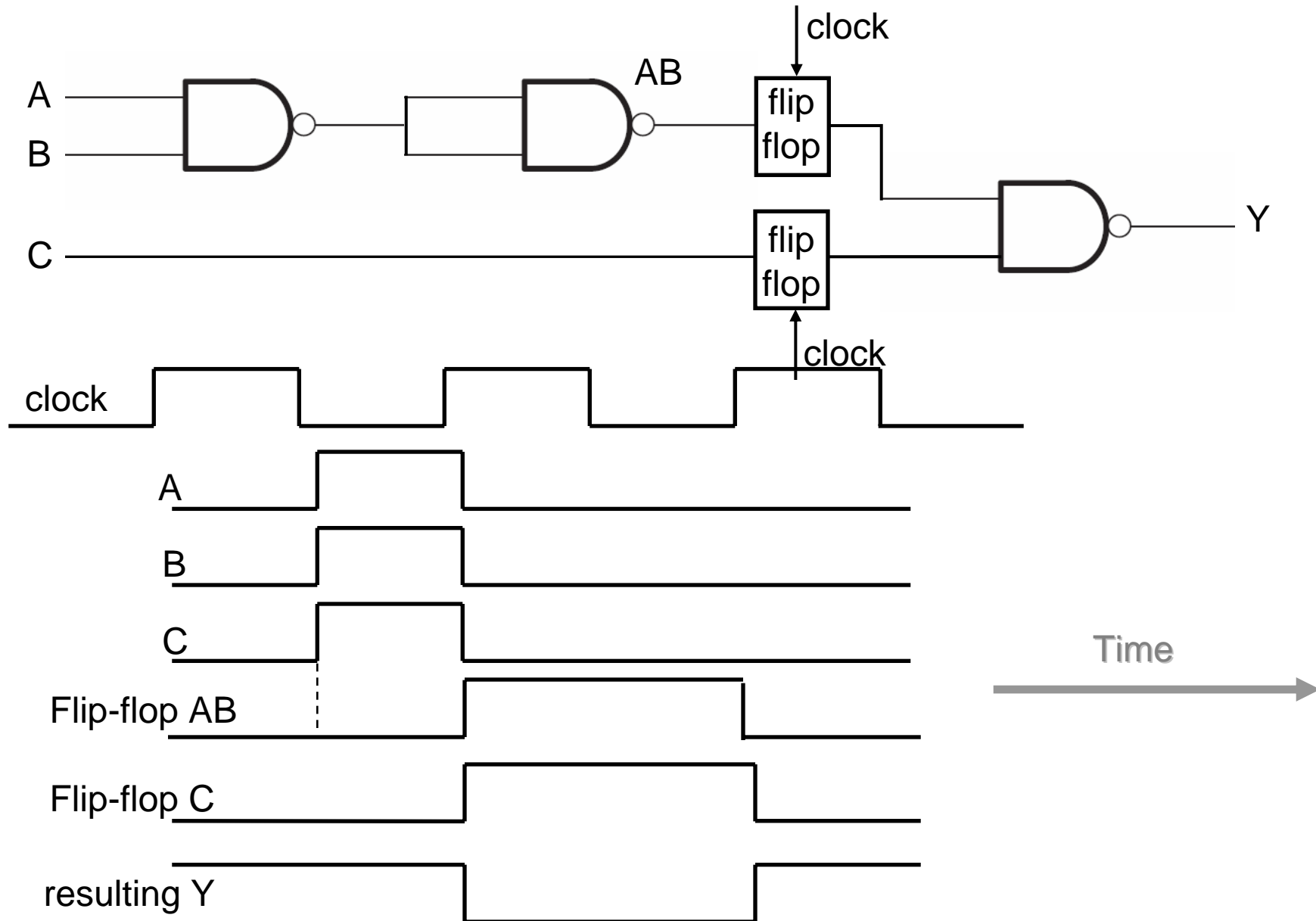

How does a flip-flop work?

Basic flip-flop: the SR latch

 

Logic table

\bar{S}	\bar{R}	Q	\bar{Q}
1	1	Q_0	\bar{Q}_0
0	1	1	0
1	0	0	1
0	0	1	1


Q_0 = value before
S&R changes

$\bar{R} = 0$ & $\bar{S} = 0$:

- $\bar{S} = 0$ & assume $\bar{Q} = 0 \rightarrow Q = 1$.
- $\bar{S} = 0$ & assume $\bar{Q} = 1 \rightarrow Q = 1$.
- $\bar{R} = 0$ & assume $Q = 0 \rightarrow \bar{Q} = 1$.
- $\bar{R} = 0$ & assume $Q = 1 \rightarrow \bar{Q} = 1$.

How does a flip-flop work?

Basic flip-flop: the SR latch

 

Logic table

\bar{S}	\bar{R}	Q	\bar{Q}
1	1	Q_0	\bar{Q}_0
0	1	1	0
1	0	0	1
0	0	1	1

Q_0 = value before
S&R changes

$\bar{R} = 0$ & $\bar{S} = 0$:

➤ $\bar{S} = 0$ & assume $\bar{Q} = 0 \rightarrow Q = 1$.

$\bar{S} = 0$ & assume $\bar{Q} = 1 \rightarrow Q = 1$.

➤ $\bar{R} = 0$ & assume $Q = 0 \rightarrow \bar{Q} = 1$.


$\bar{R} = 0$ & assume $Q = 1 \rightarrow \bar{Q} = 1$.

consistent

$\bar{R}=0$ & $\bar{S}=0 \rightarrow Q=1$ & $\bar{Q}=1$

How does a flip-flop work?

Basic flip-flop: the SR latch

 

Logic table

\bar{S}	\bar{R}	Q	\bar{Q}
1	1	Q_0	\bar{Q}_0
0	1	1	0
1	0	0	1
0	0	1	1


Q_0 = value before
S&R changes ✓

$\bar{R} = 0$ & $\bar{S} = 1$:

- $\bar{S} = 1$ & assume $\bar{Q} = 0 \rightarrow Q = 1$.
- $\bar{S} = 1$ & assume $\bar{Q} = 1 \rightarrow Q = 0$.
- $\bar{R} = 0$ & assume $Q = 0 \rightarrow \bar{Q} = 1$.
- $\bar{R} = 0$ & assume $Q = 1 \rightarrow \bar{Q} = 1$.

How does a flip-flop work?

Basic flip-flop: the SR latch

 

Logic table

\bar{S}	\bar{R}	Q	\bar{Q}
1	1	Q_0	\bar{Q}_0
0	1	1	0
1	0	0	1
0	0	1	1

Q_0 = value before
S&R changes

$\bar{R} = 0$ & $\bar{S} = 1$:

➤ $\bar{S} = 1$ & assume $\bar{Q} = 0 \rightarrow Q = 1$.

$\bar{S} = 1$ & assume $\bar{Q} = 1 \rightarrow Q = 0$.

➤ $\bar{R} = 0$ & assume $Q = 0 \rightarrow \bar{Q} = 1$.

$\bar{R} = 0$ & assume $Q = 1 \rightarrow \bar{Q} = 1$.


consistent



$\bar{R}=0$ & $\bar{S}=1 \rightarrow Q=0$ & $\bar{Q}=1$

How does a flip-flop work?

Basic flip-flop: the SR latch

 

Logic table

\bar{S}	\bar{R}	Q	\bar{Q}
1	1	Q_0	\bar{Q}_0
0	1	1	0
1	0	0	1
0	0	1	1


Q_0 = value before
S&R changes

$\bar{R} = 1$ & $\bar{S} = 0$:

→ The opposite of $\bar{R} = 0$ & $\bar{S} = 1$ by symmetry.

How does a flip-flop work?

Basic flip-flop: the SR latch

 

Logic table

\bar{S}	\bar{R}	Q	\bar{Q}
1	1	Q_0	\bar{Q}_0
0	1	1	0
1	0	0	1
0	0	1	1


Q_0 = value before
S&R changes

$\bar{R} = 1$ & $\bar{S} = 1$:

- $\bar{S} = 1$ & assume $\bar{Q} = 0 \rightarrow Q = 1$.
- $\bar{S} = 1$ & assume $\bar{Q} = 1 \rightarrow Q = 0$.
- $\bar{R} = 1$ & assume $Q = 0 \rightarrow \bar{Q} = 1$.
- $\bar{R} = 1$ & assume $Q = 1 \rightarrow \bar{Q} = 0$.

How does a flip-flop work?

Basic flip-flop: the SR latch

 

Logic table

\bar{S}	\bar{R}	Q	\bar{Q}
1	1	Q_0	\bar{Q}_0
0	1	1	0
1	0	0	1
0	0	1	1

Q_0 = value before
S&R changes

$\bar{R} = 1$ & $\bar{S} = 1$:

➤ $\bar{S} = 1$ & assume $\bar{Q} = 0 \rightarrow Q = 1$.

consistent

$\bar{R}=1$ & $\bar{S}=1 \rightarrow Q=1$ & $\bar{Q}=0$

$\bar{S} = 1$ & assume $\bar{Q} = 1 \rightarrow Q = 0$.

➤ $\bar{R} = 1$ & assume $Q = 0 \rightarrow \bar{Q} = 1$.


consistent

$\bar{R}=1$ & $\bar{S}=1 \rightarrow Q=0$ & $\bar{Q}=1$

$\bar{R} = 1$ & assume $Q = 1 \rightarrow \bar{Q} = 0$.

How does a flip-flop work?

Basic flip-flop: the SR latch

 

Logic table

\bar{S}	\bar{R}	Q	\bar{Q}
1	1	Q_0	\bar{Q}_0
0	1	1	0
1	0	0	1
0	0	1	1

Q_0 = value before
S&R changes

$\bar{R} = 1$ & $\bar{S} = 1$:

➤ $\bar{S} = 1$ & assume $\bar{Q} = 0 \rightarrow Q = 1$.

consistent

$\bar{R}=1$ & $\bar{S}=1 \rightarrow Q=1$ & $\bar{Q}=0$

$\bar{S} = 1$ & assume $\bar{Q} = 1 \rightarrow Q = 0$.

➤ $\bar{R} = 1$ & assume $Q = 0 \rightarrow \bar{Q} = 1$.

consistent

$\bar{R}=1$ & $\bar{S}=1 \rightarrow Q=0$ & $\bar{Q}=1$

$\bar{R} = 1$ & assume $Q = 1 \rightarrow \bar{Q} = 0$.

Two settings are possible




→ i.e. flip-flop keeps its state.

SR Latch Switch Debouncer


SR latch flip-flops are not used much for memory, but they are used for debouncing switches.

Switch Bounce:

  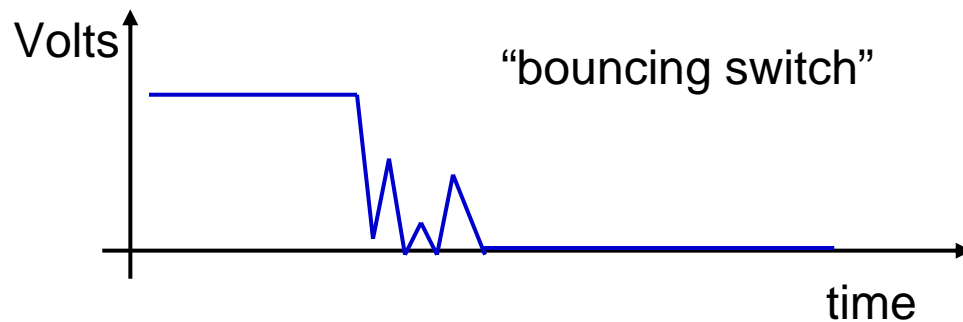When a switch is toggled it will not go smoothly from HIGH to LOW, or vice versa.



Clocked D-type Latch

 


Logic table

D	C	Q	\bar{Q}
X	0	Q_0	\bar{Q}_0
1	1	1	0
0	1	0	1

Clock Circuit Analysis:

- $C = 1 \ \& \ D = 1 \rightarrow \bar{S} = 0 \ \& \ \bar{R} = 1.$
 $C = 1 \ \& \ D = 0 \rightarrow \bar{S} = 1 \ \& \ \bar{R} = 0.$
- $C = 0 \ \& \ D = 1 \rightarrow \bar{S} = 1 \ \& \ \bar{R} = 1.$
 $C = 0 \ \& \ D = 0 \rightarrow \bar{S} = 1 \ \& \ \bar{R} = 1.$

Clocked D-type Latch

 


Logic table

D	C	Q	\bar{Q}
X	0	Q_0	\bar{Q}_0
1	1	1	0
0	1	0	1


Clock Circuit Analysis:

 - $C = 1 \ \& \ D = 1 \rightarrow \bar{S} = 0 \ \& \ \bar{R} = 1.$
- $C = 1 \ \& \ D = 0 \rightarrow \bar{S} = 1 \ \& \ \bar{R} = 0.$




Clock HIGH: D sets the flip-flop state

 - $C = 0 \ \& \ D = 1 \rightarrow \bar{S} = 1 \ \& \ \bar{R} = 1.$
- $C = 0 \ \& \ D = 0 \rightarrow \bar{S} = 1 \ \& \ \bar{R} = 1.$



Clock LOW: flip-flop state is locked

Clocked D-type Latch

 


Logic table

D	C	Q	\bar{Q}
X	0	Q_0	\bar{Q}_0
1	1	1	0
0	1	0	1


Clock Circuit Analysis:

 - $C = 1 \ \& \ D = 1 \ \rightarrow \ \bar{S} = 0 \ \& \ \bar{R} = 1.$
- $C = 1 \ \& \ D = 0 \ \rightarrow \ \bar{S} = 1 \ \& \ \bar{R} = 0.$




Clock HIGH: D sets the flip-flop state

 - $C = 0 \ \& \ D = 1 \ \rightarrow \ \bar{S} = 1 \ \& \ \bar{R} = 1.$
- $C = 0 \ \& \ D = 0 \ \rightarrow \ \bar{S} = 1 \ \& \ \bar{R} = 1.$




Clock LOW: flip-flop state is locked

Master-Slave D-type Flip-Flop

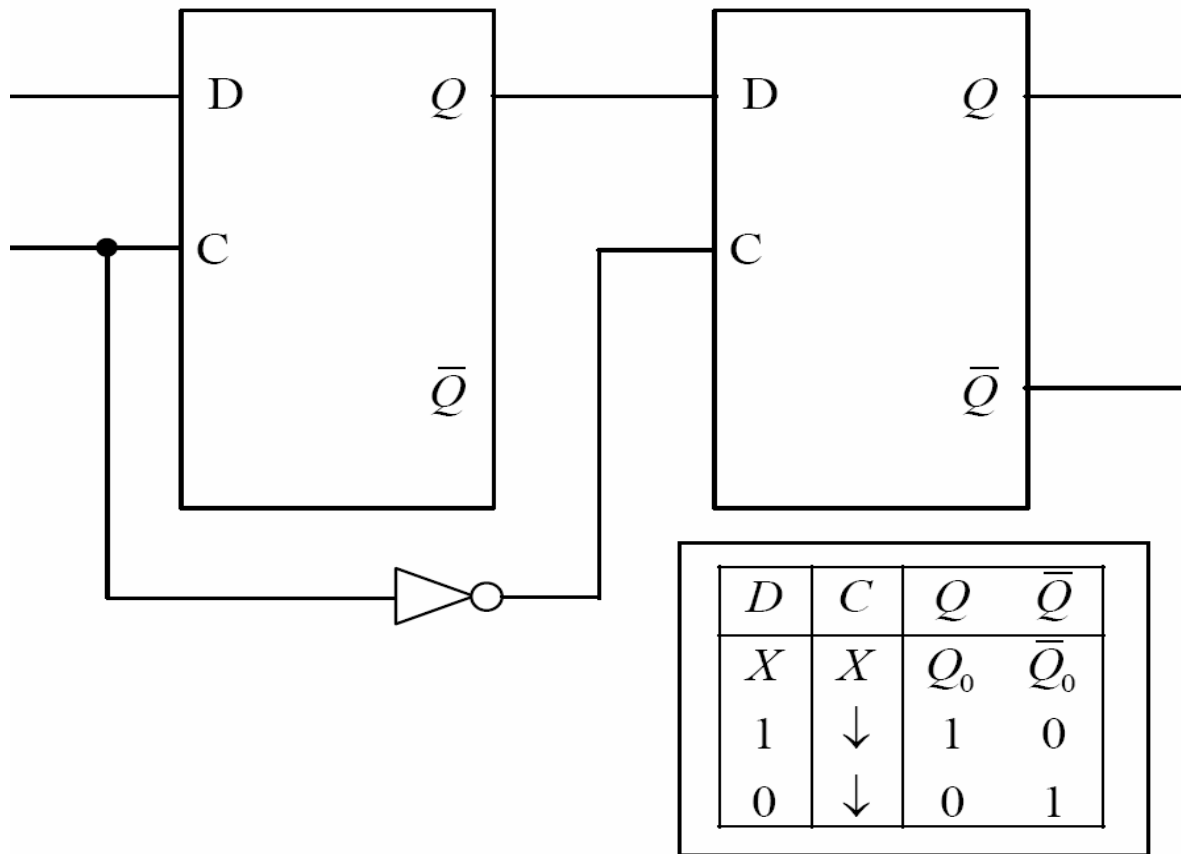

Note: The flip-flop triggers on a the falling edge of the clock.

74LS74 D-type edge-triggered flip-flop

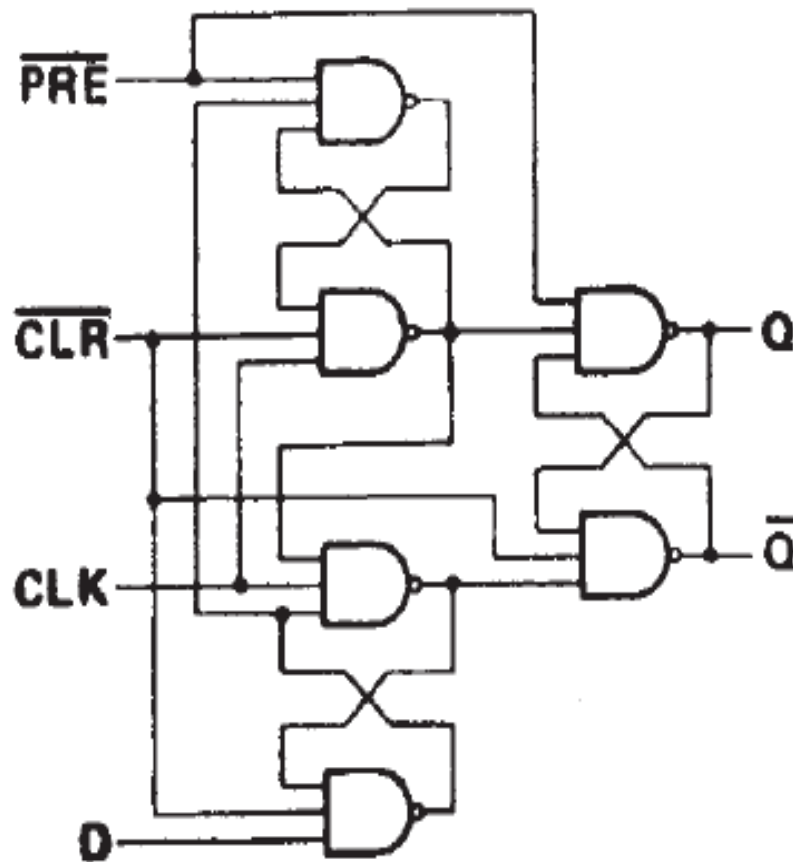

FUNCTION TABLE

INPUTS				OUTPUTS	
\overline{PRE}	\overline{CLR}	CLK	D	Q	\overline{Q}
L	H	X	X	H	L
H	L	X	X	L	H
L	L	X	X	H^\dagger	H^\dagger
H	H	\uparrow	H	H	L
H	H	\uparrow	L	L	H
H	H	L	X	Q_0	\overline{Q}_0


[Texas Instruments 74LS74 flip-flop datasheet]

Both \overline{PRE} and \overline{CLR} behave like \overline{S} and \overline{R} inputs, respectively, on the SR latch.

IMPORTANT: Both \overline{PRE} and \overline{CLR} must be high for normal D-type operation.

Note: The flip-flop triggers on a the rising edge of the clock.

JK-type flip-flop

 


Logic table
for clock falling edge

J	K	Q_{n+1}
0	0	Q_n
1	0	0
0	1	1
1	1	$\overline{Q_n}$

JK-type flip-flops are used in counters.

Flip-flops in FPGAs

Architecture of a single Logic Element

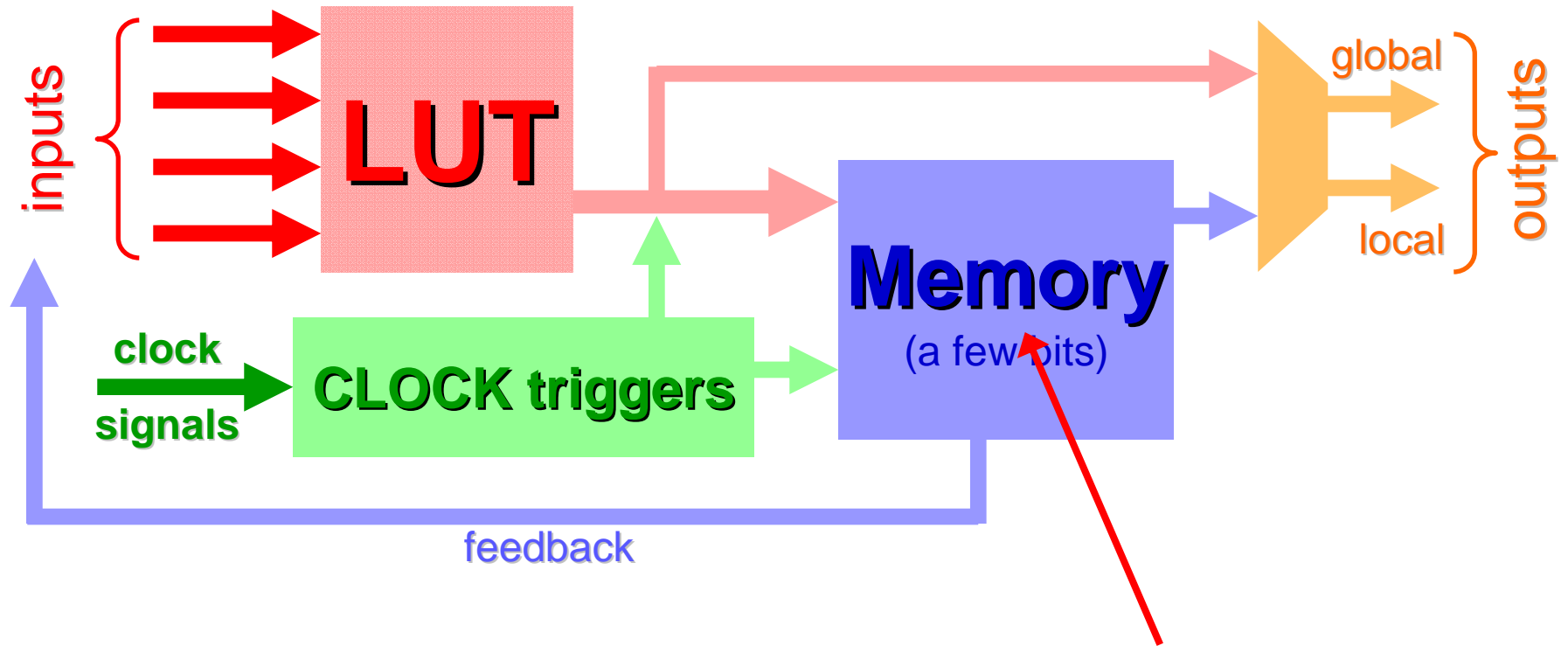


Frequently a D-type Flip-Flop



FPGAs are already set-up for synchronous circuit designs

Flip-flops in FPGAs

Architecture of a single Logic Element

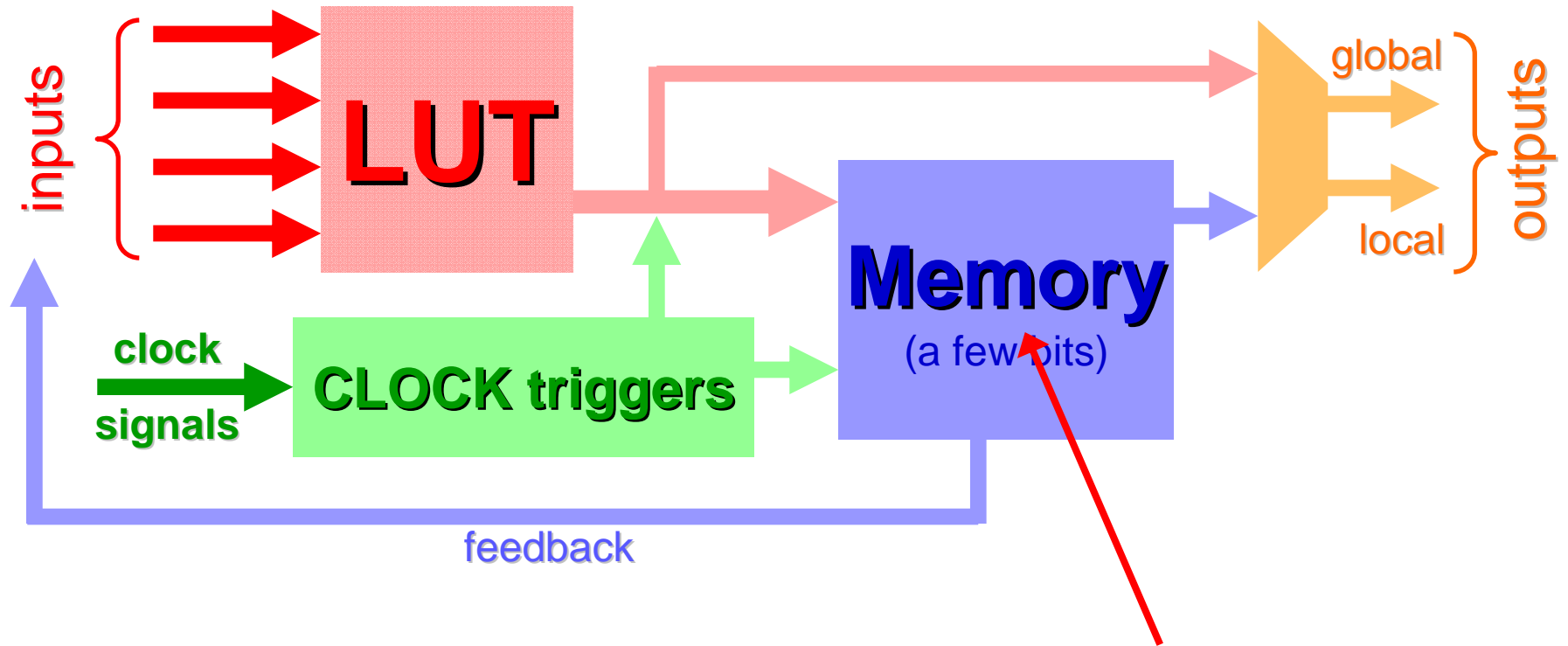

Frequently a D-type Flip-Flop



FPGAs are already set-up for synchronous circuit designs

Synchronous programming in Verilog (I)

```
1  module adder_always(clock, input1, input2, result);
2      input [3:0] input1;           // 4-bit input, first number
3      input [3:0] input2;           // 4-bit input, second number
4
5      input clock;                  // 1-bit clock input
6
7      output reg [4:0] result;      // 5-bit output register
8
9      always@(posedge clock)       // performs this section on the positive clock edge
10     begin
11         result = input1 + input2; // Standard 4-bit addition
12     end
13
14 endmodule
15
```


Synchronous programming in Verilog (I)

```
1 module adder_always(clock, input1, input2, result);
2     input [3:0] input1;           // 4-bit input, first number
3     input [3:0] input2;           // 4-bit input, second number
4
5     input clock;                  // 1-bit clock input
6
7     output reg [4:0] result;      // 5-bit output register
8
9     always@(posedge clock)        // performs this section on the positive clock edge
10    begin
11        result = input1 + input2; // Standard 4-bit addition
12    end
13
14 endmodule
15
```

Clock variable

output register
(i.e. flip-flop memory)

Synchronous programming in Verilog (I)

```
1 module adder_always(clock, input1, input2, result);
2     input [3:0] input1;           // 4-bit input, first number
3     input [3:0] input2;           // 4-bit input, second number
4
5     input clock;                  // 1-bit clock input
6
7     output reg [4:0] result;      // 5-bit output register
8
9     always@(posedge clock)        // performs this section on the positive clock edge
10    begin
11        result = input1 + input2; // Standard 4-bit addition
12    end
13
14 endmodule
15
```

Clock variable

output register (i.e. flip-flop memory)


Read as “always at the positive clock edge do the following ...”

“always” is the core command for synchronous programming, it should be used as frequently as possible.

“assign” should be used as little as possible. It is only useful for DC-type signals (signals that don’t change).


Synchronous programming in Verilog (II)

Quartus II circuit simulation

 

Synchronous programming in Verilog (II)


Quartus II circuit simulation

 

No more glitches


How did the FPGA implement the circuit?

Tools > Netlists > Technology Map Viewer

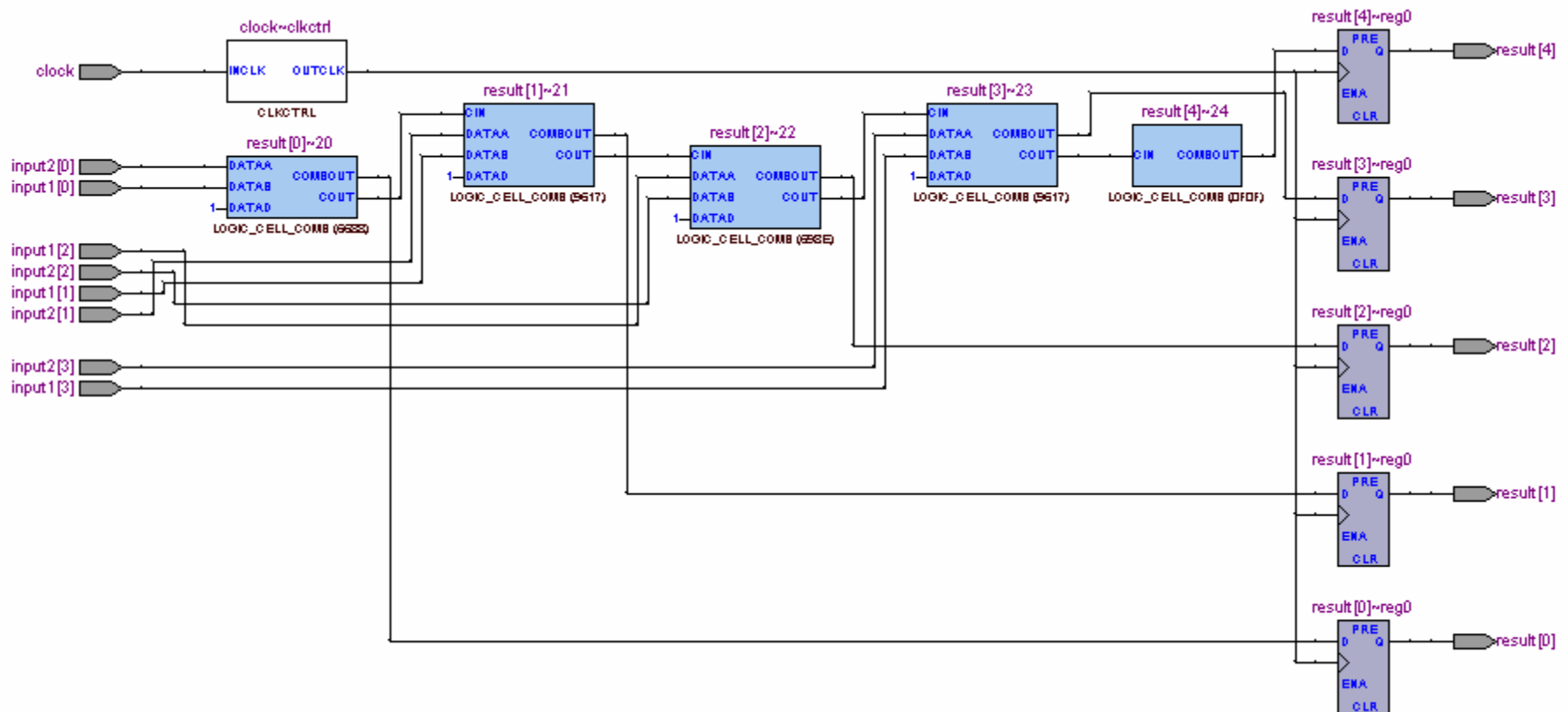

How did the FPGA implement the circuit?

Tools > Netlists > Technology Map Viewer

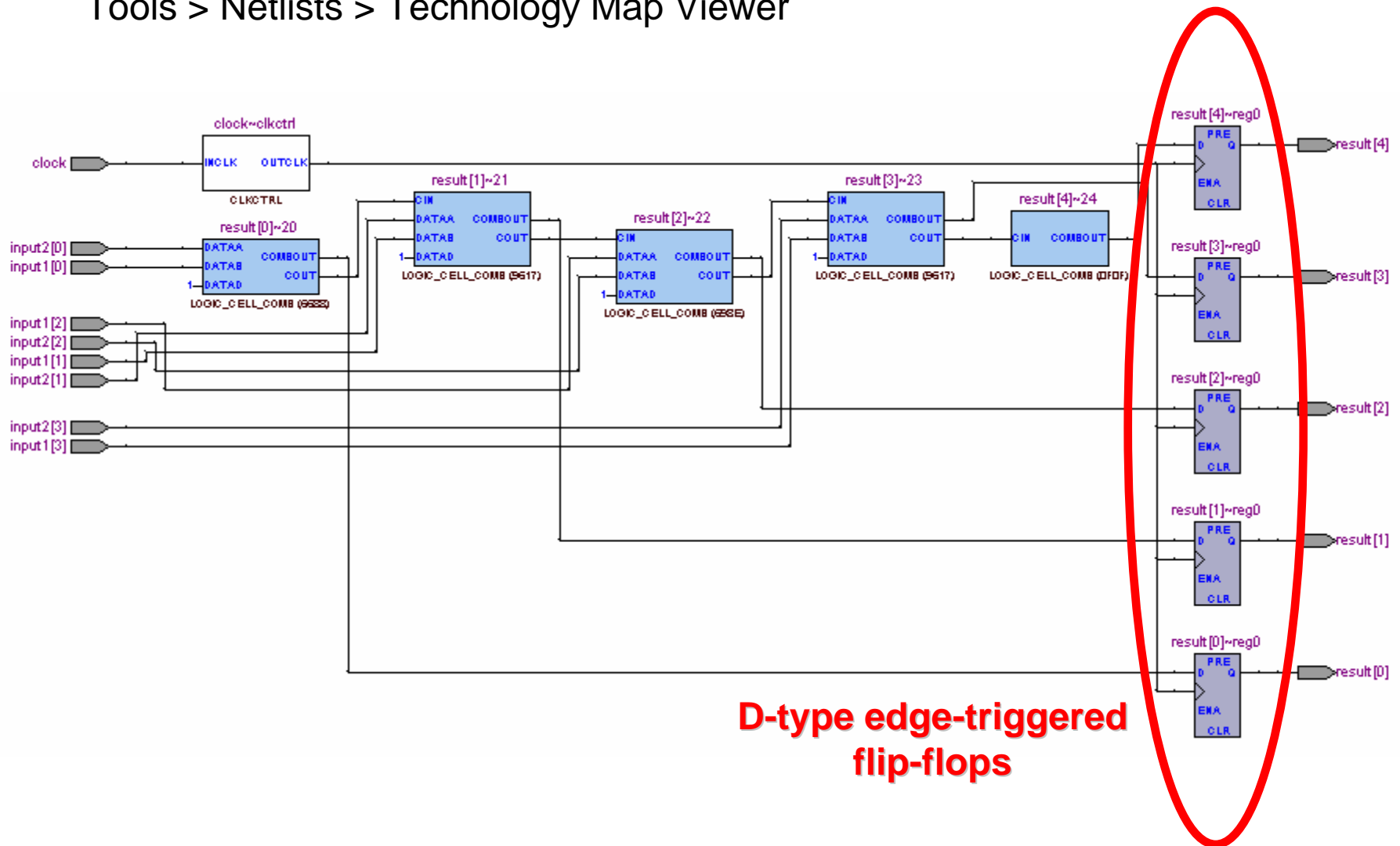

**Always use
“always”**

– A. Stummer, U. of Toronto.

Parallel programming in Verilog

- The “always” structure is used for exploiting the parallel processing features of the FPGA.
- Parallel processing must almost always be synchronous if several processes exchange data.

Parallel and Sequential processing examples:

Sequential

```
always@ (negedge clock)  
begin  
a = b;  
c = a;  
end
```

Parallel


```
always@ (negedge clock)  
begin  
a <= b;  
c <= a;  
end
```


Parallel programming in Verilog

- The “always” structure is used for exploiting the parallel processing features of the FPGA.
- Parallel processing must almost always be synchronous if several processes exchange data.

Parallel and Sequential processing examples:
 
```
Sequential  
always@ (negedge clock)  
begin  
  a = b;  
  c = a;  
end
```



```
Parallel  
always@ (negedge clock)  
begin  
  a <= b;  
  c <= a;  
end
```

executed simultaneously

