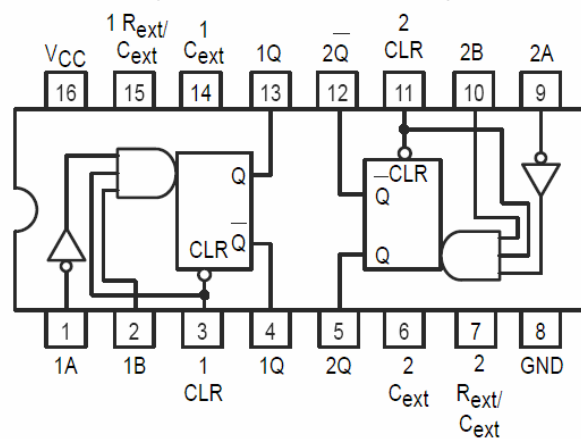


Laboratory 4: One Shots, clocks, and timing

1. Use 74LS123 dual one-shots with external resistors and capacitors to generate pulses with a $30\ \mu\text{s}$ width.
2. Use two one-shots to generate a $30\ \mu\text{s}$ pulse that is delayed from a trigger by $1\ \text{ms}$.
3. Use a Verilog program, an FPGA, and a $50\ \text{MHz}$ clock to generate a $30\ \mu\text{s}$ pulse that is delayed from a trigger by $1\ \text{ms}$.
4. Generate a $1\ \text{MHz}$ square wave with a function generator. Use a Verilog program and an FPGA to transform this $1\ \text{MHz}$ square wave to a $125\ \text{kHz}$ square wave.

Monostable Multivibrator (74__123N)



**LS123
FUNCTIONAL TABLE**

INPUTS			OUTPUTS	
CLEAR	A	B	Q	Q
L	X	X	L	H
X	H	X	L	H
X	X	L	L	H
H	L	↑		
H	↓	H		
↑	L	H		