 



Laboratory 6: Counters and State Machines

This week we learn how to use a counter and how to implement a state machine.

- Use a 74F269 as an eight-bit count-down counter. Its functional table, truth table, pinout, and logical symbol are shown below. Use your TTL pulse generator at a very low frequency as the clock input. Your counter should be designed to load a number from your slide switches when you push a button and then count down. Verify the truth table for \overline{TC} . What effects do \overline{CEP} and \overline{CET} have on \overline{TC} ? One can use \overline{TC} to control \overline{CEP} to ensure count-and-stop operation. What happens if you try to control \overline{CET} instead?
- Implement either Design Exercise 6-1 OR Design Exercise 6-2. You may construct the circuit with 74XXXXX-type chips OR use the FPGA on the DE2 board (your Quartus II project can be in either schematic or Verilog format).



Pin Names	Description
P ₀ -P ₇	Parallel Data Inputs
\overline{PE}	Parallel Enable Input (Active LOW)
U/ \overline{D}	Up-Down Count Control Input
\overline{CEP}	Count Enable Parallel Input (Active LOW)
\overline{CET}	Count Enable Trickle Input (Active LOW)
CP	Clock Input
\overline{TC}	Terminal Count Output (Active LOW)
Q ₀ -Q ₇	Flip-Flop Outputs

 

\overline{PE}	\overline{CEP}	\overline{CET}	U/ \overline{D}	CP	Function
L	X	X	X	↗	Parallel Load All Flip-Flops
H	H	X	X	↗	Hold
H	X	H	X	↗	Hold (\overline{TC} Held HIGH)
H	L	L	H	↗	Count Up
H	L	L	L	↗	Count Down

H = HIGH Voltage Level
 L = LOW Voltage Level
 X = Immaterial
 ↗ = Transition LOW-to-HIGH