

# Undergraduate Research

Today 3:30-5pm @ Tucker Hall → Summer Research Info Session.

Today 7-8pm @ Tucker Hall → Graduate School Fellowships.

More info on-line at:

<http://web.wm.edu/charlescenter/FOURweek08.php>



The summer between Junior and Senior year is the best time to get into an REU summer program !!!


# Project Teams

## Reminder:

Choose project teams on or before lab on Wednesday.

Max number of teams: 5

New budget: \$200/team


 


*Last year's DSP Design Competition winners  
Trevor Harrison, William Ames, and Sarah Mohon*

## Current teams:


- Jordan Gates, Ryan Zielinski, Justin Vazquez.

# T-type flip-flop

  

JK Logic table

J	K	$Q_{n+1}$
0	0	$Q_n$
1	0	0
0	1	1
1	1	$\bar{Q}_n$

 

T Logic table  
(clock falling edge)

T	$Q_{n+1}$
0	$Q_n$
1	$\bar{Q}_n$

T-type flip-flops are used in counters.

# Multiplexers

## What's a multiplexer ?

A multiplexer is a generalized multi-input and multi-output gate. It will produce a specific multiple line output for each specific multiple line input.

**Example:** 3-line input and 4-line output (i.e. 3-to-4 multiplexer).

A	B	C	1	2	3	4
0	0	0	0	0	0	1
0	0	1	0	0	1	0
0	1	0	0	1	0	0
1	0	0	1	0	0	0
1	1	0	1	1	0	0
0	1	1	0	1	1	0
1	0	1	1	0	1	0
1	1	1	0	0	0	1

N.B. Multiplexers can be very useful for converting a binary number to a HEX display code.

# Multiplexers with FPGAs (1a)

You could build a multiplexer out of logic gates using Karnaugh maps  
... or you could let the Verilog compiler figure it out.

N-to-1 multiplexer:

```
mux_primitive.v
1 primitive mux_primitive(out1,A,B,C); // 3-to-1 multiplexer
2     input A, B, C; // 3 input wires
3     output out1; // 1 output wire
4
5     table // table defines the output based on the 3 inputs
6         // A B C out1
7         0 0 0 : 0 ;
8         0 0 1 : 0 ;
9         0 1 0 : 0 ;
10        1 0 0 : 1 ;
11        1 1 0 : 1 ;
12        0 1 1 : 0 ;
13        1 0 1 : 1 ;
14        1 1 1 : 0 ;
15    endtable
16
17 endprimitive
18
```

# Multiplexers with FPGAs (Ila)

An always block with “if” statements can be used for an N-to-M multiplexer:

mux\_always\_if.v

```
1 module mux_always_if(input_3bit, output_4bit); // 3-to-4 multiplexer
2     input [2:0] input_3bit; // 3 input lines (bits)
3     output reg [3:0] output_4bit; // 4-bit output register
4
5     // always block with "if" statement for each input case
6     always
7     begin
8         if(input_3bit == 3'b000) output_4bit <= 4'b0001;
9         if(input_3bit == 3'b001) output_4bit <= 4'b0010;
10        if(input_3bit == 3'b010) output_4bit <= 4'b0100;
11        if(input_3bit == 3'b100) output_4bit <= 4'b1000;
12        if(input_3bit == 3'b110) output_4bit <= 4'b1100;
13        if(input_3bit == 3'b011) output_4bit <= 4'b0110;
14        if(input_3bit == 3'b101) output_4bit <= 4'b1010;
15        if(input_3bit == 3'b111) output_4bit <= 4'b0001;
16    end
17 endmodule
18
```

An always block guarantees that you won't have any signal races or glitches.

# Multiplexers with FPGAs (III)

An always block with “case” constructs can be used for an N-to-M multiplexer:

```
1  module mux_always_case(input_3bit,output_4bit);    // 3-to-4 multiplexer
2      input  [2:0] input_3bit;                      // 3-bit input
3      output reg [3:0] output_4bit;                // 4-bit output
4
5      always // always block with "case" construct
6      begin
7          case(input_3bit)
8              3'b000: output_4bit <= 4'b0001;
9              3'b001: output_4bit <= 4'b0010;
10             3'b010: output_4bit <= 4'b0100;
11             3'b100: output_4bit <= 4'b1000;
12             3'b110: output_4bit <= 4'b1100;
13             3'b011: output_4bit <= 4'b0110;
14             3'b101: output_4bit <= 4'b1010;
15             3'b111: output_4bit <= 4'b0001;
16         endcase
17     end
18
19 endmodule
```

# Multiple Modules

multiple\_modules.v

```
1 module multiple_modules(input_clock, output_FourBits); // top-level module
2     input input_clock; // input wire
3     output [3:0] output_FourBits; // output wires
4
5     wire [2:0] counter_output; // output wires of counter
6     wire [2:0] mux_input; // input wires of multiplexer
7
8     assign mux_input = counter_output; // connect the counter output and multiplexer input wires
9
10    counter counter_result(input_clock, counter_output); // call the "counter" module
11 // with instance "counter_result"
12
13    mux_always_case mux_output(mux_input, output_FourBits); // call the "mux_always_case" module
14 // with instance " mux_output"
15
16 endmodule
17
```

mux\_always\_case.v\*

```
1 module mux_always_case(input_3bit,output_4bit); // 3-
2     input [2:0] input_3bit; // 3-bit input
3     output reg [3:0] output_4bit; // 4-bit output
4
5     always // always block with "case" construct
6     begin
7         case(input_3bit)
8             3'b000: output_4bit <= 4'b0001;
9             3'b001: output_4bit <= 4'b0010;
10            3'b010: output_4bit <= 4'b0100;
11            3'b100: output_4bit <= 4'b1000;
12            3'b110: output_4bit <= 4'b1100;
13            3'b011: output_4bit <= 4'b0110;
14            3'b101: output_4bit <= 4'b1010;
15            3'b111: output_4bit <= 4'b0001;
16        endcase
17    end
18
19 endmodule
20
```

counter.v

```
1 module counter(input_clk, output_3bit);
2     input input_clk;
3     output reg [2:0] output_3bit;
4
5     always@(posedge input_clk)
6     begin
7         output_3bit <= output_3bit + 3'b001;
8     end
9
10 endmodule
11
```



# Multiple Modules

multiple\_modules.v

```
1 module multiple_modules(input_clock, output_FourBits); // top-level module
2     input input_clock; // input wire
3     output [3:0] output_FourBits; // output wires
4
5     wire [2:0] counter_output; // output wires of counter
6     wire [2:0] mux_input; // input wires of multiplexer
7
8     assign mux_input = counter_output; // connect the counter output and multiplexer input wires
9
10    counter counter_result(input_clock, counter_output); // call the "counter" module
11    // with instance "counter_result"
12
13    mux_always_case mux_output(mux_input, output_FourBits); // call the "mux_always_case" module
14    // with instance " mux_output"
15
16 endmodule
17
```

**Wires for connecting the 2 lower level modules**

**module name instance name**

mux\_always\_case.v\*

```
1 module mux_always_case(input_3bit,output_4bit); // 3-
2     input [2:0] input_3bit; // 3-bit input
3     output reg [3:0] output_4bit; // 4-bit output
4
5     always // always block with "case" construct
6     begin
7         case(input_3bit)
8             3'b000: output_4bit <= 4'b0001;
9             3'b001: output_4bit <= 4'b0010;
10            3'b010: output_4bit <= 4'b0100;
11            3'b100: output_4bit <= 4'b1000;
12            3'b110: output_4bit <= 4'b1100;
13            3'b011: output_4bit <= 4'b0110;
14            3'b101: output_4bit <= 4'b1010;
15            3'b111: output_4bit <= 4'b0001;
16        endcase
17    end
18
19 endmodule
20
```

counter.v

```
1 module counter(input_clk, output_3bit);
2     input input_clk;
3     output reg [2:0] output_3bit;
4
5     always@(posedge input_clk)
6     begin
7         output_3bit <= output_3bit + 3'b001;
8     end
9
10 endmodule
11
```

# Multiple Modules

multiple\_modules.v

```
1 module multiple_modules(input_clock, output_FourBits); // top-level module
2     input input_clock; // input wire
3     output [3:0] output_FourBits; // output wires
4
5     wire [2:0] counter_output; // output wires of counter
6     wire [2:0] mux_input; // input wires of multiplexer
7
8     assign mux_input = counter_output; // connect the counter output and multiplexer input wires
9
10    counter counter_result(input_clock, counter_output); // call the "counter" module
11                                     // with instance "counter_result"
12
13    mux_always_case mux_output(mux_input, output_FourBits); // call the "mux_always_case" module
14                                                         // with instance " mux_output"
15
16 endmodule
17
```

**Warning: DO NOT make these registers !!!**

**module name instance name**

counter.v

```
1 module counter(input_clk, output_3bit);
2     input input_clk;
3     output reg [2:0] output_3bit;
4
5     always@(posedge input_clk)
6     begin
7         output_3bit <= output_3bit + 3'b001;
8     end
9
10 endmodule
11
```

mux\_always\_case.v\*

```
1 module mux_always_case(input_3bit,output_4bit); // 3-
2     input [2:0] input_3bit; // 3-bit input
3     output reg [3:0] output_4bit; // 4-bit output
4
5     always // always block with "case" construct
6     begin
7         case(input_3bit)
8             3'b000: output_4bit <= 4'b0001;
9             3'b001: output_4bit <= 4'b0010;
10            3'b010: output_4bit <= 4'b0100;
11            3'b100: output_4bit <= 4'b1000;
12            3'b110: output_4bit <= 4'b1100;
13            3'b011: output_4bit <= 4'b0110;
14            3'b101: output_4bit <= 4'b1010;
15            3'b111: output_4bit <= 4'b0001;
16        endcase
17    end
18
19 endmodule
20
```