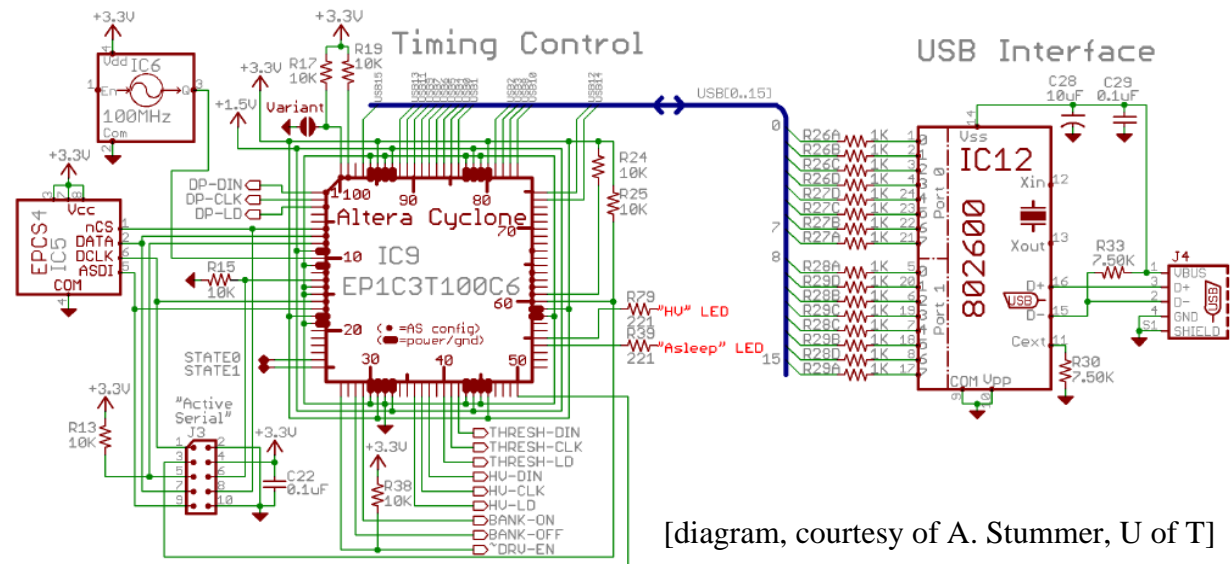


# Physics 351: Electronics II

## Introduction to Digital Circuits

*Prerequisites: PHYS 252.*

Introduction to digital electronics: Theory, design, and application of digital circuits ... or how to understand and make circuits like these:



[diagram, courtesy of A. Stummer, U of T]

*Small print: If you don't have any experience with analog electronics you should talk to me after class.*

# Instructors

## Prof. Seth Aubin

Office: room 333, Small Hall (3rd floor back hall), tel: 1-3545

Lab: room 15, Small Hall (basement, next to machine shop), tel: 1-3532

e-mail: [saaubi@wm.edu](mailto:saaubi@wm.edu)

web: <http://www.physics.wm.edu/~saubin/index.html>

## Austin Ziltz

Office: rooms 123S, Small Hall

e-mail: [arziltz@wm.edu](mailto:arziltz@wm.edu)

## Office hours:

Monday: 3-4 pm (Aubin, room 333, Small Hall)

Thursday: 11am-noon (Aubin, room 123S, Millington)

# Course Objectives

**Primary:** Design and test both basic and advanced digital circuits for *digital logic*, *signal acquisition*, and *digital signal processing*.

**Secondary:** Learn experimental research skills.



## Covered topics:

- Binary numbers, logic gates, and Karnaugh maps.
- Memory, flip-flops, and clocked latches.
- Clocks, timing, and one-shots.
- Counters, registers, and state machines.
- Analog-to-Digital Converters (ADC) and Digital-to-Analog Converters (DAC).
- Optical and magnetic isolation.
- **Field Programmable Gate Arrays (FPGA).**
- Verilog language FPGA programming.
- **Digital Signal Processing (DSP).**
- Microprocessors.

# FPGAs for Physicists

## Field Programmable Gate Array (FPGA) chips for physicists

- Contain 2,000-100,000 logic gates + memory.
- Reprogrammable via a computer (Quartus II v7-9).
- Stand alone circuitry (with flash memory).
- Parallel processing.
- ***Useful for complex circuits and Digital Signal Processing (DSP).***



Please download and install Quartus II WebEdition onto your laptop.

If necessary request a WebEdition license from Altera Inc.

(see course webpage for the necessary internet links)

Note: Quartus II is available on lab computers, in room 134 (Learning Center) of Swem library, and Morton 240 (24/7)

# DSP design project (I)

A central component of the course is an FPGA-based digital signal processing (DSP) project. The general guidelines for the projects are:

- Teams of 2-3 students (depends on lab section distribution).
- Each team has a budget of \$250 USD.
- All teams have the same project.
- This section of the course is a design and construction competition.

The purpose of the one month team project is to help you develop practical circuit design skills, as well as the following more general research skills:

- Complex device design.
- Project budgeting.
- Formal project proposal writing.
- Finding, selecting, and purchasing device components.
- Device construction.
- Troubleshooting and debugging.
- Oral and web presentations of the device.

# DSP design project (II)

## 2 choices for the design project:

### 1. Phase coherent, triggerable output **DSP PULSE FUNCTION GENERATOR**

- 1 analog output, several digital inputs.
- FPGA core.
- External clock option.
- Comments: more DSP, easier analog.



### 2. Digital **DSP VOICE RECORDER** with playback

- 1 analog input (i.e. microphone).
- 1 analog output (i.e. speaker).
- FPGA core.
- Comments: more memory handling, more involved analog.



# DSP design project (III)

- Easier project than last year, with more project time scheduled.
- The project will be based on an FPGA.
- The specific project requirements will be announced next week.
- The project is the most important part of the course.
- It will be graded according to the following weights:

Formal project proposal	10%
Device construction	15%
Device performance	20%
Oral presentation of device.	5%
Web presentation of device	5%
Project lab book and wiki	5%
<b>Total</b>	<b>60%</b>

# Evaluation

Notebooks/Reports:	30%
Quizzes/Participation:	10%
<u>DSP project:</u>	<u>60%</u>
Total =	100%

Note: There is no final exam for the course



# Due Dates

## ➤ Lab books

In addition to lab notes, the lab books should include all design exercises.

Lab books are due by 5pm 2 days after lab & will be returned by the next lab period:

- Thursdays for the Tuesday section
- Fridays for the Wednesday section

## ➤ Reports

- Reports are due on monday the following week.
- Instructor will indicate for which labs a report is due.
- You can expect 1-2 reports for the semester.
- Lab books should not be turned in when lab report is due.
- Important measured numbers should include an estimated uncertainty.

# Schedule (I)

**Week 0: 8/26**

**NO CLASS**

**Week 1: 8/31-9/2**

**Digital Logic**

Class & lab: Binary numbers, logic gates, Karnaugh maps.

**Week 2: 9/7-9**

**Introduction to FPGAs**

Class & lab: FPGAs, Verilog programming language, applications.

**Week 3: 9/14-16**

**Memory**

Class & lab: Memory, flip-flops.

**Week 4: 9/21-23**

**Timing**

Class & lab: Clocks, timing, one-shots, and counters.

**Week 5: 9/28-30**

**Counters and Registers**

Class & lab: Counters II and registers.

**Week 6: 10/5-7**

**Analog-Digital Interfacing**

Class & lab: Analog-to-digital converters, digital-to-analog converters.

**Project:** Formal project proposals are due October 9, 2009.

# Schedule (II)

**Week 6.5: 10/14** Wednesday lab group jumps one week ahead  
Class: No class; Lab: Project; project funds are released.

**Week 6: 10/19-21** **State Machines and Microprocessors**  
Class & lab: State machines and sequencing.

**Week 8: 10/26-28** **Project week 1**  
Class: Surface mount soldering review and machine shop training.  
**Project:** Project construction begins.

**Week 9: 11/2-4** **Project week 2**  
Class: Digital signal processing.  
**Lab & Project:** Project construction continues.

**Week 10: 11/9-11** **Project week 3**  
Class: Tri-state logic.  
**Lab & Project:** Project construction continues.

**Week 11: 11/16-18** **Project week 4**  
Class: Ground loops and opto-isolation.  
**Lab & Project:** Project construction and debugging.

# Schedule (III)

**Week 12: 11/23-24**

**Project week 5**

Class: Pulse electronics *or* phase-lock loops.

**Lab & Project:** Project debugging and troubleshooting. 2 sections equalize labs.

**Week 13: 11/30-12/2**

**Project week 6**

Class: Oral presentations and website launch.

**Lab & Project:** Device performance testing and review.

# **Introduction to Digital Logic**

# Digital Variables

A digital circuit has only 2 possible values HIGH (H or 1) and LOW (L or 0)

→ Does not need to be precision designed.

→ Not very sensitive to electronic noise.

Here are a few voltage-logic conventions:

Convention	Supply	LOW	HIGH	Speed
TTL	+ 5 V	< 0.7 V	> 2.0 V	~5 nS
LVTTL	+ 3.3 V	< 0.7 V	> 2.0 V	~5 nS
CMOS	+ 3-15 V	< 20% Supply	> 80% Supply	~10 nS
GaAs	undefined	undefined	undefined	~100 pS

# Digital vs. Analog

## **Digital**

- Easy to design (linear logic flow).
  - No feedback !
- Insensitive to electronic noise.
- Easy to design and make very complex circuits.
- Insensitive to specific components.
- Reliable isolation circuitry.
- Tends to consume a lot of power.
- Slower than analog equivalent.
- Very bad if a single bit is corrupted (std. error rate 1 part per  $10^{10}$ ).
  - Error correction is important.

## **Analog**

- Harder to design and read a circuit, especially with feedback.
- Noise is critical.
- Complex circuits are hard to design.
- Sensitive to specific components and quality of assembly.
- Isolation circuitry reduces accuracy.
- Can be low power.
- Very fast.
- Some circuits must be analog.

# Transistor-Transistor-Logic (TTL)

In this course, we will use almost exclusively the TTL family of logic chips.

Characteristics:

- Very reliable.
- Widely available.
- Silicon-based with bipolar transistors.
- Supply: + 5 V, High > 2 V, Low < 0.7 V
- 1 output can drive 10 inputs (fanout = 10).
- Never leave an input (or output) floating: it will tend to wander between H and L.

**CAUTION:** If any of your voltages are close to the range 0.7 – 2.0 V, then you should check your circuit and the components.




# Boolean Operators

## Identity

1 input  $\rightarrow$  1 output

0 input  $\rightarrow$  0 output

 


(also called a buffer)

## Inverter

1 input  $\rightarrow$  0 output

0 input  $\rightarrow$  1 output

 

Note: Boolean (adj.) refers to something that is 2-valued (named after G. Boole, 1815-1864).

# 2-input operators

## AND

→ Outputs H only if both inputs are H.

→ Written as a product:  
 $Y=AB$



INPUTS		OUTPUT
A	B	$AB = Y$
L	L	L
L	H	L
H	L	L
H	H	H

## OR

→ Outputs H only if either input is H.

→ Written as a sum:  
 $Y=A+B$



INPUTS		OUTPUT
A	B	$A+B = Y$
L	L	L
L	H	H
H	L	H
H	H	H

# More operators

## NAND



INPUTS		OUTPUT
A	B	$\overline{AB} = Y$
L	L	H
L	H	H
H	L	H
H	H	L

## NOR




INPUTS		OUTPUT
A	B	$\overline{A+B} = Y$
L	L	H
X	H	L
H	X	L

X = don't care (H or L)

# A little bit of analog

Analog realization of a NOR gate

 

INPUTS		OUTPUT
A	B	$\overline{A+B} = Y$
L	L	H
X	H	L
H	X	L

# Boolean logic identities

## Associative

$$ABC = (AB)C = A(BC)$$

$$A+B+C = (A+B)+C = A+(B+C)$$

## Commutative

$$AB = BA$$

$$A+B = B+A$$

## Others

$$AA = A$$

$$A1 = A$$

$$A0 = 0$$

$$A+A = A$$

$$A+1 = 1$$

$$A+0 = A$$

$$A + AB = A$$

$$A+BC = (A+B)(A+C)$$

$$A + \bar{A} = 1$$

$$A \bar{A} = 0$$

$$A + \bar{A} B = A+B$$

## DeMorgan's Theorem

$$\overline{A+B} = \bar{A} \bar{B}$$

$$\overline{AB} = \bar{A} + \bar{B}$$

# Exclusive OR

## XOR


→ Outputs H if either input is H, but not both.

→ Written as a plus sign with a circle around it:  $Y=A\oplus B$

INPUTS		OUTPUT
A	B	$A\oplus B = Y$
L	L	L
L	H	H
H	L	H
H	H	L



*XOR realization*

 

[diagram courtesy of Altera Inc.]

# The NAND and NOR gates

## DeMorgan's theorem corollary:

Any logic gate or operation can be constructed exclusively of NAND gates (or NOR gates).

**Note:** a NAND gate with the inputs tied together is a NOT gate.

# Hardware

Name	Expression	Inputs	Part #
AND	$AB$	2 (also 3&4)	74xx08
NAND	$\overline{AB}$	2 (also 3&4)	74xx00
OR	$A+B$	2 (also 3&4)	74xx32
NOR	$\overline{A+B}$	2 (also 3&4)	74xx02
Invert	$\overline{A}$	1	74xx04
Buffer	$A$	1	74xx365
XOR	$A\oplus B$	2 (also 3&4)	74xx86 / 386
XNOR	$\overline{A\oplus B}$	2 (also 3&4)	74xx266



Note: We will use mostly Low Speed TTL (xx = LS).



# Example: 74LS00
  
## Quad NAND gate chip

- 4 gates per chip.
- Requires + 5 V of power at  $V_{CC}$ .
- Requires a ground connection at GND.
- Never float an input (i.e. it will wander between 0 and 1).
- Each gate consists of about 20 components.



# Karnaugh Maps (I)

Logic table  $\rightarrow$  Karnaugh Map  $\rightarrow$  digital logic circuit

- Up to 4 inputs, 1 output.
- Always gives a solution, though not the most efficient one.

## Example:

- 3 person vote.
- 2-person majority produces H output.

A	B	C	Q
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

# Karnaugh Maps (II)

- Arrange inputs on either one of the two table axes.
  - Up to 2 inputs per axis.
  - Order of inputs is important: only one input change per row or column.
- (note: column order is circular.)

	A	L	L	H	H
	B	L	H	H	L
C					
L		L	L	H	L
H		L	H	H	H

# Karnaugh Maps (II)

- Arrange inputs on either one of the two table axes.
- Up to 2 inputs per axis.
- Order of inputs is important: only one input change per row or column.
- Group together the adjacent “ones”: these correspond to AND gates.
- Alternatively, group adjacent “zeros”:  
these correspond to OR gates.
- Write down the corresponding AND gates: AB, BC, AC

	A	L	L	H	H
	B	L	H	H	L
C					
L		L	L	H	L
H		L	H	H	H
			BC	AB	AC

**Solution:  $AB + BC + AC$**

# Karnaugh Maps (III)

		A	0	0	1	1
		B	0	1	1	0
C	D					
	0	0	1	1	0	1
0	1	0	1	0	0	
1	1	0	1	1	0	
1	0	1	1	1	0	

# Karnaugh Maps (III)

		A	0	0	1	1
		B	0	1	1	0
C	D					
	0	0	1	1	0	1
0	1	0	1	0	0	
1	1	0	1	1	0	
1	0	1	1	1	0	

# Karnaugh Maps (III)

		A			
		0	0	1	1
C \ D		B			
		0	1	1	0
0	0	1	1	0	1
0	1	0	1	0	0
1	1	0	1	1	0
1	0	1	1	1	0

AD̄ (green oval around (0,0) and (1,0))  
AB̄ (red oval around (0,0) and (0,1))  
BC (blue oval around (0,1), (1,1), (1,0), and (0,0))  
BCD̄ (orange dashed oval around (0,0) and (1,0))

Solution:  $\bar{A}B + BC + \bar{A}\bar{D} + \bar{B}\bar{C}\bar{D}$

# Binary Numbers

## Base 10 (i.e. decimal numbers)

$$73691 = 1 \times 10^0 + 9 \times 10^1 + 6 \times 10^2 + 3 \times 10^3 + 7 \times 10^4 = 73691_{10}$$

We can represent any integer in a digital circuit if we use base-2 representation.

## Base 2 (i.e. binary numbers)

$$\begin{aligned} 10011101 &= 1 \times 2^0 + 0 \times 2^1 + 1 \times 2^2 + 1 \times 2^3 + 1 \times 2^4 + 0 \times 2^5 + 0 \times 2^6 + 1 \times 2^7 = 10011101_2 \\ &= 1 + 0 + 4 + 8 + 16 + 0 + 0 + 128 = 157_{10} \end{aligned}$$



# Binary Numbers

## Base 10 (i.e. decimal numbers)

$$73691 = 1 \times 10^0 + 9 \times 10^1 + 6 \times 10^2 + 3 \times 10^3 + 7 \times 10^4 = 73691_{10}$$

We can represent any integer in a digital circuit if we use base-2 representation.

## Base 2 (i.e. binary numbers)

$$1001\textcircled{1}101 = 1 \times 2^0 + 0 \times 2^1 + 1 \times 2^2 + 1 \times 2^3 + 1 \times 2^4 + 0 \times 2^5 + 0 \times 2^6 + 1 \times 2^7 = 10011101_2$$

$$\text{1-bit} = 1 + 0 + 4 + 8 + 16 + 0 + 0 + 128 = 157_{10}$$

8-bits = 1 byte

# Binary Numbers

## Base 10 (i.e. decimal numbers)

$$73691 = 1 \times 10^0 + 9 \times 10^1 + 6 \times 10^2 + 3 \times 10^3 + 7 \times 10^4 = 73691_{10}$$

We can represent any integer in a digital circuit if we use base-2 representation.

## Base 2 (i.e. binary numbers)

$$1001\textcircled{1}101 = 1 \times 2^0 + 0 \times 2^1 + 1 \times 2^2 + 1 \times 2^3 + 1 \times 2^4 + 0 \times 2^5 + 0 \times 2^6 + 1 \times 2^7 = 10011101_2$$

1-bit = 1 + 0 + 4 + 8 + 16 + 0 + 0 + 128 = 157<sub>10</sub>

8-bits = 1 byte

## Base 16 (i.e. Hexadecimal numbers)

0, 1, 2, 3, 4, 5, 6, 7, 8, 9, A, B, C, D, E, F

# Decimal → Binary

- To convert from decimal to binary
  - Divides by 2 repeatedly & write the remainders
- To convert  $13_{10}$  to binary
  - $13/2 = 6$  remainder 1
  - $6/2 = 3$  remainder 0
  - $3/2 = 1$  remainder 1
  - $1/2 = 0$  remainder 1
- The digits come out in **right to left** order
  - $13_{10} = 1101_2$

# Binary Addition

## ➤ Examples

$$0101_2 + 0010_2 = 0111_2$$

$$0101_2 + 0001_2 = 0110_2$$

$$0111_2 + 0001_2 = 1000_2$$

## ➤ Differences between decimal & binary addition...

- In binary we carry half the time, on average.
- There are only a limited number of possible operands & resultants (1s or 0s).
- Makes digital implementation fairly simple.