

# Wiki Lab Book

- Use a wiki as a lab book.
- Wikis are excellent tools for collaborative work (i.e. where you need to efficiently share lots of information and files with multiple people).
- This week is practice for wiki usage during the project.
- Both lab partners will use the same wiki (i.e. you will both submit the same link to instructor and grader).
- Completeness is very important ... neatness should be easy.
- You may use any available wiki hosting service (wm, etc ...)
  - suggested provider: <http://pbwiki.com/>  
(... with only 10 MB of space, you can link to your W&M webspace to increase the effective memory available to your wiki).

# Web page lab report

- The lab report for this week's lab will be in the form of a webpage. The webpage should be in HTML (i.e. "filename.html"). You are free to use any webpage making program you wish, but extra credit will be awarded for those reports programmed directly by you in HTML.
- The webpage should be hosted on your public H drive space (i.e. if you name your webpage "index.html" and put it in the "public\_html" folder of your H drive, then you can view it at:  
    " <http://username.people.wm.edu/> "
- You should send a link to your "lab report webpage" by e-mail to the grader and the instructor by Monday, September 29 (midnight deadline).
- Lab report should cover lab exercises 1, 2, and 3.
- There is no length limit on the lab report.
- 1 lab report per person.

**Timing pulses  
&  
Intro to counters  
(hardware & Verilog)**


# Timing Pulses

- Important element of laboratory electronics
- Pulses can control logical sequences with precise timing.
  - If your detector “sees” a charged particle or a photon, you might want to signal a clock to store the time at which it occurred.
  - You could use the event to generate a standard pulse so that your clock always responds in the same way.
- Alternatively, you might need to reset your electronics after the event
  - Clearly you want the reset pulse to arrive as soon as possible after the data has been processed
  - This requires a precision time *delay generator*

# Timing Pulses

- A simple type of delay generator...
  1. A **D-type flip-flop** receives a clock edge and goes from low to high at the output
  2. The output charges up an **RC circuit** after going high.
  3. The charged capacitor also serves as the **clear input** to the D flip-flop.
  4. **So, that after a fixed time (roughly  $RC$ ) the flip-flop resets back to its initial state.**
  5. The net result is a single pulse that has a duration (or *pulse width*) determined by the combination of the resistor & capacitor
  
- This is called a *monostable multivibrator* or *one-shot*.

# One-shot: D-type flip-flop

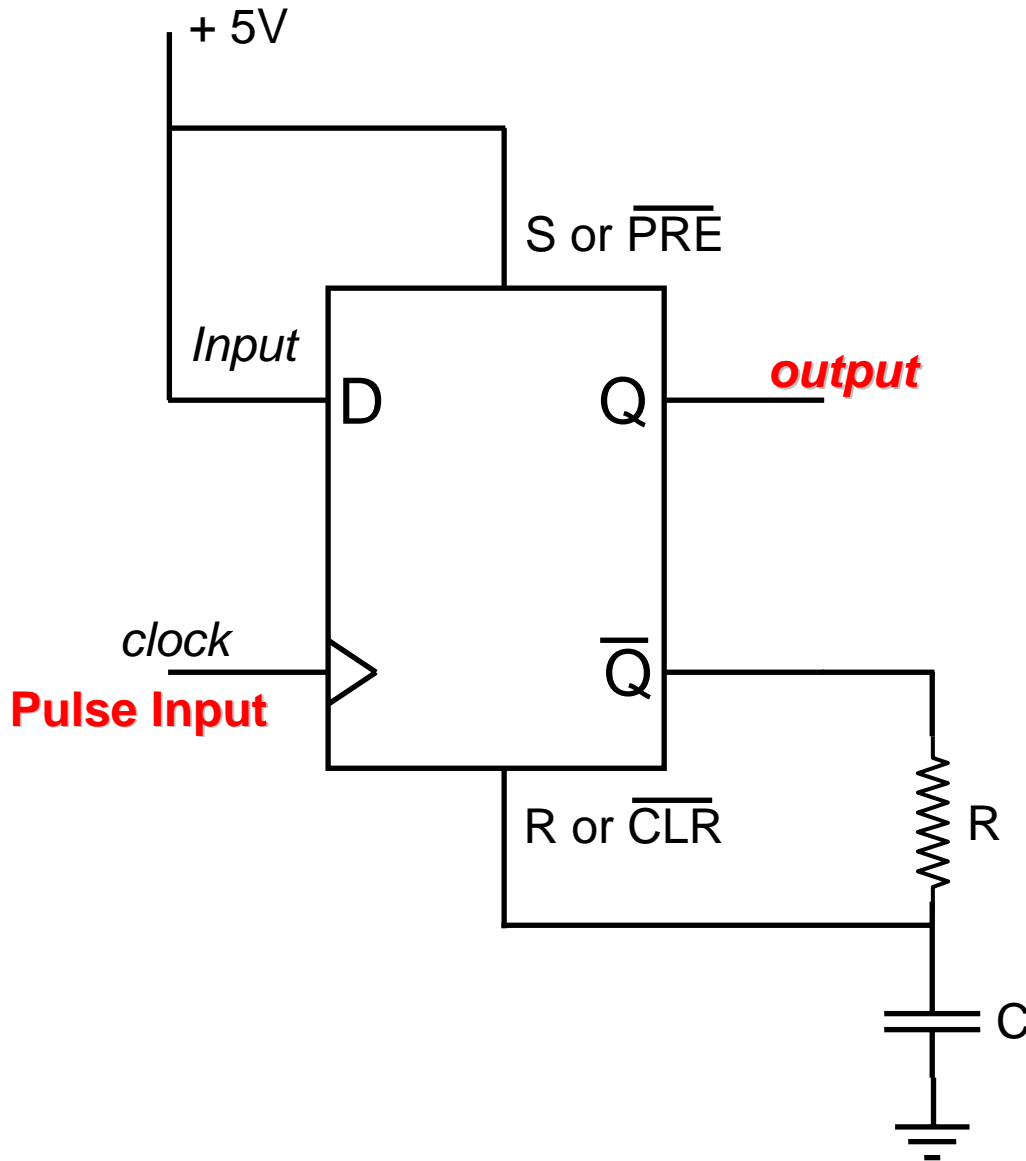


FUNCTION TABLE

INPUTS				OUTPUTS	
$\overline{\text{PRE}}$	$\overline{\text{CLR}}$	CLK	D	Q	$\overline{\text{Q}}$
L	H	X	X	H	L
H	L	X	X	L	H
L	L	X	X	H <sup>†</sup>	H <sup>†</sup>
H	H	↑	H	H	L
H	H	↑	L	L	H
H	H	L	X	Q <sub>0</sub>	$\overline{\text{Q}}_0$

[Texas Instruments 74LS74 flip-flop datasheet]

# One-shot: D-type flip-flop

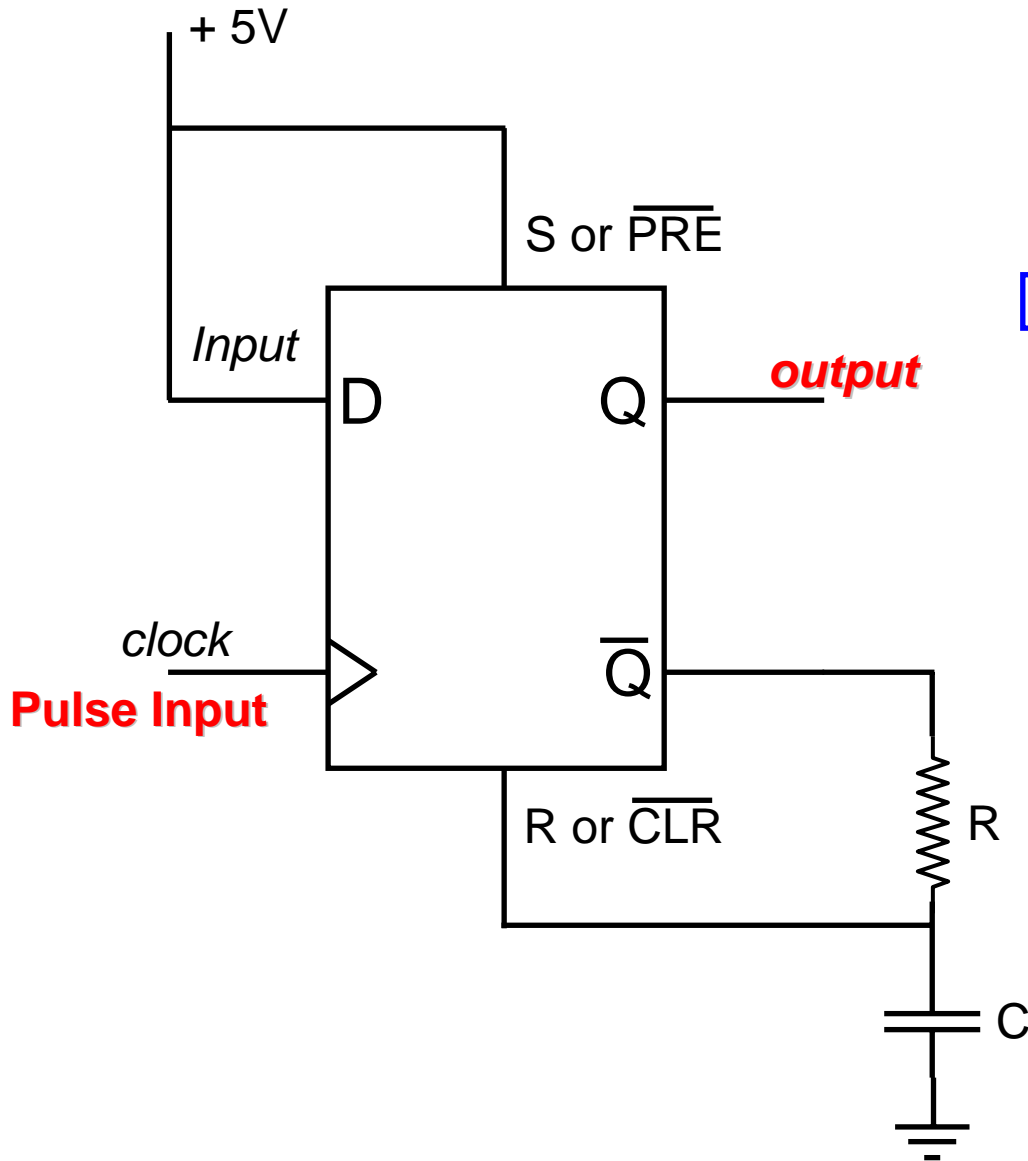


FUNCTION TABLE

INPUTS				OUTPUTS	
$\overline{\text{PRE}}$	$\overline{\text{CLR}}$	CLK	D	Q	$\overline{\text{Q}}$
L	H	X	X	H	L
H	L	X	X	L	H
L	L	X	X	H $\uparrow$	H $\uparrow$
H	H	$\uparrow$	H	H	L
H	H	$\uparrow$	L	L	H
H	H	L	X	Q <sub>0</sub>	$\overline{\text{Q}}_0$

[Texas Instruments 74LS74 flip-flop datasheet]

# One-shot: D-type flip-flop

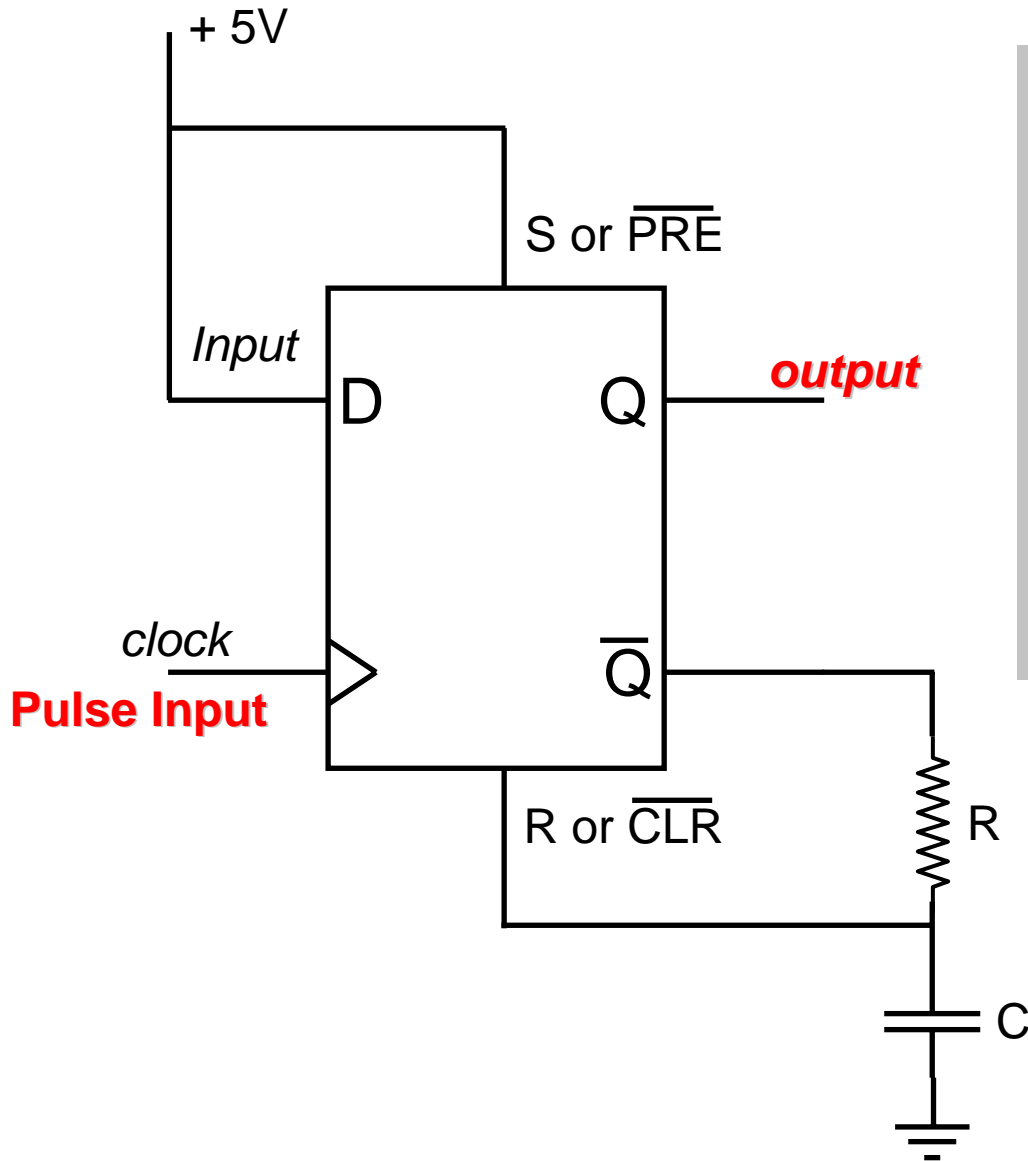

FUNCTION TABLE

PRE	INPUTS			OUTPUTS	
	$\overline{\text{CLR}}$	CLK	D	Q	$\overline{\text{Q}}$
L	H	X	X	H	L
H	L	X	X	L	H
L	L	X	X	H	H
H	H	↑	H	H	L
H	H	↑	L	L	H
H	H	L	X	$Q_0$	$\overline{Q_0}$

[Texas Instruments 74LS74 flip-flop datasheet]




# One-shot: 74LS123

## Characteristics:

- 2 clock inputs triggered by either a **rising edge** or a **falling edge**.
- 2 outputs ( $Q$  &  $\overline{Q}$ ).
- A **reset or clear input**, instantly sets the output to a standard condition regardless of the current state or clock level.
- Can be confused a little by pulses in quick succession.

INPUTS			OUTPUTS	
CLEAR	A	B	Q	$\overline{Q}$
L	X	X	L	H
X	H	X	L	H
X	X	L	L	H
H	L	↑	⌋	⌌
H	↓	H	⌋	⌌
↑	L	H	⌋	⌌

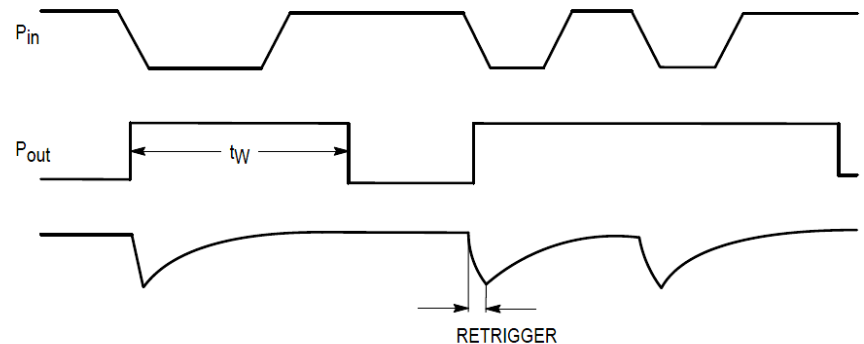

# One-shot: 74LS123


## Characteristics:

- 2 clock inputs triggered by either a **rising edge** or a **falling edge**.
- 2 outputs ( $Q$  &  $\overline{Q}$ ).
- A **reset or clear input**, instantly sets the output to a standard condition regardless of the current state or clock level.
- Can be confused a little by pulses in quick succession.


INPUTS			OUTPUTS	
CLEAR	A	B	Q	$\overline{Q}$
L	X	X	L	H
X	H	X	L	H
X	X	L	L	H
H	L	↑	⌋	⌌
H	↓	H	⌋	⌌
↑	L	H	⌋	⌌

armed


output pulse

 

# 74LS123 usage

 

INPUTS			OUTPUTS	
CLEAR	A	B	Q	$\bar{Q}$
L	X	X	L	H
X	H	X	L	H
X	X	L	L	H
H	L	↑	⌊	⌋
H	↓	H	⌊	⌋
↑	L	H	⌊	⌋

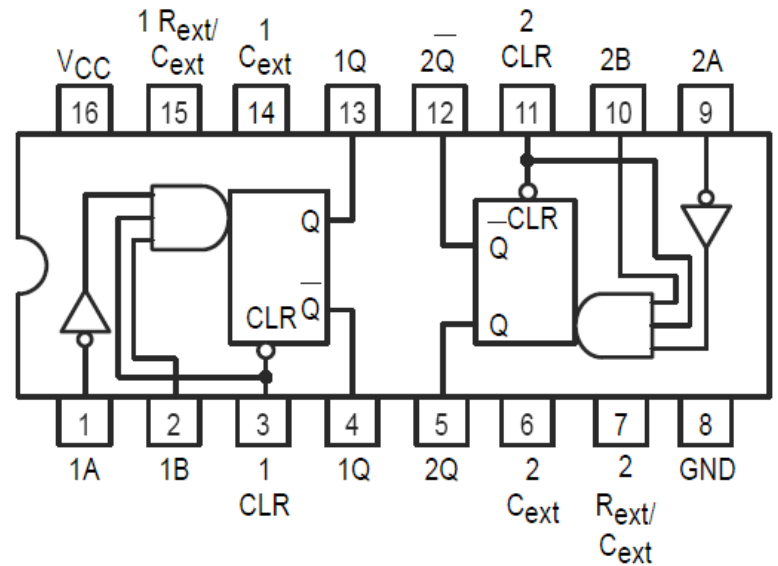

# Pulse Delay Generator

- A **single one-shot** will produce a **variable delay** pulse.
- **2 one-shots** can be combined to produce a pulse of **variable duration/width** produced at **variable delay** after a trigger.
  - Pulse Delay Generator ... very useful in a research lab.


# Pulse Delay Generator

- A **single one-shot** will produce a **variable delay** pulse.
- **2 one-shots** can be combined to produce a pulse of **variable duration/width** produced at **variable delay** after a trigger.
  - Pulse Delay Generator ... very useful in a research lab.




[image from [www.thinksrs.com](http://www.thinksrs.com)]

# Setting the Pulse Width

 

$$t_W = K R_{ext} C_{ext}$$

with

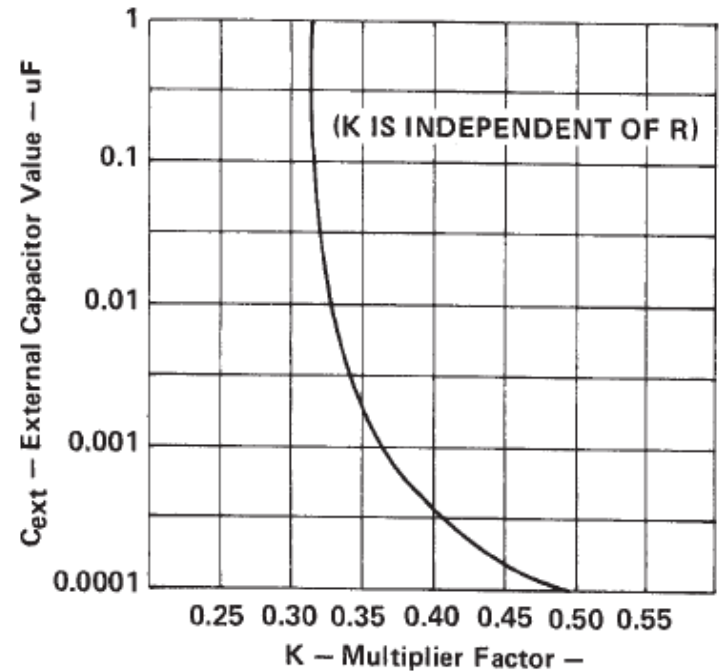


# The Problem with One-Shots

1. One-shots are very useful in a research laboratory as pulse delay generators.
2. **One-shots should be avoided in regular circuitry, because**
  - They are useful in **asynchronous circuits** for avoiding glitches and signal races ...
  - It's very easy to put them all over your asynchronous circuit with all the pulse timing set just right. It is very hard to figure out how the circuit works just by looking at it (or even a circuit diagram).
  - The **pulse width depends on temperature** (R, C, and chip).
  - The **pulse width depends on supply voltage**.
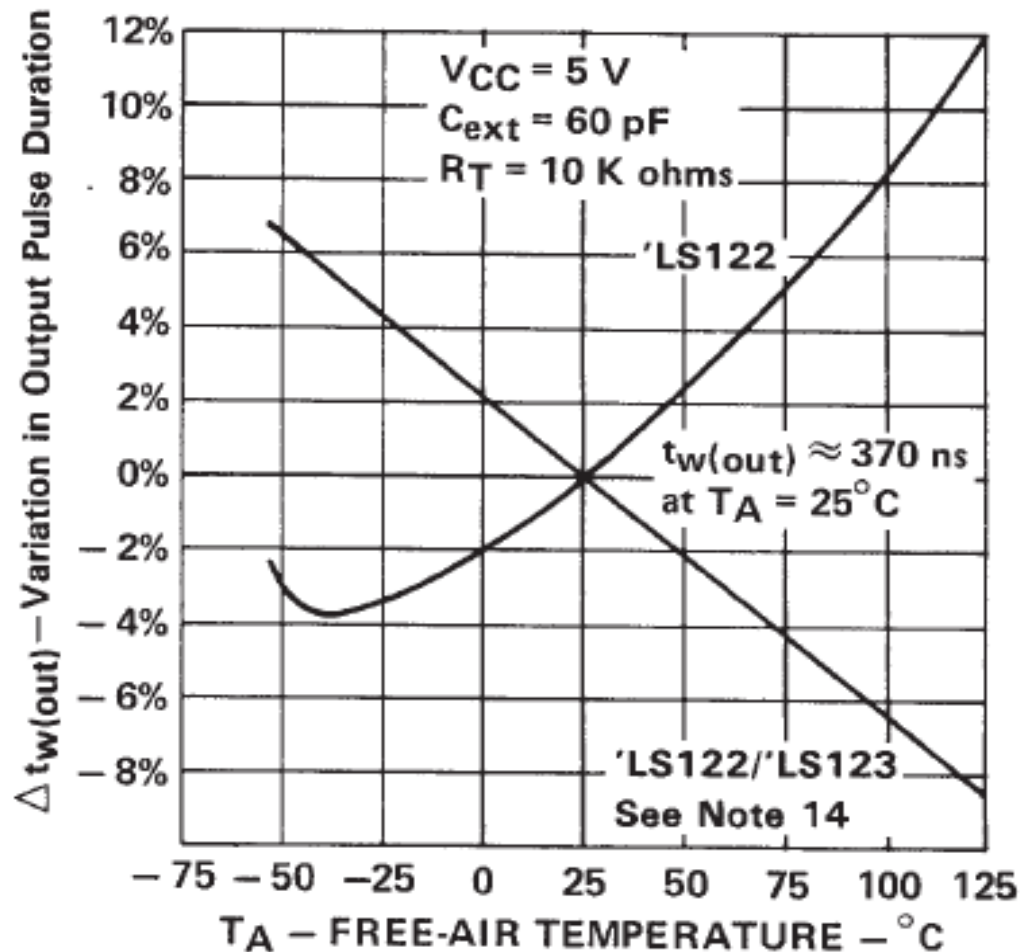
# Pulse Width vs. Temperature


VARIATION IN OUTPUT PULSE DURATION  
VS  
FREE-AIR TEMPERATURE




 
# Pulse Width vs. Supply Voltage


VARIATION IN OUTPUT PULSE DURATION  
vs  
SUPPLY VOLTAGE



# Counters ... 1 2 3 4

1. Frequency dividers.
2. Counters in Verilog.
3. Ripple counter (next week).
4. Synchronous counter (next week).

# JK-type flip-flop



 


Logic table  
for clock falling edge

J	K	$Q_{n+1}$
0	0	$Q_n$
1	0	0
0	1	1
1	1	$\overline{Q_n}$


JK-type flip-flops are used in counters.

# T-type flip-flop

   

JK Logic table

J	K	$Q_{n+1}$
0	0	$Q_n$
1	0	0
0	1	1
1	1	$\bar{Q}_n$

 

T Logic table  
(clock falling edge)

T	$Q_{n+1}$
0	$Q_n$
1	$\bar{Q}_n$

T-type flip-flops are used in counters.

# Counters in Verilog

Counters in Verilog are easy → just use `always` (synchronous).

→ and a self-referential “add 1” assignment.

```
1 module counter_v3(input1,output1);           // module for an 8-bit synchronous counter
2     input input1;                           // 1-bit input
3     output reg [7:0] output1;               // 8-bit output register
4
5     always@ (posedge input1)                 // synchronous loop, clocked on input1 rising edge
6     begin
7
8         output1 <= output1 + 1;             // self-referential add+1 assignment.
9     // output1 = output1 + 8'b00000001;    could have used this instruction line instead.
10
11     end
12
13 endmodule
14
```

# Initializing a register

```
1  module counter_v3(input1,output1);           // module for an 8-bit synchronous counter
2      input input1;                             // 1-bit input
3      output reg [7:0] output1;                 // 8-bit output register
4
5      initial                                     // this block initializes the output register
6      begin                                       // to zero.
7          output1 = 8'b00000000;
8      end
9
10     always@ (posedge input1)                   // synchronous loop, clocked on input1 rising edge
11     begin
12
13         output1 <= output1 + 1;                // self-referential add+1 assignment.
14         // output1 = output1 + 8'b000000001;  could have used this instruction line instead.
15
16     end
17
18 endmodule
19 |
```

# Initializing a register

```
1 module counter_v3(input1,output1); // module for an 8-bit synchronous counter
2     input input1; // 1-bit input
3     output reg [7:0] output1; // 8-bit output register
4
5     initial // this block initializes the output register
6     begin // to zero.
7         output1 = 8'b00000000;
8     end
9
10    always@ (posedge input1) // synchronous loop, clocked on input1 rising edge
11    begin
12
13        output1 <= output1 + 1; // self-referential add+1 assignment.
14        // output1 = output1 + 8'b00000001; could have used this instruction line instead.
15
16    end
17
18 endmodule
19 |
```

This section initializes the register to zero.  
("initial" is only for simulation !)

# “if” statement

```
1 module counter_v3(input1,output1, output2);    // module for an 8-bit synchronous counter
2     input input1;                               // 1-bit input
3     output reg [7:0] output1;                   // 8-bit output register
4     output reg [2:0] output2;                   // 3-bit output register
5
6     initial                                     // this block initializes the output registers
7     begin                                     // to zero.
8         output1 = 8'b00000000;
9         output2 = 3'b000;
10    end
11
12    always@ (posedge input1)                   // synchronous loop, clocked on input1 rising edge
13    begin
14
15        output1 <= output1 + 1;                // self-referential add+1 assignment.
16        // output1 = output1 + 8'b00000001;    could have used this instruction line instead.
17
18        if (output1 <= 8'b11100111)
19        begin
20            output2 = 3'b000;    // output2 stays at zero for output1 <= 231.
21        end
22    else
23    begin
24        output2 = output2 + 1;    // output2 starts counting for output1 > 231.
25    end
26
27    end
28
29 endmodule
```



# Variable Registers

```
1  module counter_v3(input1,output1, output2);    // module for an 8-bit synchronous counter
2      input input1;                            // 1-bit input
3      output reg [7:0] output1;                // 8-bit output register
4      output reg [2:0] output2;                // 3-bit output register
5      reg [1:0] temp;                          // "temp" variable 2-bit register.
6
7      initial                                  // this block initializes the output registers
8      begin                                    // to zero.
9          output1 = 8'b00000000;
10         output2 = 3'b000;
11         temp = 2'b00;
12     end
13
14     always@ (posedge input1)                 // synchronous loop, clocked on input1 rising edge
15     begin
16
17         output1 <= output1 + 1;              // self-referential add+1 assignment.
18
19         temp <= temp + 1;                    // temp is used as counter.
20
21         if (output1 <= 8'b11100111)
22         begin
23             output2 = 3'b000 + temp;        // output2 counts continuously to 2 for output1 <= 231.
24         end
25     else
26     begin
27         output2 = output2 + 1 ; // output2 starts counting for output1 > 231.
28     end
29
30     end
31
32 endmodule
```

Recommendation: check the Technology Map Viewer after compiling.

# The “function” command (I)

```
1 // Module translates 2-bit inputs to an 8-bit output code
2 module Input_to_Output_converter(input_register1, input_register2, input_register3,
3     output_register1, output_register2, output_register3);
4     input [1:0] input_register1;
5     input [1:0] input_register2;
6     input [1:0] input_register3;
7     output reg [7:0] output_register1;
8     output reg [7:0] output_register2;
9     output reg [7:0] output_register3;
10
11     always
12     begin
13
14         // 1st output
15         output_register1 = output_8bit(input_register1);
16
17         // 2nd output
18         output_register2 = output_8bit(input_register2);
19
20         // 3rd output
21         output_register3 = output_8bit(input_register3);
22
23     end
24
```

# The “function” command (II)

```
24 |  
25 // This function defines the output codes given a 2-bit input  
26 function [7:0] output_8bit;  
27     input [1:0] input_number_2bit;  
28     begin  
29         output_8bit = 7'b1111111;  
30  
31         if (input_number_2bit == 4'b00)  
32             output_8bit = 7'b1111111;  
33  
34         if (input_number_2bit == 4'b01)  
35             output_8bit = 7'b1001011;  
36  
37         if (input_number_2bit == 4'b10)  
38             output_8bit = 7'b1000000;  
39  
40         if (input_number_2bit == 4'b11)  
41             output_8bit = 7'b0000000;  
42  
43  
44         end  
45  
46     endfunction  
47  
48 endmodule  
49  
50
```