

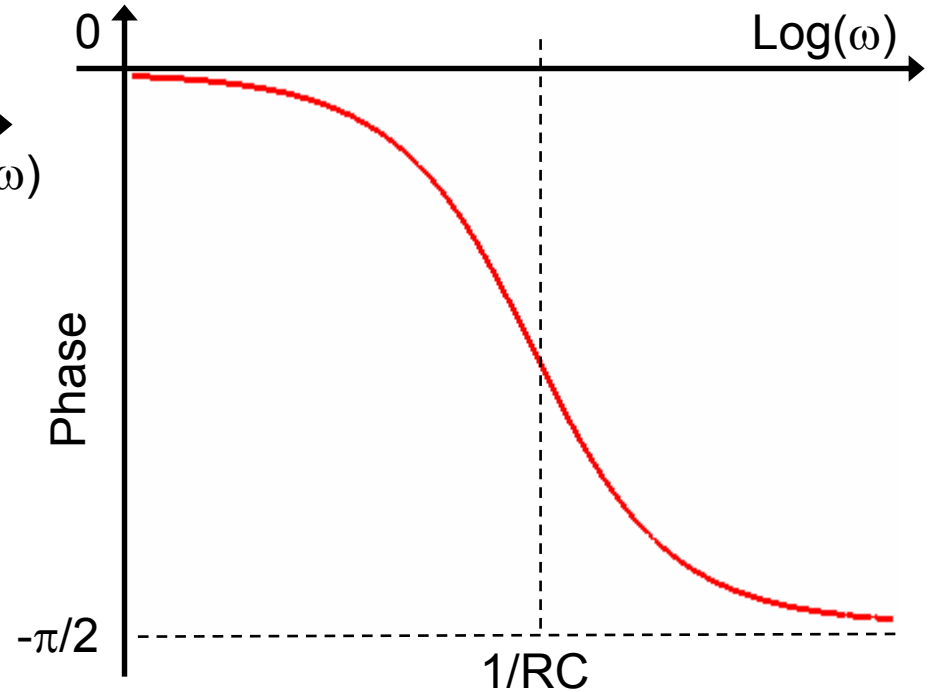
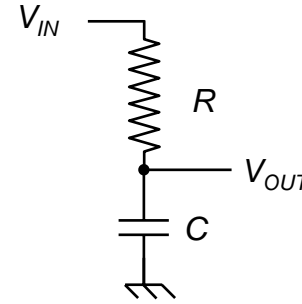


Low-Pass RC Filter

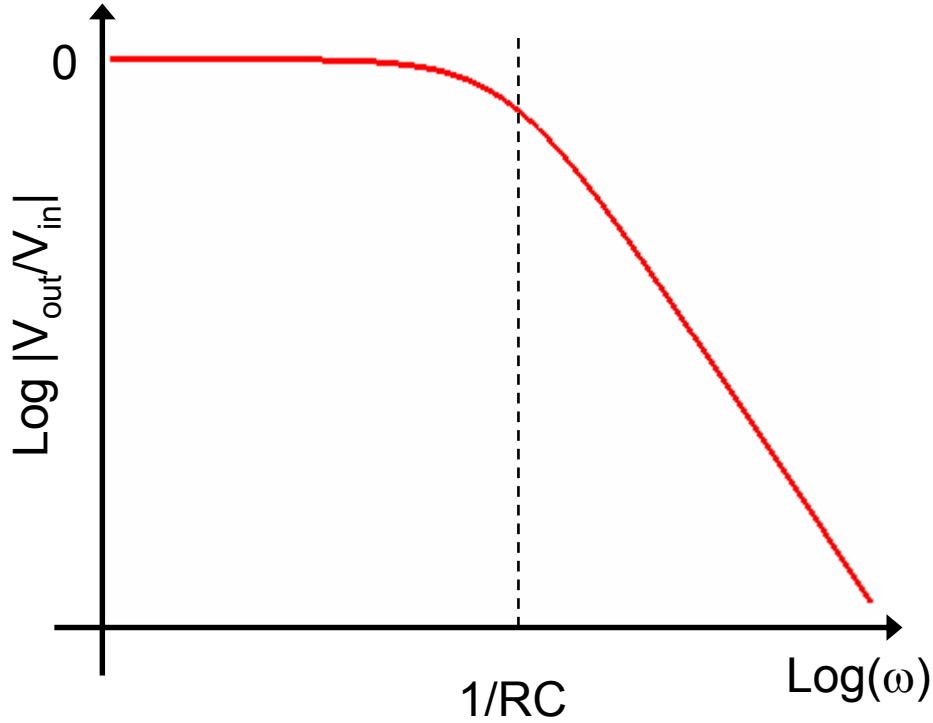


RC integrator

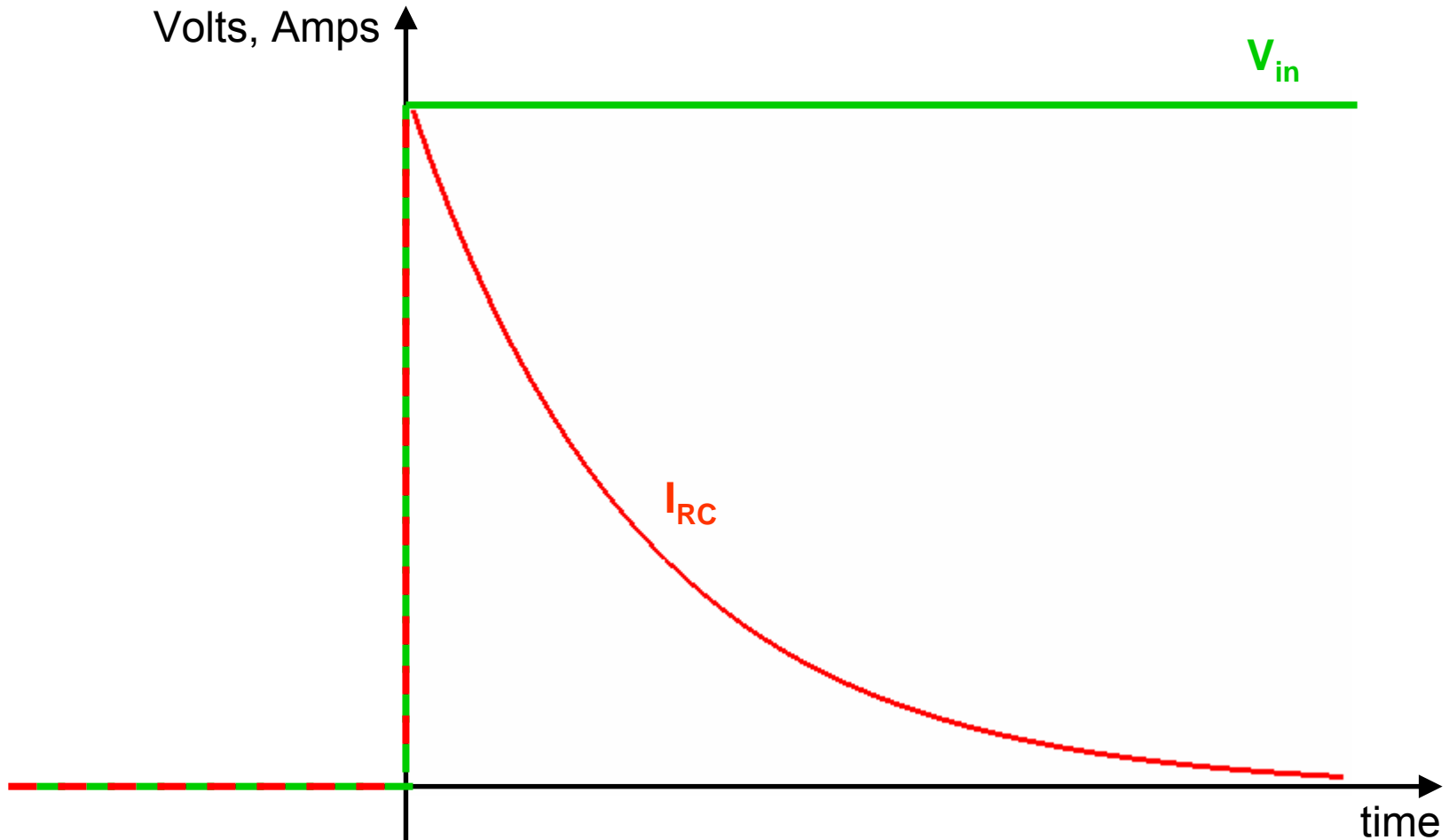For frequencies above $\omega=1/RC$, the RC low-pass filter integrates the current on the capacitor.






RC integrator

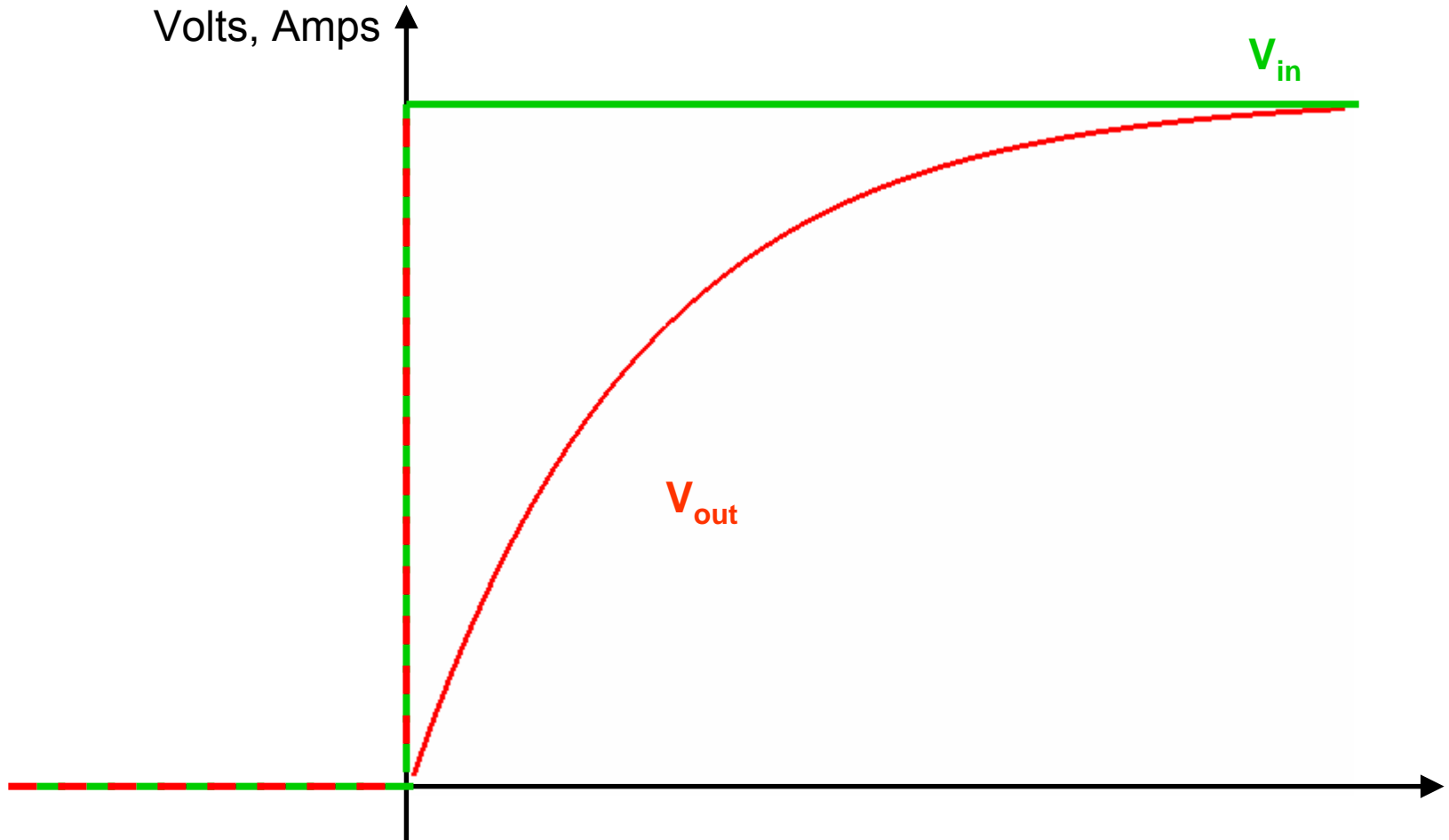For frequencies above $\omega=1/RC$, the RC low-pass filter integrates the current on the capacitor.




High-Pass RC Filter

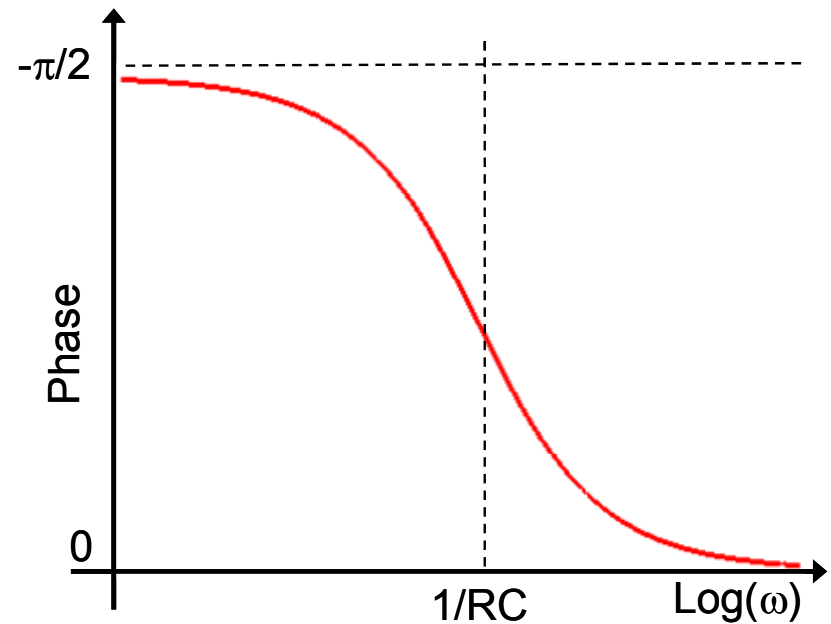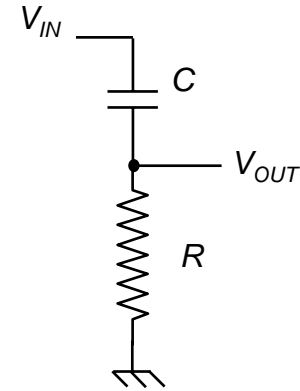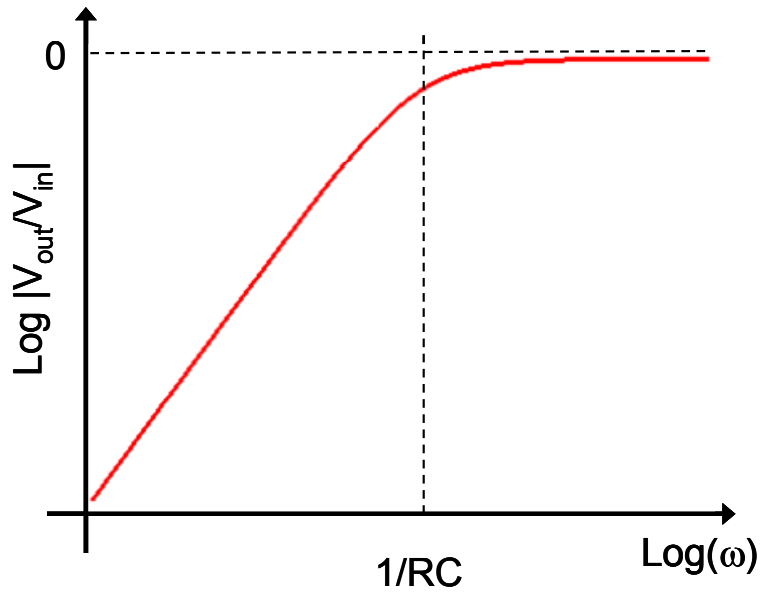


RC Differentiator

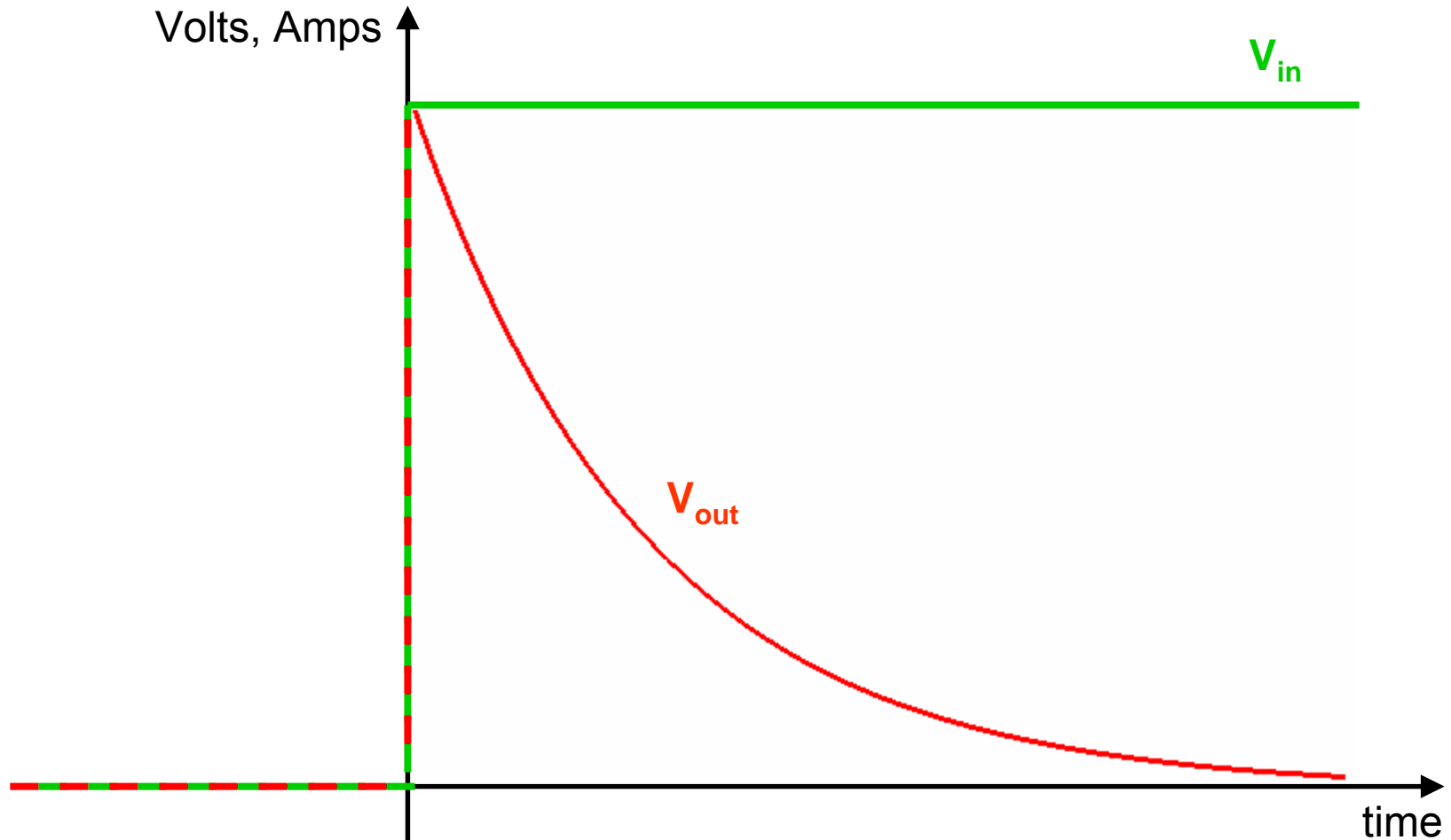For frequencies below $\omega=1/RC$, the RC high-pass filters differentiates the voltage on the resistor.



Capacitors ...

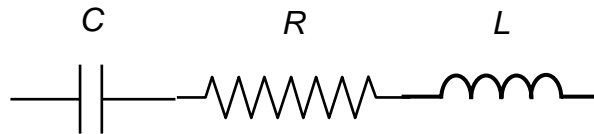- Capacitors perform better than inductors, and they're cheaper to make.
- Nevertheless, capacitors behave like inductors at high frequencies.
 - wire leads on capacitor have an inductance
 - Maxwell's equations ($dE/dt \rightarrow B$)
 - $Z_{inductor} = i\omega L$
- Circuit diagram for a real capacitor:



Capacitors Spec Sheet


Type FCA Acrylic Surface Mount Film Capacitors

Acrylic Stacked Metallized Film Capacitors for Filtering and Noise Attenuation

Type FCA acrylic film chips are non-inductive stacked metallized film capacitors which feature large capacitance values in standard surface mount case sizes.

Highlights

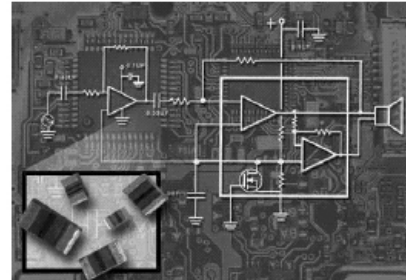- ◆ Smallest film chips
- ◆ No piezoelectric effect
- ◆ Non-polarized, non-magnetic
- ◆ Low ESR
- ◆ 1.0 $\mu\text{F}/10\text{V}$ in 1206 case



Filtering • Decoupling • Noise Attenuation • Distortion Free Audio

Type FCA acrylic film capacitors offer high capacitance values in standard surface mount case sizes. They excel in attenuating DC power bus noise, and as ripple filters in dc to dc power conversion circuits. As coupling capacitors in audio circuits, they yield distortion free sound and better high frequency filtering. The 1.0 μF 10 Vdc rating offers a film capacitor that is a direct replacement for tantalum "A" case capacitors. The nonpolar FCA capacitor has

lower ESR and lower DCL than an equivalent tantalum capacitor, and in high frequency applications it takes a tantalum capacitor with ten times the capacitance to perform as well as the FCA capacitor.

The capacitor is constructed of noninductive stacked layers of metallized acrylic resin film with lead free solder (Sn/Ag/Cu) plated copper alloy terminals.

Specifications

Capacitance Range:	0.10 μF to 1.0 μF
Capacitance Tolerance:	$\pm 20\%$ @ 1 kHz and +20 °C
Rated Voltage:	16 Vdc [1.0 μF in 1206 case, 10 Vdc]
AC Voltage Rating:	12 Vrms
Operating Temperature Range:	-40 °C to +85 °C
Dissipation Factor:	0.015 @ 1 kHz and +20 °C
Dielectric Strength:	175% of rated voltage for 5 seconds
Insulation Resistance (IR):	After 1 minute @10 Vdc; +20 °C IR >1000 M Ω (C \leq 0.33 μF) IR > 300 M Ω · μF (C >0.33 μF)
Resistance to Soldering:	The capacitor can withstand being heated in an oven at 235 °C for 200 seconds

Capacitors Spec Sheet

Type FCA Acrylic Surface Mount Film Capacitors

Specifications

Moisture Resistance:

After 500 hours with rated voltage applied at +40 °C and 90 to 95% RH, the capacitor will meet the following limits:

$\Delta C = +20/-3\%$ of the initial measured value

DF $\leq 2.25\%$ (at 1 kHz)

IR > 100M Ω (C $\leq 0.33 \mu F$)

IR > 30M $\Omega \cdot \mu F$ (C > 0.33 μF)

Dielectric Strength: Capacitor will withstand 130% of the rated voltage for 1 minute.

Life Test:

Apply 125% of the rated DC working voltage at 85 °C for 1000 hours, and then stabilize them to +20 °C.

Capacitors will meet the following limits:

C = +7%/-20% of the initial measured value

DF $\leq 1.65\%$ (at 1 kHz)


IR > 300M Ω (C $\leq 0.33 \mu F$)

IR > 100M $\Omega \cdot \mu F$ (C > 0.33 μF)

Ratings

Capacitance (μF)	Voltage Rating (Vdc)	Catalog Part Number	dV/dt (V/ μs)	Maximum Current (Arms)						
				10kHz	20kHz	50kHz	100kHz	200kHz	500kHz	1MHz
1.00	10	FCA1208A105M-H3	3	0.80	0.76	1.05	1.220	1.35	1.43	1.43
0.10	16	FCA0806C104M-J2	19	0.15	0.21	0.30	0.375	0.46	0.56	0.65
0.15	16	FCA1208C154M-H1	15	0.21	0.28	0.37	0.450	0.54	0.62	0.68
0.22	16	FCA1208C224M-H1	13	0.25	0.33	0.46	0.560	0.66	0.76	0.84
0.33	16	FCA1208C334M-H2	10	0.35	0.45	0.61	0.740	0.84	0.94	1.00
0.47	16	FCA1208C474M-H3	7	0.39	0.52	0.71	0.860	1.00	1.10	1.17
0.68	16	FCA1208C684M-H3	5	0.48	0.625	0.85	1.040	1.19	1.31	1.34
1.00	16	FCA1210C105M-G2	3	0.80	0.78	1.05	1.250	1.38	1.46	1.46

Outline Drawing

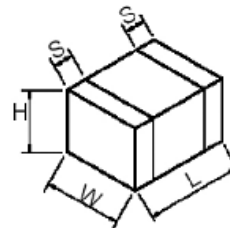




Outline Dimensions

Part Number Suffix	Case Code	Inches				Millimeters			
		L (± 0.008 in.)	W (± 0.008 in.)	H (± 0.008 in.)	S (± 0.012 in.)	L (± 0.2 mm)	W (± 0.2 mm)	H (± 0.2 mm)	S (± 0.3 mm)
J2	0805	0.079	0.049	0.039	0.018	2.0	1.25	1.0	0.45
H1	1206	0.126	0.063	0.032	0.026	3.2	1.60	0.8	0.65
H2	1206	0.126	0.063	0.039	0.026	3.2	1.60	1.0	0.65
H3	1206	0.126	0.063	0.055	0.026	3.2	1.60	1.4	0.65
G2	1210	0.126	0.098	0.055	0.026	3.2	2.50	1.4	0.65




Capacitors Spec Sheet

Type FCA Acrylic Surface Mount Film Capacitors

Temperature Characteristics

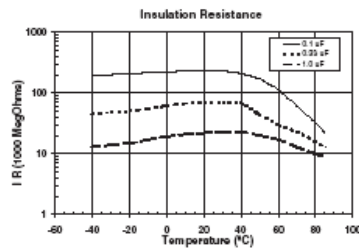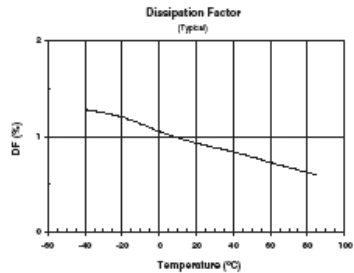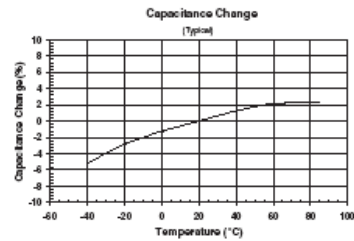




Frequency Characteristics

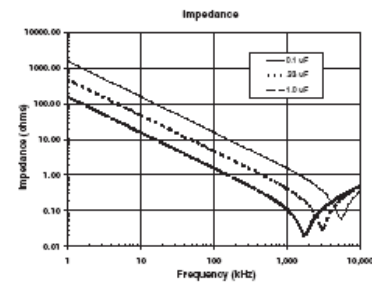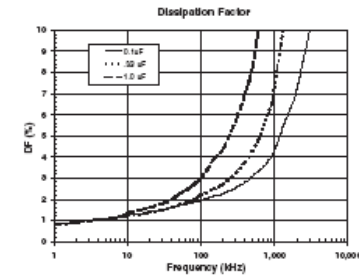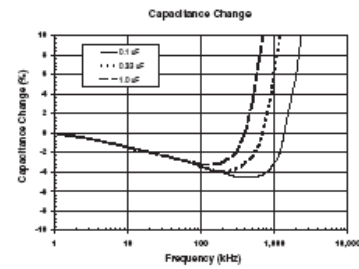




Capacitors Spec Sheet

Type FCA Acrylic Surface Mount Film Capacitors


Temperature Characteristics

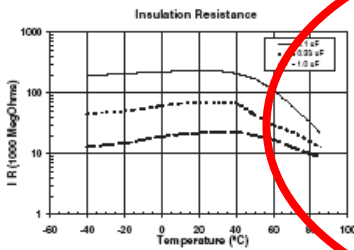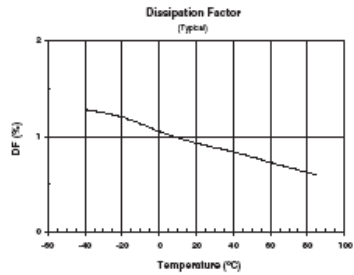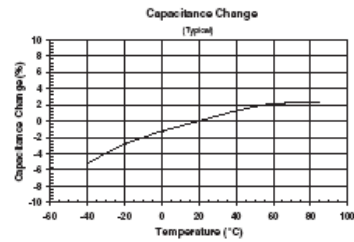


Frequency Characteristics

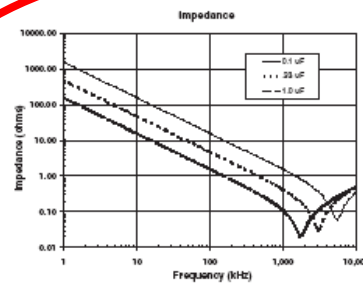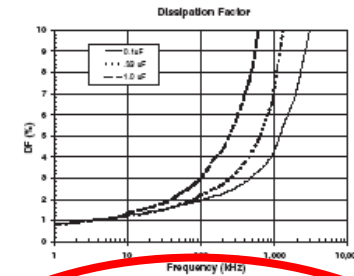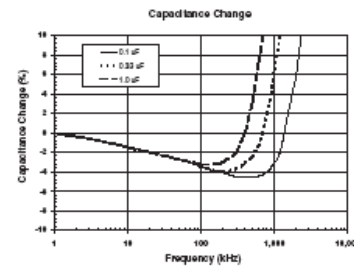


Capacitors Spec Sheet

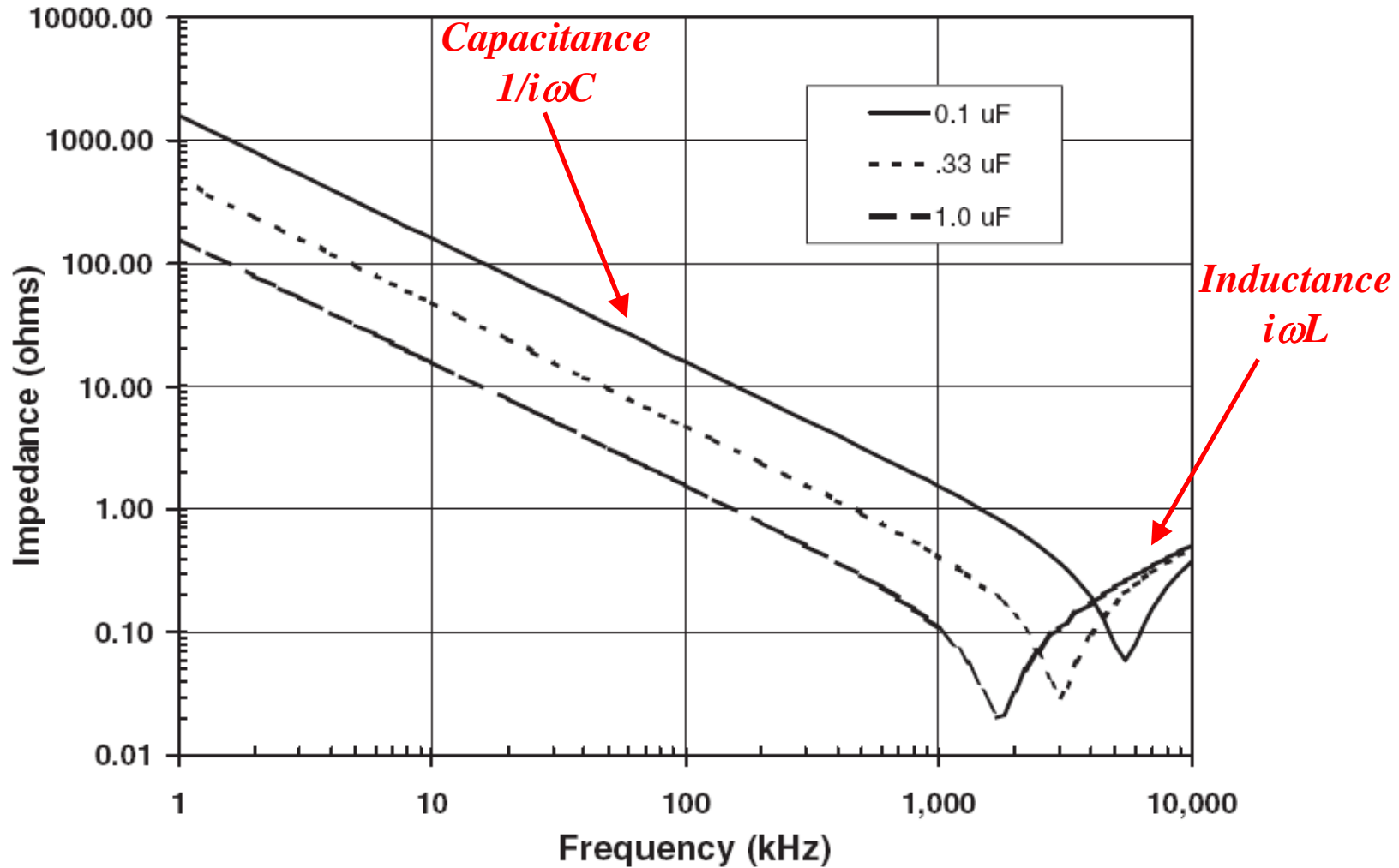


RC Filter Combinations II

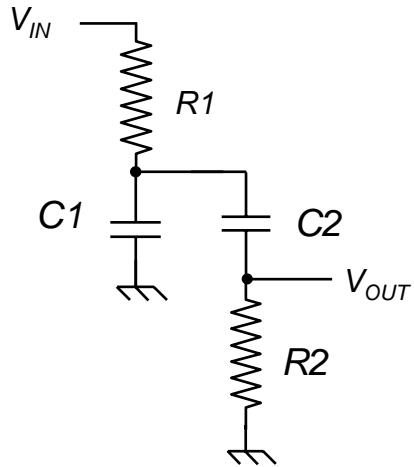



Pass-band filter

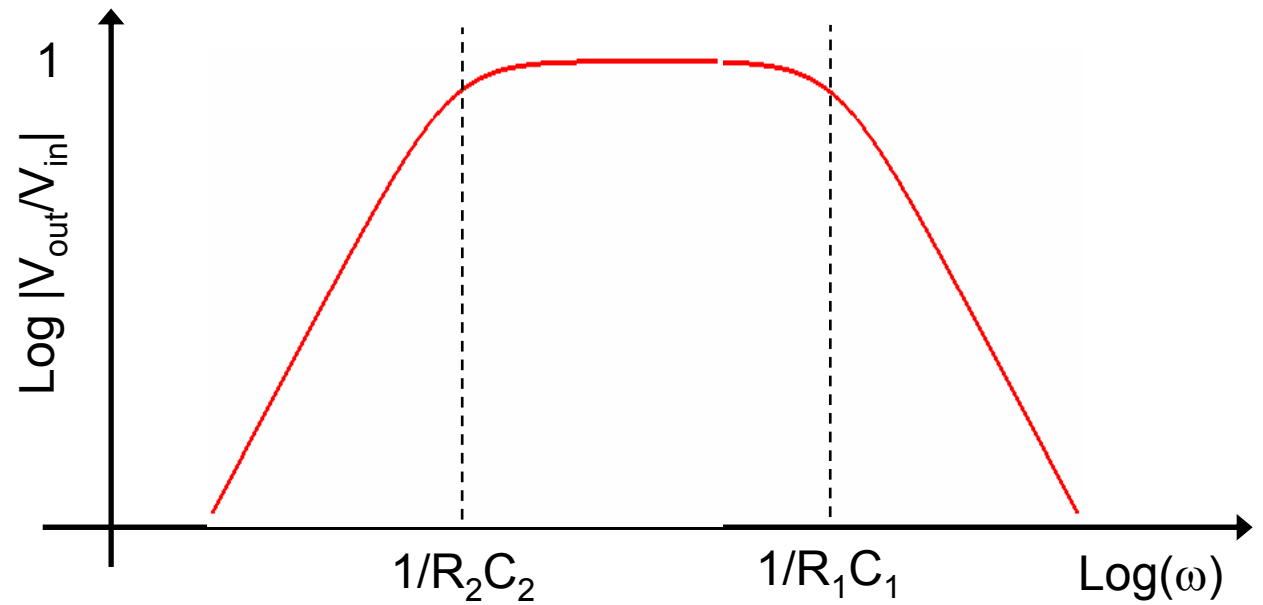


RC Filter Combinations I

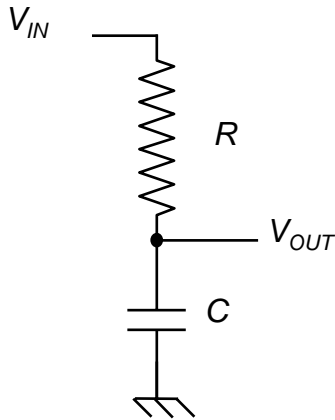

- 20 dB/decade

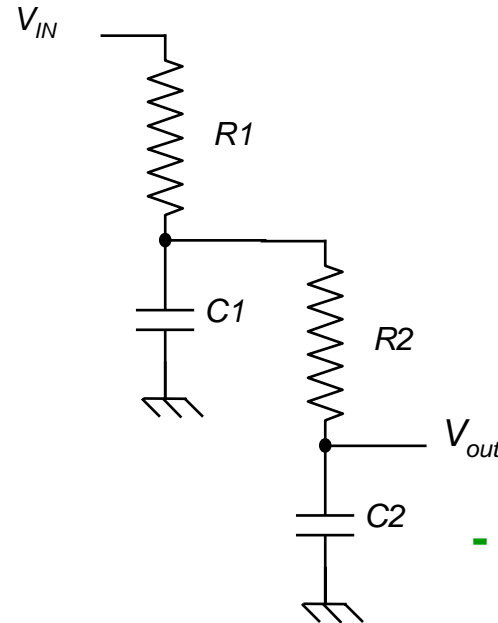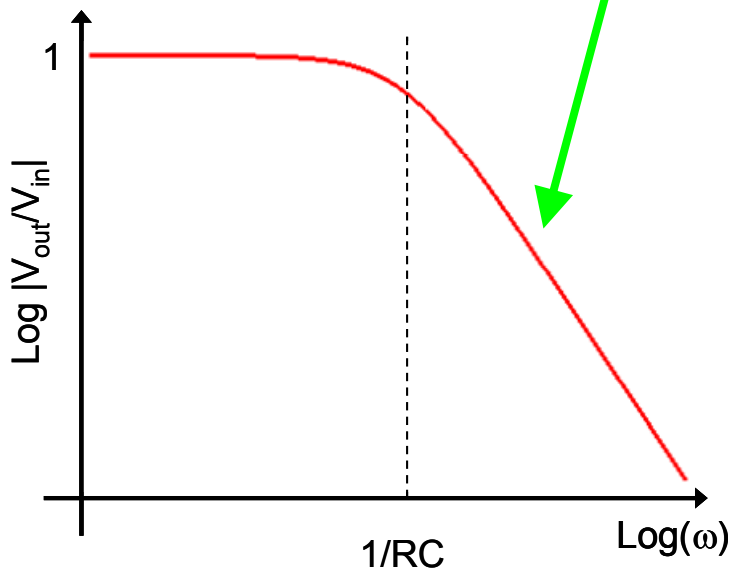



- 40 dB/decade

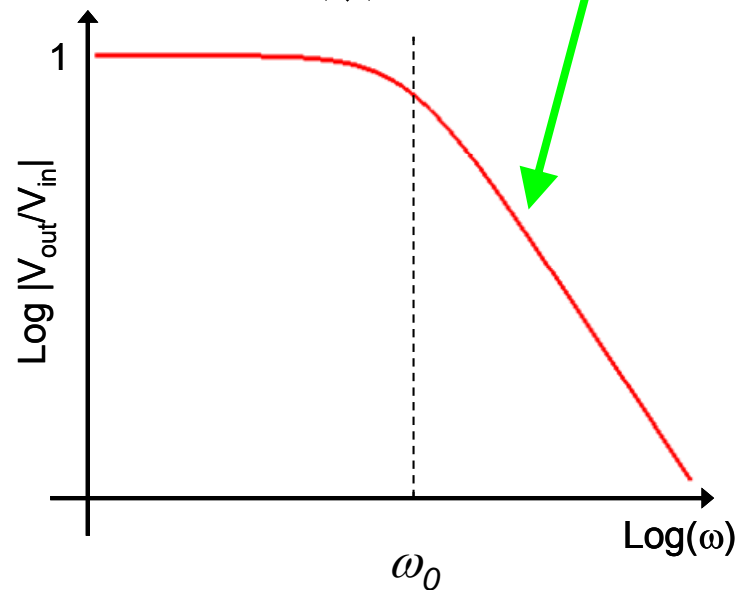

LC Filters

- LC filters trade off smoothness and regularity (especially in the phase) for **very sharp cut-offs**.
- They don't have to change the effective source **impedance** of a signal.
- They are used for **high frequency** applications.
- They are much **harder** to design.

Butterworth Filter

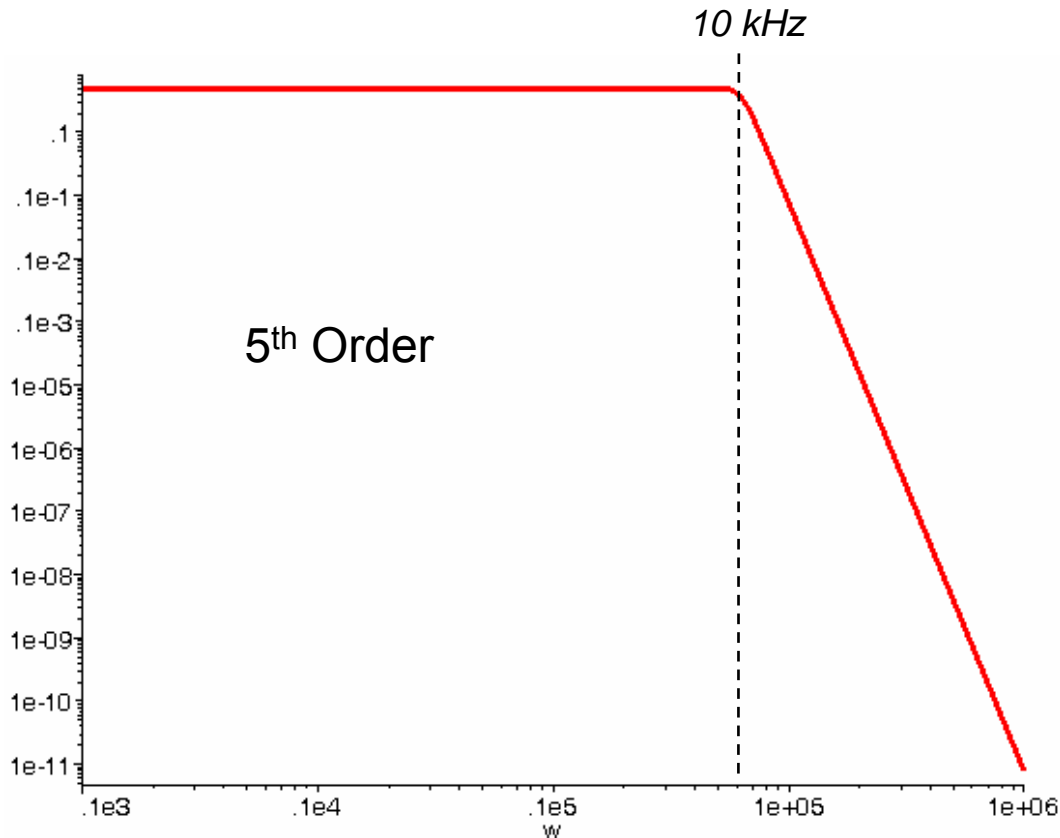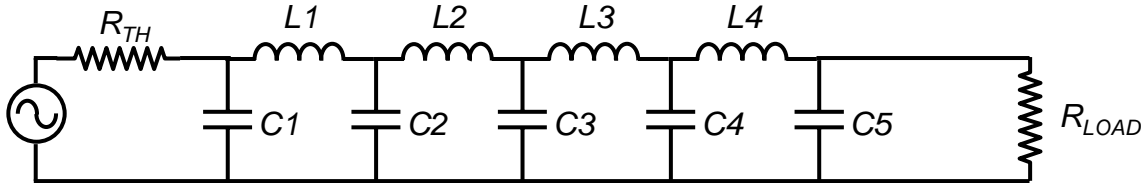



$$\begin{aligned} C1 &= C5 = 0.6946 \mu\text{F} \\ C2 &= C4 = 3.0642 \mu\text{F} \\ C3 &= 4 \mu\text{F} \end{aligned}$$

$$\begin{aligned} L1 &= L4 = 5 \text{ mH} \\ L2 &= L3 = 9.397 \text{ mH} \end{aligned}$$

Butterworth filters have very flat pass-bands

Use Maple or another program to design

Chebyshev Filter

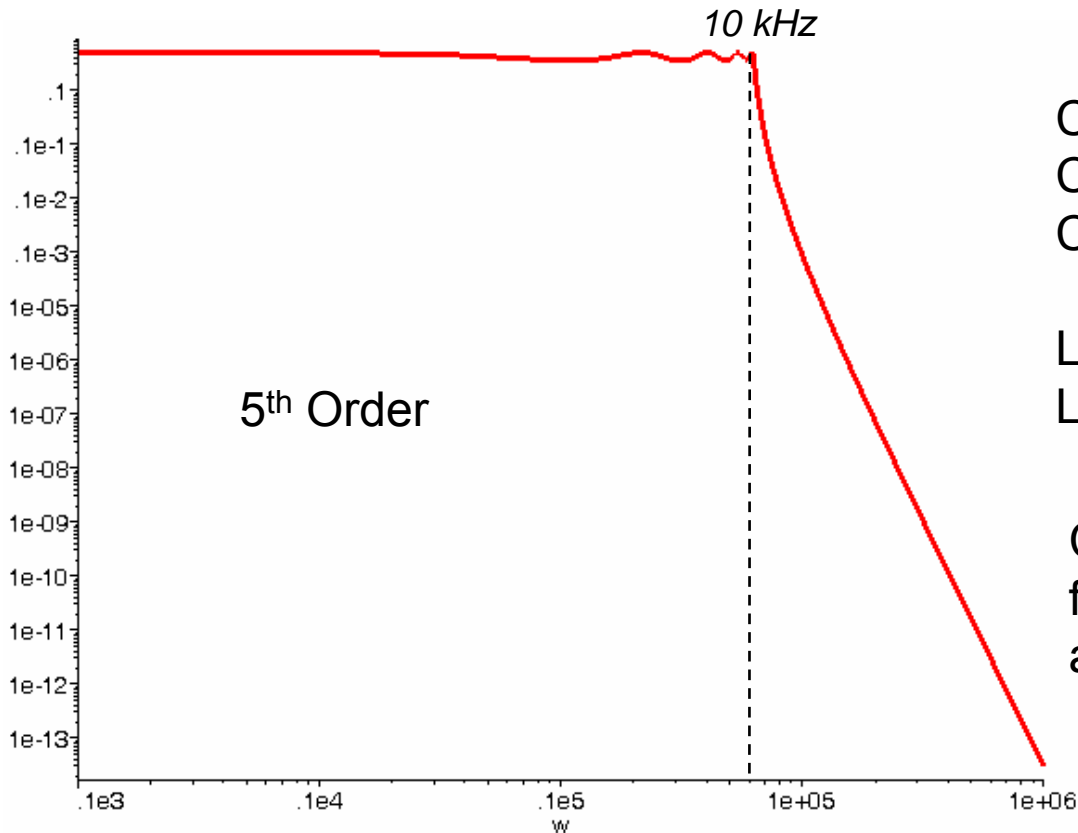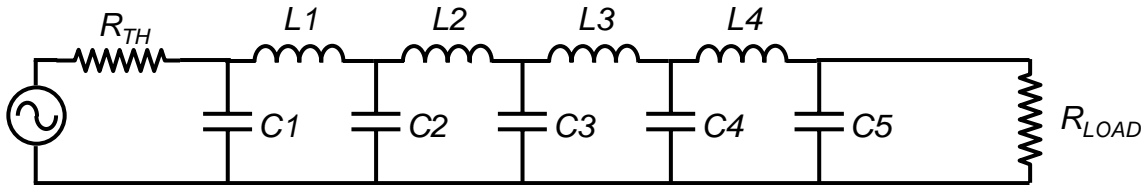

$$\begin{aligned}C1 &= C5 = 1.125 \mu\text{F} \\C2 &= C4 = 1.486 \mu\text{F} \\C3 &= 1.505 \mu\text{F}\end{aligned}$$

$$\begin{aligned}L1 &= L4 = 0.617 \text{ mH} \\L2 &= L3 = 0.646 \text{ mH}\end{aligned}$$

Chebyshev filters have very flat sharp cut-off knees, but are not very flat in pass-band.

Use Maple or another program to design

Transmission Lines


They're the wires you use to connect different components (resistors on a breadboard ... function generator to oscilloscope).

3 Types: ➤ Wires:

- Simple and Cheap.
- Almost no interference suppression.
- Radiate and receive like an antenna.
- To be avoided.

➤ Twisted Pairs:

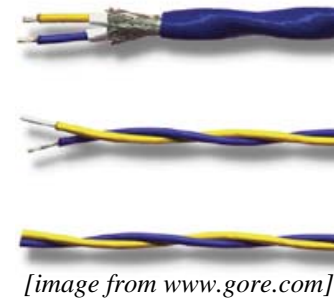- Decent interference suppression.
- do not radiate much.
- Max analog ~ 250 kHz to 1 MHz.
- Max digital ~ 100 MHz.
- Easy to make.



➤ Coaxial Cables

- Excellent performance up to 1 GHz.
- No external interference.
- Do not radiate.
- typical impedance 50 Ω .

