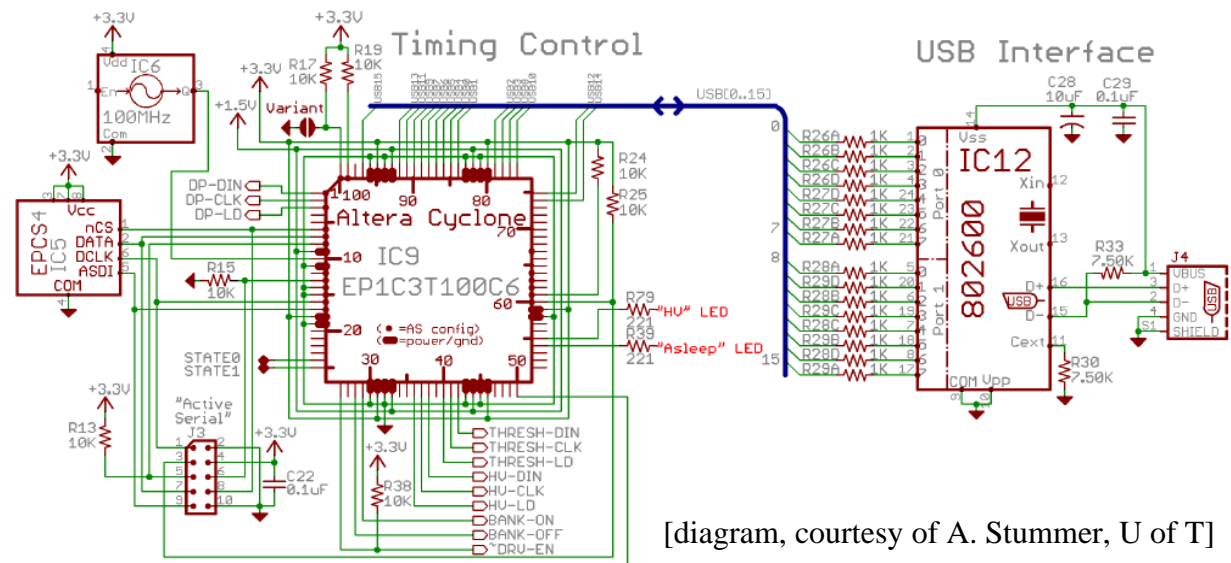


Physics 351: Electronics II

Introduction to Digital Circuits

Prerequisites: PHYS 252.

Introduction to digital electronics: Theory, design, and application of digital circuits ... or how to understand and make circuits like these:



Small print: If you don't have any experience with analog electronics you should talk to me after class.

Instructors

Prof. Seth Aubin

Office: room 333 (3rd floor back hall), tel: 1-3545

Lab: room 15 (basement next to machine shop), tel: 1-3532

e-mail: saaubi@wm.edu

web: <http://www.physics.wm.edu/~saubin/index.html>

Austin Ziltz

Office: rooms 243, tel: 1-3570

e-mail: arziltz@wm.edu

Office hours:

Monday: 3-4 pm (Ziltz, room 243)

Tuesday: 4-5 pm (Aubin, room 333)

Course Objectives

Primary: Design and test both basic and advanced digital circuits for *digital logic*, *signal acquisition*, and *digital signal processing*.

Secondary: Learn experimental research skills.



Covered topics:

- Binary numbers, logic gates, and Karnaugh maps.
- Memory, flip-flops, and clocked latches.
- Clocks, timing, and one-shots.
- Counters, registers, and state machines.
- Analog-to-Digital Converters (ADC) and Digital-to-Analog Converters (DAC).
- Optical and magnetic isolation.
- **Field Programmable Gate Arrays (FPGA).**
- Verilog language FPGA programming.
- **Digital Signal Processing (DSP).**
- Microprocessors.

FPGAs for Physicists

Field Programmable Gate Array (FPGA) chips for physicists

- Contain 2,000-100,000 logic gates + memory.
- Rerogrammable via a computer (Quartus II v7-8).
- Stand alone circuitry (with flash memory).
- Parallel processing.
- ***Useful for complex circuits and Digital Signal Processing (DSP).***



Please download and install Quartus II WebEdition onto your laptop.

Please request a WebEdition license from Altera Inc.

(see course webpage for the necessary internet links)

Note: Quartus II is available on lab computers, in room 134 (Learning Center) of Swem library, and Morton 240 (24/7)

DSP design project (I)

A central component of the course is an FPGA-based digital signal processing (DSP) project. The general guidelines for the projects are:

- Teams of 2-3 students (depends on lab section distribution).
- Each team has a budget of \$250 USD.
- All teams have the same project.
- This section of the course is a design and construction competition.

The purpose of the one month team project is to help you develop practical circuit design skills, as well as the following more general research skills:

- Complex device design.
- Project budgeting.
- Formal project proposal writing.
- Finding, selecting, and purchasing device components.
- Device construction.
- Troubleshooting and debugging.
- Oral and web presentations of the device.

DSP design project (II)

2 choices for the design project:

1. Phase coherent, dual output **DSP FUNCTION GENERATOR**

- 2 analog outputs.
- FPGA core.
- External clock option.
- Comments: more DSP, easier analog.



2. Digital **VOICE RECORDER** with playback

- 1 analog input (i.e. microphone).
- 1 analog output (i.e. speaker).
- FPGA core.
- Comments: more memory handling, more involved analog.



DSP design project (III)

- Easier project than last year, with more project time scheduled.
- The project will be based on an FPGA.
- The specific project requirements will be announced next week.
- The project is the most important part of the course.
- It will be graded according to the following weights:

Formal project proposal	10%
Device construction	15%
Device performance	20%
Oral presentation of device.	5%
Web presentation of device	5%
Project lab book and wiki	5%
Total	60%

Evaluation

Notebooks/Reports:	30%
Quizzes/Participation:	10%
<u>DSP project:</u>	<u>60%</u>
Total =	100%

Note: There is no final exam for the course

Due Dates

➤ Lab books

In addition to lab notes, the lab books should include all design exercises.

Lab books are due by 5pm 2 days after lab & will be returned by the next lab period:

- Thursdays for the Tuesday section
- Fridays for the Wednesday section

➤ Reports

- Reports are due on monday the following week.
- Instructor will indicate for which labs a report is due.
- You can expect 1-2 reports for the semester.
- Lab books should not be turned in when lab report is due.
- Important measured numbers should include an estimated uncertainty.

Schedule (I)

Week 0: 8/25-27

NO CLASS

Week 1: 9/1-3

Digital Logic

Class & lab: Binary numbers, logic gates, Karnaugh maps.

Week 2: 9/8-10

Introduction to FPGAs

Class & lab: FPGAs, Verilog programming language, applications.

Week 3: 9/15-17

Memory

Class & lab: Memory, flip-flops.

Week 4: 9/22-24

Timing

Class & lab: Clocks, timing, one-shots, and counters.

Week 5: 9/29 -10/1

Counters and Registers

Class & lab: Counters II and registers.

Week 6: 10/6-8

Analog-Digital Interfacing

Class & lab: Analog-to-digital converters, digital-to-analog converters.

Project: Formal project proposals are due October 10, 2008.

Schedule (II)

Week 6.5: 10/15 Wednesday lab group jumps one week ahead
Class: No class; Lab: Project; project funds are released.

Week 6: 10/20-22 **State Machines and/or Microprocessors**
Class & lab: State machines and sequencing.

Week 8: 10/27-29 **Project week 1**
Class: Surface mount soldering review and machine shop training.
Project: Project construction begins.

Week 9: 11/3-5 **Project week 2**
Class: Digital signal processing.
Lab & Project: Project construction continues.

Week 10: 11/10-12 **Project week 3**
Class: Tri-state logic.
Lab & Project: Project construction continues.

Week 11: 11/17-19 **Project week 4**
Class: Ground loops and opto-isolation.
Lab & Project: Project construction and debugging. 2 sections equalize labs.

Schedule (III)

Week 12: 11/24-25

Class: Microprocessors on FPGAs or phase-lock loops.

Lab & Project: Project debugging and troubleshooting.

Project week 5

Week 13: 12/1-3

Class: Oral presentations and website launch.

Lab & Project: Device performance testing and review.

Project week 6

Introduction to Digital Logic

Digital Variables

A digital circuit has only 2 possible values HIGH (H or 1) and LOW (L or 0)

→ Does not need to be precision designed.

→ Not very sensitive to electronic noise.

Here are a few voltage-logic conventions:

Convention	Supply	LOW	HIGH	Speed
TTL	+ 5 V	< 0.7 V	> 2.0 V	~5 nS
LVTTL	+ 3.3 V	< 0.7 V	> 2.0 V	~5 nS
CMOS	+ 3-15 V	< 20% Supply	> 80% Supply	~10 nS
GaAs	undefined	undefined	undefined	~100 pS

Digital vs. Analog

Digital

- Easy to design (linear logic flow).
 - No feedback !
- Insensitive to electronic noise.
- Easy to design and make very complex circuits.
- Insensitive to specific components.
- Reliable isolation circuitry.
- Tends to consume a lot of power.
- Slower than analog equivalent.
- Very bad if a single bit is corrupted (std. error rate 1 part per 10^{10}).
 - Error correction is important.

Analog

- Harder to design and read a circuit, especially with feedback.
- Noise is critical.
- Complex circuits are hard to design.
- Sensitive to specific components and quality of assembly.
- Isolation circuitry reduces accuracy.
- Very fast.
- Can be low power.
- Some circuits must be analog.

Transistor-Transistor-Logic (TTL)

In this course, we will use almost exclusively the TTL family of logic chips.

Characteristics:

- Very reliable.
- Widely available.
- Silicon-based with bipolar transistors.
- Supply: + 5 V, High > 2 V, Low < 0.7 V
- 1 output can drive 10 inputs (fanout = 10).
- Never leave an input (or output) floating: it will tend to wander between H and L.


CAUTION: If any of your voltages are close to the range 0.7 – 2.0 V, then you should check your circuit and the components.

Boolean Operators

Identity

1 input \rightarrow 1 output

0 input \rightarrow 0 output

 


(also called a buffer)

Inverter

1 input \rightarrow 0 output

0 input \rightarrow 1 output

 

Note: Boolean (adj.) refers to something that is 2-valued (named after G. Boole, 1815-1864).

2-input operators

AND

→ Outputs H only if both inputs are H.

→ Written as a product:
 $Y=AB$



INPUTS		OUTPUT
A	B	$AB = Y$
L	L	L
L	H	L
H	L	L
H	H	H

OR

→ Outputs H only if either input is H.

→ Written as a sum:
 $Y=A+B$



INPUTS		OUTPUT
A	B	$A+B = Y$
L	L	L
L	H	H
H	L	H
H	H	H

More operators

NAND



INPUTS		OUTPUT
A	B	$\overline{AB} = Y$
L	L	H
L	H	H
H	L	H
H	H	L

NOR




INPUTS		OUTPUT
A	B	$\overline{A+B} = Y$
L	L	H
X	H	L
H	X	L

X = don't care (H or L)

A little bit of analog

Analog realization of a NOR gate

 

INPUTS		OUTPUT
A	B	$\overline{A+B} = Y$
L	L	H
X	H	L
H	X	L

Boolean logic identities

Associative

$$ABC = (AB)C = A(BC)$$

$$A+B+C = (A+B)+C = A+(B+C)$$

Commutative

$$AB = BA$$

$$A+B = B+A$$

Others

$$AA = A$$

$$A1 = A$$

$$A0 = 0$$

$$A+A = A$$

$$A+1 = 1$$

$$A+0 = A$$

$$A + AB = A$$

$$A+BC = (A+B)(A+C)$$

$$A + \bar{A} = 1$$

$$A \bar{A} = 0$$

$$A + \bar{A} B = A+B$$

DeMorgan's Theorem

$$\overline{A+B} = \bar{A} \bar{B}$$

$$\overline{AB} = \bar{A} + \bar{B}$$

Exclusive OR

XOR


→ Outputs H if either input is H, but not both.

→ Written as a plus sign with a circle around it: $Y=A\oplus B$

INPUTS		OUTPUT
A	B	$A\oplus B = Y$
L	L	L
L	H	H
H	L	H
H	H	L



XOR realization

 

[diagram courtesy of Altera Inc.]

The NAND and NOR gates

DeMorgan's theorem corollary:

Any logic gate or operation can be constructed exclusively of NAND gates (or NOR gates).

Note: a NAND gate with the inputs tied together is a NOT gate.

Hardware



Name	Expression	Inputs	Part #
AND	AB	2 (also 3&4)	74xx08
NAND	\overline{AB}	2 (also 3&4)	74xx00
OR	$A+B$	2 (also 3&4)	74xx32
NOR	$\overline{A+B}$	2 (also 3&4)	74xx02
Invert	\overline{A}	1	74xx04
Buffer	A	1	74xx365
XOR	$A\oplus B$	2 (also 3&4)	74xx86 / 386
XNOR	$\overline{A\oplus B}$	2 (also 3&4)	74xx266

Note: We will use mostly Low Speed TTL (xx = LS).

  Example: 74LS00

Quad NAND gate chip

- 4 gates per chip.
- Requires + 5 V of power at V_{CC} .
- Requires a ground connection at GND.
- Never float an input (i.e. it will wander between 0 and 1).
- Each gate consists of about 20 components.



Karnaugh Maps (I)

Logic table \rightarrow Karnaugh Map \rightarrow digital logic circuit

- Up to 4 inputs, 1 output.
- Always gives a solution, though not the most efficient one.

Example:

- 3 person vote.
- 2-person majority produces H output.

A	B	C	Q
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Karnaugh Maps (II)

- Arrange inputs on either one of the two table axes.
 - Up to 2 inputs per axis.
 - Order of inputs is important: only one input change per row or column.
- (note: column order is circular.)

	A	L	L	H	H
	B	L	H	H	L
C					
L		L	L	H	L
H		L	H	H	H

Karnaugh Maps (II)

- Arrange inputs on either one of the two table axes.
- Up to 2 inputs per axis.
- Order of inputs is important: only one input change per row or column.
- Group together the adjacent “ones”: these correspond to AND gates.
- Alternatively, group adjacent “zeros”: these correspond to OR gates.
- Write down the corresponding AND gates: AB, BC, AC

C \ A B	L	L	H	H
	L	L	H	L
H	L	H	H	H
		BC	AB	AC

Solution: $AB + BC + AC$

Karnaugh Maps (III)

		A	0	0	1	1
		B	0	1	1	0
C	D					
	0	0	1	1	0	1
0	1	0	1	0	0	
1	1	0	1	1	0	
1	0	1	1	1	0	

Karnaugh Maps (III)

		A	0	0	1	1
		B	0	1	1	0
C	D					
	0	0	1	1	0	1
0	1	0	1	0	0	
1	1	0	1	1	0	
1	0	1	1	1	0	

The Karnaugh map shows the following groupings:

- A red vertical group of four 1s at (C,D) = (0,0), (0,1), (1,1), and (1,0).
- A blue horizontal group of four 1s at (C,D) = (0,0), (0,1), (1,1), and (1,0).
- A green horizontal group of two 1s at (C,D) = (0,0) and (1,0).
- Two dashed orange circles around the 1s at (C,D) = (0,0) and (0,4).

Karnaugh Maps (III)

		A			
		0	0	1	1
C \ D		B			
		0	1	1	0
0	0	1	1	0	1
0	1	0	1	0	0
1	1	0	1	1	0
1	0	1	1	1	0

Solution: $\bar{A}B + BC + \bar{A}\bar{D} + \bar{B}\bar{C}\bar{D}$

Binary Numbers

Base 10 (i.e. decimal numbers)

$$73691 = 1 \times 10^0 + 9 \times 10^1 + 6 \times 10^2 + 3 \times 10^3 + 7 \times 10^4 = 73691_{10}$$

We can represent any integer in a digital circuit if we use base-2 representation.

Base 2 (i.e. binary numbers)

$$\begin{aligned} 10011101 &= 1 \times 2^0 + 0 \times 2^1 + 1 \times 2^2 + 1 \times 2^3 + 1 \times 2^4 + 0 \times 2^5 + 0 \times 2^6 + 1 \times 2^7 = 10011101_2 \\ &= 1 + 0 + 4 + 8 + 16 + 0 + 0 + 128 = 157_{10} \end{aligned}$$

Binary Numbers

Base 10 (i.e. decimal numbers)

$$73691 = 1 \times 10^0 + 9 \times 10^1 + 6 \times 10^2 + 3 \times 10^3 + 7 \times 10^4 = 73691_{10}$$

We can represent any integer in a digital circuit if we use base-2 representation.

Base 2 (i.e. binary numbers)

$$1001\textcircled{1}101 = 1 \times 2^0 + 0 \times 2^1 + 1 \times 2^2 + 1 \times 2^3 + 1 \times 2^4 + 0 \times 2^5 + 0 \times 2^6 + 1 \times 2^7 = 10011101_2$$

$$\text{1-bit} = 1 + 0 + 4 + 8 + 16 + 0 + 0 + 128 = 157_{10}$$

8-bits = 1 byte

Binary Numbers

Base 10 (i.e. decimal numbers)

$$73691 = 1 \times 10^0 + 9 \times 10^1 + 6 \times 10^2 + 3 \times 10^3 + 7 \times 10^4 = 73691_{10}$$

We can represent any integer in a digital circuit if we use base-2 representation.

Base 2 (i.e. binary numbers)

$$1001\textcircled{1}101 = 1 \times 2^0 + 0 \times 2^1 + 1 \times 2^2 + 1 \times 2^3 + 1 \times 2^4 + 0 \times 2^5 + 0 \times 2^6 + 1 \times 2^7 = 10011101_2$$

$$\text{1-bit} = 1 + 0 + 4 + 8 + 16 + 0 + 0 + 128 = 157_{10}$$

8-bits = 1 byte

Base 16 (i.e. Hexadecimal numbers)

0, 1, 2, 3, 4, 5, 6, 7, 8, 9, A, B, C, D, E, F

Decimal → Binary

- To convert from decimal to binary
 - Divides by 2 repeatedly & write the remainders
- To convert 13_{10} to binary
 - $13/2 = 6$ remainder 1
 - $6/2 = 3$ remainder 0
 - $3/2 = 1$ remainder 1
 - $1/2 = 0$ remainder 1
- The digits come out in **right to left** order
 - $13_{10} = 1101_2$

Binary Addition

➤ Examples

$$0101_2 + 0010_2 = 0111_2$$

$$0101_2 + 0001_2 = 0110_2$$

$$0111_2 + 0001_2 = 1000_2$$

➤ Differences between decimal & binary addition...

- In binary we, on average, carry half the time.
- There are only a limited number of possible operands & resultants (1s or 0s).
- Makes digital implementation fairly simple.